


LM3401 MR16 Reference Designs for Non-Dimming & Dimming LED Applications

February 18, 2011
Revision 1.1

Table of Contents

MR16 Halogen/SSL Retro-Fit Analysis	3
Differences between Magnetic and Electronic Transformers	3
SSL MR16 lamps compatibility concerns with ELVT and ELV dimmers (true retro-fit)	3
Halogen vs SSL MR16 waveforms	4
Halogen MR16	5
LM3401 Standard Reference Design.....	7
Operating Specifications	7
Final PCB Schematic	8
PCB Layout	8
LM3401 Standard Schematic	9
Standard LM3401 PCB Photo (top/bottom)	9
MR16 with LM3401 driver board and CREE MT-G LED	9
Bill of Materials	10
Current Sense Configuration Variants	10
Typical Performance (Two series LEDs @ 1.0A).....	11
LM3401 Dimming Waveforms	14
Thermal Analysis	16
Reference Design Transformer Compatibility	17
LM3401 Standard Reference Design (Two Series Connected LEDs @ 1.0A)	18
Performance without transformer	18
Performance with transformer	19
LM3401 Standard Reference Design (Three Series Connected LEDs @ 600mA)	19
Performance without transformer	19
Performance with transformer	20
Revision History.....	21

MR16 Halogen/SSL Retro-Fit Analysis

Differences between Magnetic and Electronic Transformers

Magnetic Transformers

Magnetic transformers step down 120VAC line voltage to 12VAC. Magnetic transformers consist only of magnetic core, and copper wire, no electronics are used to step down the voltage from 120VAC to 12VAC. Due to the fact that the frequency of operation is 50Hz or 60Hz, the size of the Magnetic transformers is large and heavy. Magnetic transformers are primarily available in two types of construction; toroidal and laminated EI core.

With existing Halogen MR16 systems that require dimming, Magnetic Low Voltage Dimmers are required to be used.

Electronic Transformers

Electronic transformers also step down 120VAC line voltage to 12VAC. Electronic transformers are much smaller and more efficient than magnetic transformers. Electronic transformers are more common than magnetic transformers in existing Halogen MR16 system. Electronic Low Voltage Transformers (ELVT) consists of a small self resonant tank power supply. Electronic Low Voltage Dimmers (ELV dimmers) are used with ELVT for dimming systems.



Although electronic transformers are more complex, with many more components, than their magnetic counterparts, electronic transformers are far less expensive and smaller. The sheer amount of core material and copper within a magnetic transformer adds cost, and the weight of the product makes it expensive to manufacture, and ship.

SSL MR16 lamps compatibility concerns with ELVT and ELV dimmers (true retro-fit)

Electronic transformers modulate (PWM) the input AC voltage with a frequency of 35 kHz to 150 kHz. This waveform is step-down from 120V or 230V (typical) to 12VAC with a transformer. The higher switching frequency allows for the smaller magnetic components, and the overall smaller design. As mentioned earlier, the electronic transformer is a self driven resonant half bridge topology. The self resonance half-bridge topology requires the converter to have a minimal load at all times to function properly. Common minimum loads for ELV dimmers are from 6W – 12W depending on manufacture, and maximum power rating of the ELVT. With traditional Halogen lamps, the minimal load is of no concern, common Halogen MR16 lamps use about 50W of power per lamp. These lamps are very inefficient, and 10W of Halogen power produces very little light.

With the current efficacy of the LEDs above 100 lumens per watt, 6W of SSL power is equivalent to about 40W to 50W of Halogen power. One can quickly see the compatibility issue of SSL MR16 lamps and the ELVT's. If the output power of the ELVT reduces below the minimum requirement, the ELV dimmer will stop operating. The turning on, and off of the ELVT will cause visible flicker from the SSL MR16 lamp, and could also cause reliability issues with the lamp or ELVT.

Halogen vs SSL MR16 waveforms

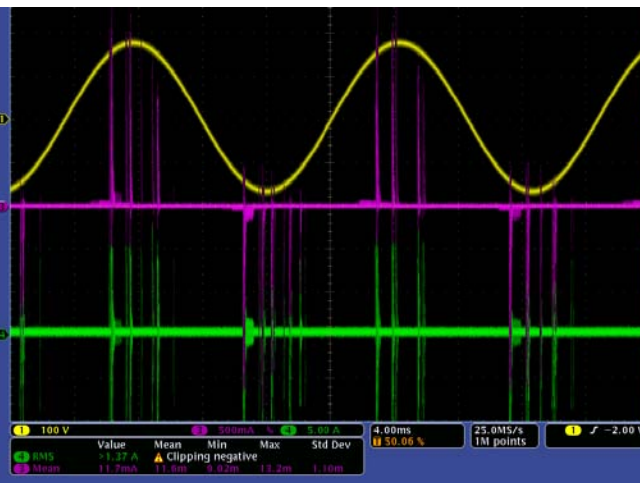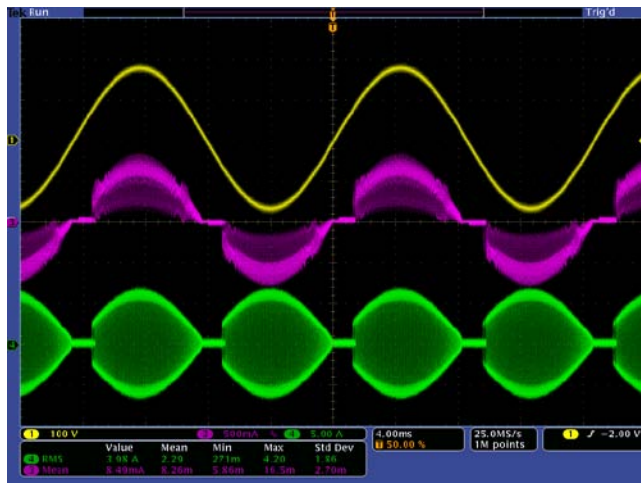

- Channel - 1 (yellow trace) = Input line voltage
- Channel - 3 (purple trace) = Input line current
- Channel - 4 (green trace) = bulb current

Issue #1 - The two scope captures above illustrate the SSL MR16 technical challenges. Figure one shows typical Halogen MR16 waveforms, and figure two is common MR16 replacement bulbs waveforms. The SSL replacement bulb looks capacitive to the ELVT; therefore large current spikes charge the energy storage device within the SSL MR16 bulb. The switching converter within the bulb then processes the input power from the energy storage element to the LED load. At this time the minimum load requirement of the ELVT is not satisfied, and the ELVT turns off. Once the energy is depleted within the MR16 converter, the ELVT will start up, and the process cycles. The turning off/on of the ELVT will manifest itself as visible flicker.



Issue #2 – The maximum input current to the Halogen bulb is approximately 4.25A. The maximum input current to the SSL bulb is approximately 12A. The large magnitude spike associated with charging the SSL MR16 input capacitor can cause premature failures within the SSL bulb, or even the ELVT.

Halogen MR16


Summary: No flickering observed. There is a delay (1.12ms, 24° angle) from when the supply voltage starts ramping up from zero volts to when the electronic transformer starts to operate and the bulb turns on. This delay shows up on the LED MR16s as well although the magnitude of delay does vary from bulb to bulb. No current spikes observed out of the transformer.



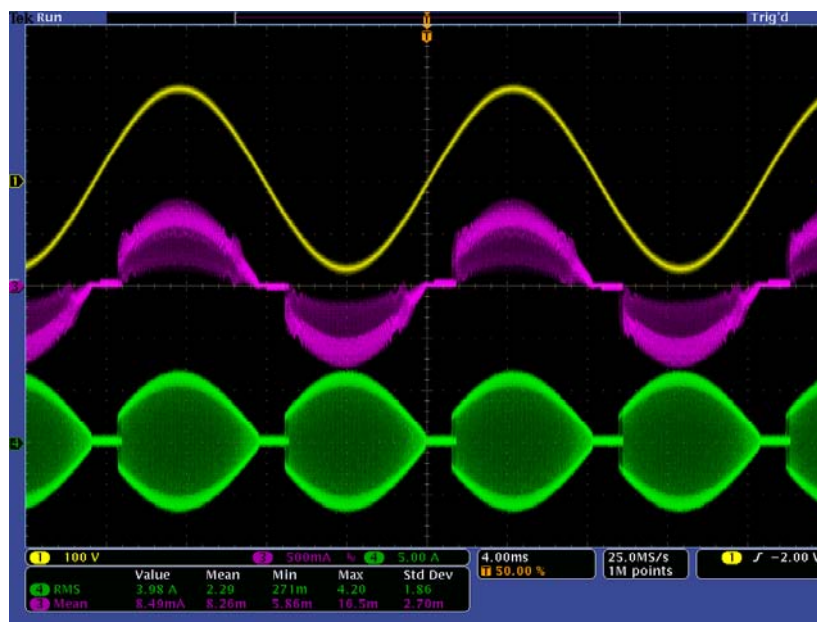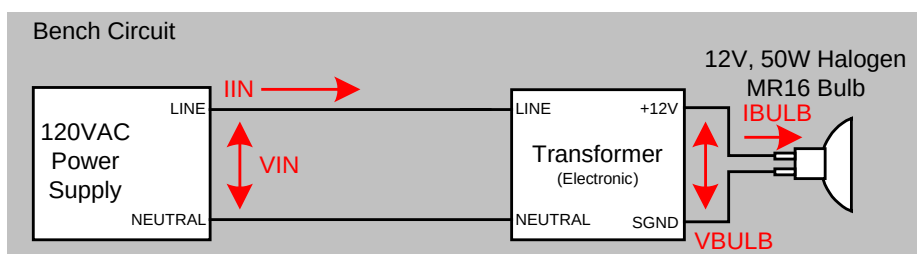
The bench set-up diagram below was used in the evaluation of the halogen MR16 bulb. The following scope plots show voltage and current waveforms designated by the labels indicated in the bench set-up diagram. The electronic transformer used was the Lightech LET-75.



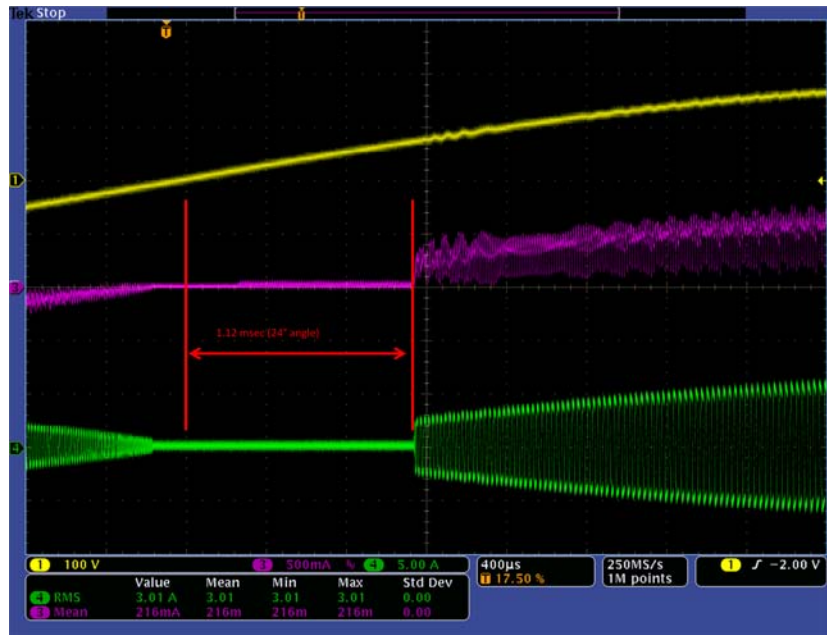VIN (Yellow), IIN (Magenta), IBULB (Green)



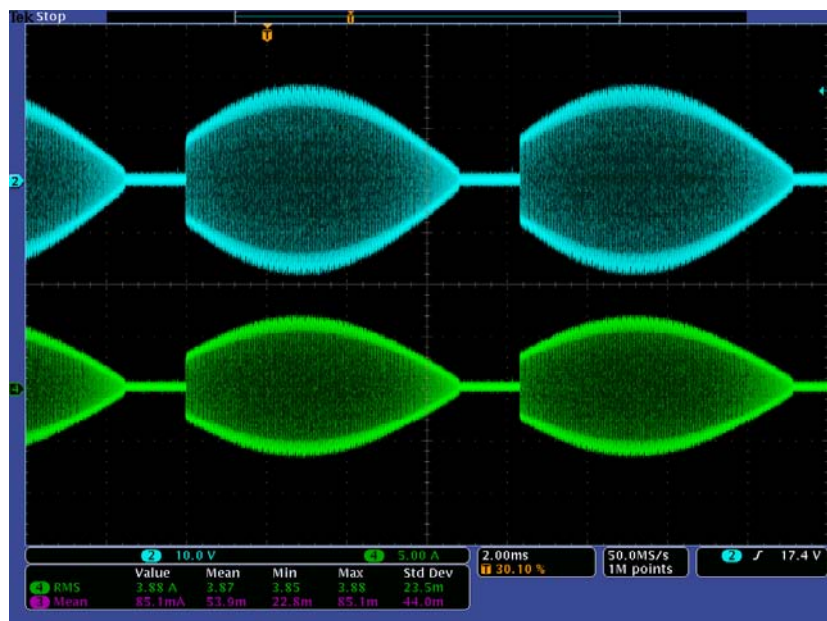VIN (Yellow), IIN (Magenta), IBULB (Green)



VBULB (Blue), IBULB (Green)

LM3401 Standard Reference Design

This reference design was based on the released LM3401 IC from National Semiconductor. A common LM3401 reference board is available today: <http://www.national.com/pf/LM/LM3401.html#Overview>

A MR16 specific evaluation PCB is currently being manufactured for customers, please contact your National Semiconductor representative.

This design was developed to minimize the current spikes coming out of an electronic transformer to less than 5A, which is a typical transformer rating, when driving an LED MR16 circuit. The off the shelf LED MR16 solutions exhibit spikes that significantly exceed a transformer's maximum rated output current which will degrade the reliability of the transformer and reduce its operating lifetime.


This design also generates a constant LED current over most of the power cycle when an electronic transformer is on versus the short bursts of current applied to an LED stack from the off the shelf LED MR16 bulbs. This results in better power factor and more stable circuit operation.

Operating Specifications


NOTE: The following specifications are typical values based on the LED driver being powered directly by a 12VAC supply (i.e. no electronic or magnetic step-down transformer).

Input Voltage, V_{IN} :	 12 VAC
Output Voltage, V_{OUT} :	 6.2V (Single string of 2 LEDs)
Input Current, I_{IN} :	 650mA
LED Output Current, I_{LED} :	 1.0 A
Input Power, P_{IN} :	 ~ 7.7W
Output Power, P_{OUT} :	 ~ 6.2W
Efficiency:	 ~ 81 %
Power Factor:	 0.85
SMPS Topology:	 Buck


Final PCB Schematic

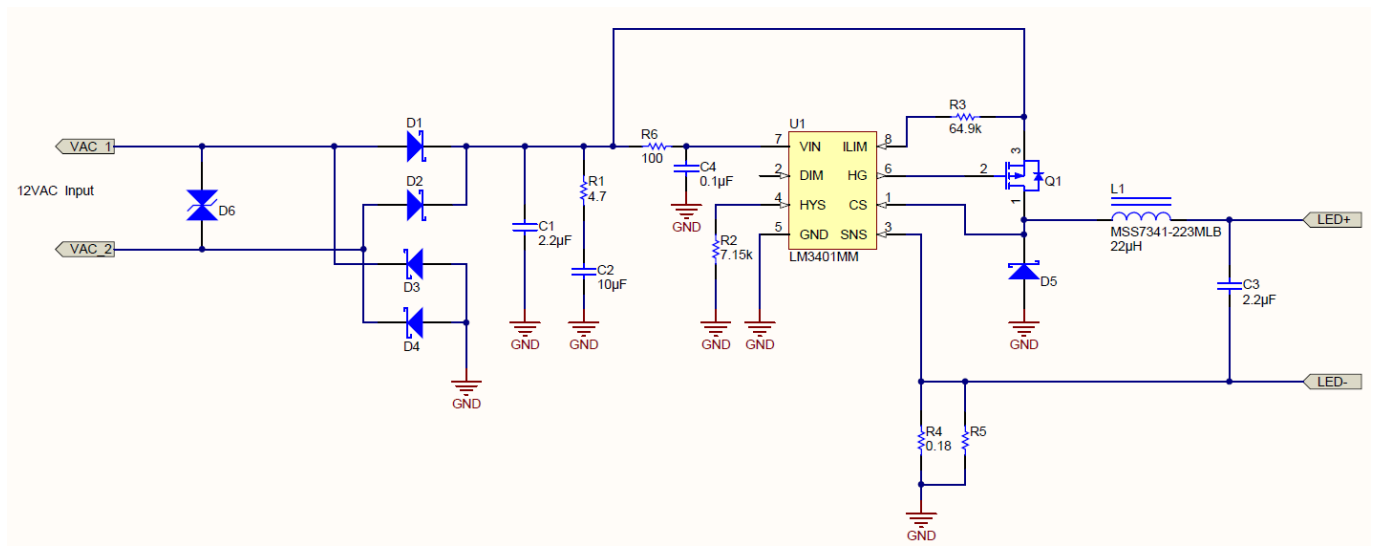


PCB Layout

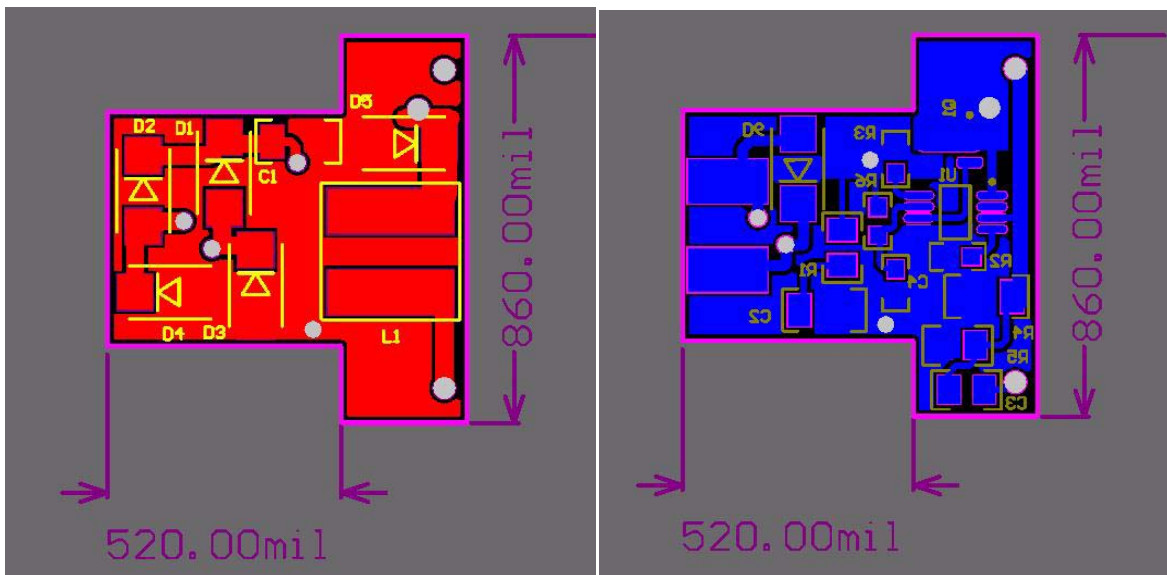

LM3401 Standard Schematic

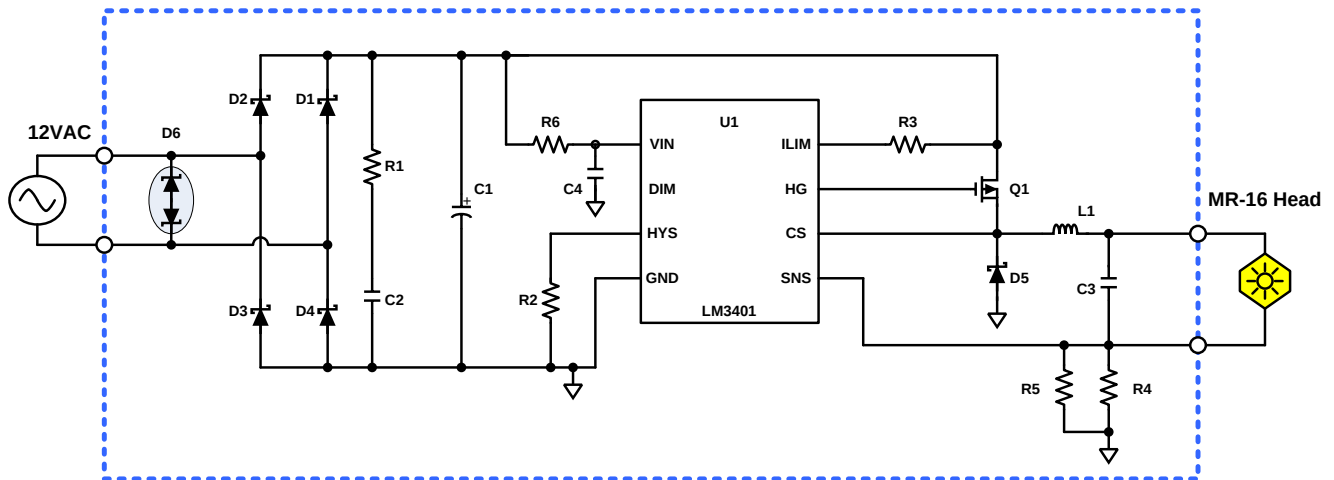

Standard LM3401 PCB Photo (top/bottom)

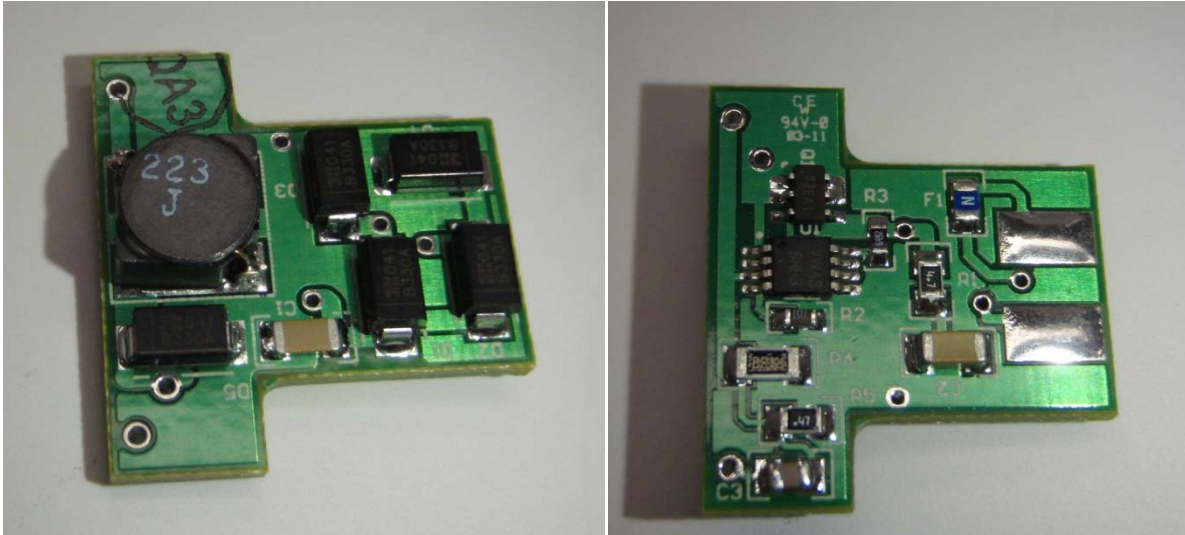

MR16 with LM3401 driver board and CREE MT-G LED



LM3401 with CREE LED and MR16 assembly

Bill of Materials

Designator	Description	MFG	Part Number
C1	CAP, CERM, 2.2uF, 25V, +/-10%, X5R, 1206	MuRata	GRM316R61E225KA12D
C2	CAP, CERM, 10uF, 25V, +/-10%, X5R, 1206	MuRata	GRM31CR61E106KA12L
C3	CAP, CERM, 2.2uF, 16V, +/-10%, X7R, 0805	MuRata	GRM21BR71C225KA12L
C4	CAP, CERM, 0.1uF, 25V, +/-10%, X7R, 0603	MuRata	GRM188R71E104KA01D
D1-D5	Diode, Schottky, 30V, 3A, SMA	Diodes Inc.	B330A-13-F
D6	TVS BI-DIR 24V 400W SMA (Optional)	Diodes Inc	SMAJ24CA-13-F
F1	Fuse, SMD, 2A, 0805		MFU0805FF02000P100
L1	Ind, Shielded Core, Ferrite, 22uH, 1.42A, 0.082 ohm, SMD	Coilcraft	MSS7341-223MLB
Q1	MOSFET, P-CH, -30V, -4A, SOT-23-6	Fairchild	FDC658AP
R1	RES, 4.7 ohm, 5%, 0.125W, 0805	Panasonic	ERJ-6GEYJ4R7V
R2	RES, 7.15k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06037K15FKED
R3	RES, 64.9k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060364K9FKEA
R4	RES, 0.18 ohm, 1%, 0.25W, 1206		
R5	See variants below		
R6	RES, 100 ohm, 1%, 0.1W, 0603 (optional 0 ohm)	Vishay-Dale	CRCW0603100R
U1	Hysteretic PFET Controller for High Power LED Drive	National Semiconductor	LM3401MM



Current Sense Configuration Variants

Series LEDs	V_{LED}	I_{LED}	R4	R5
2	~ 6V	1.0 A	0.18 Ω	0.47 Ω
3	~ 9V	700 mA	0.18 Ω	open


Typical Performance (Two series LEDs @ 1.0A)

The following scope plots show voltage and current waveforms designated by the labels indicated in the following bench set-up diagram. This bench set-up was used in the evaluation of the LM3401 Standard MR16 design. The electronic transformer used was the Lightech LET-75.


Bench Circuit

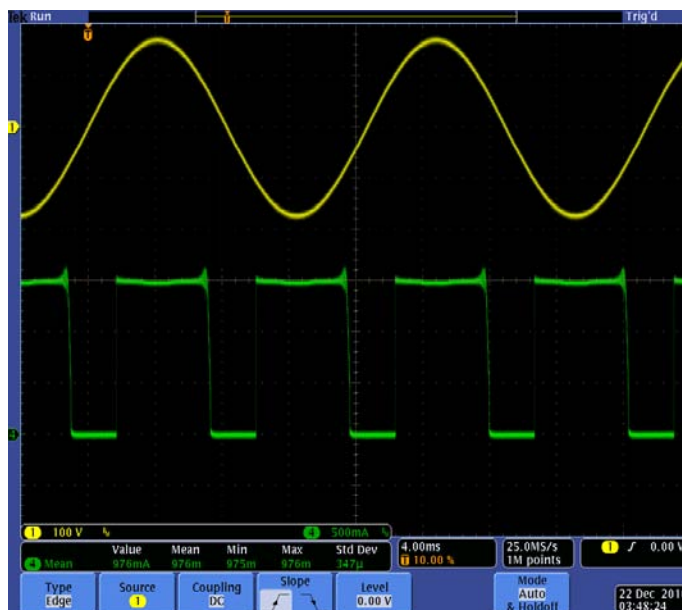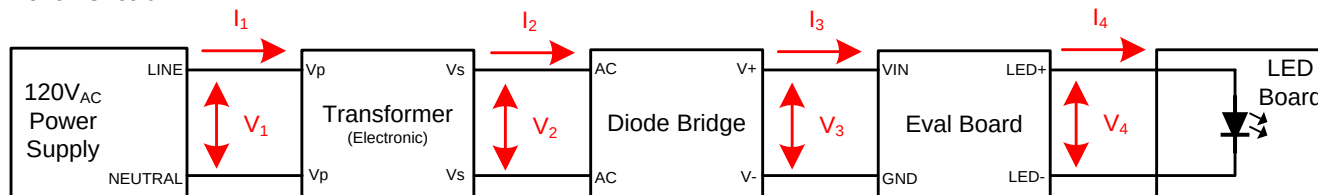


CH1 V1 Voltage, CH4 I4 Current

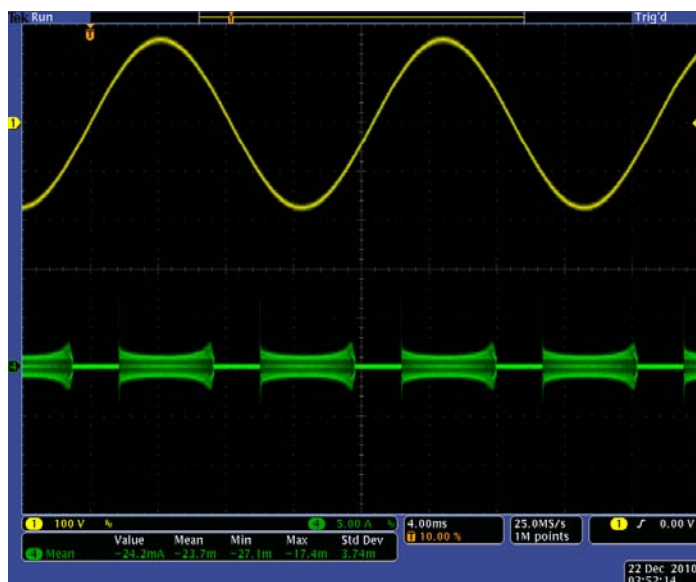


CH1 V1 Voltage, CH4 I2 Current

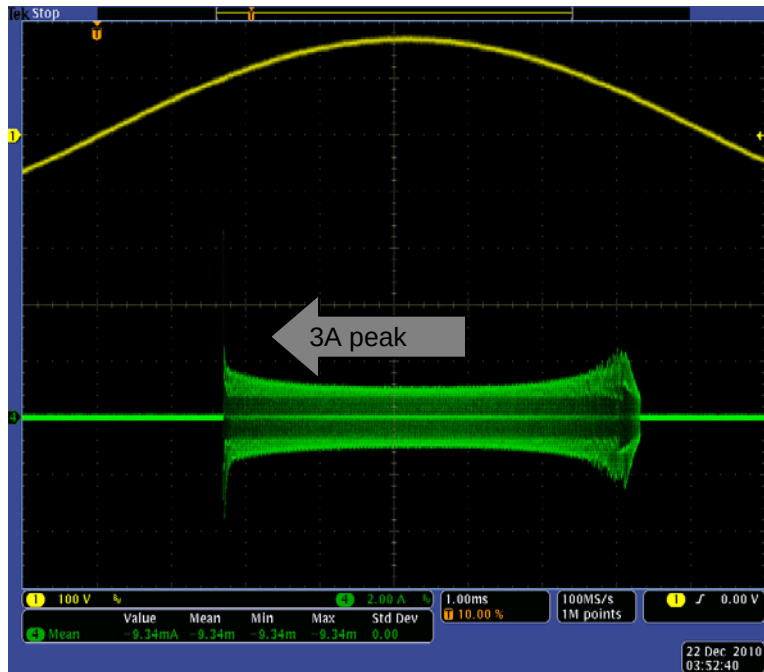

CH1 V1 Voltage, CH4 I2 Current

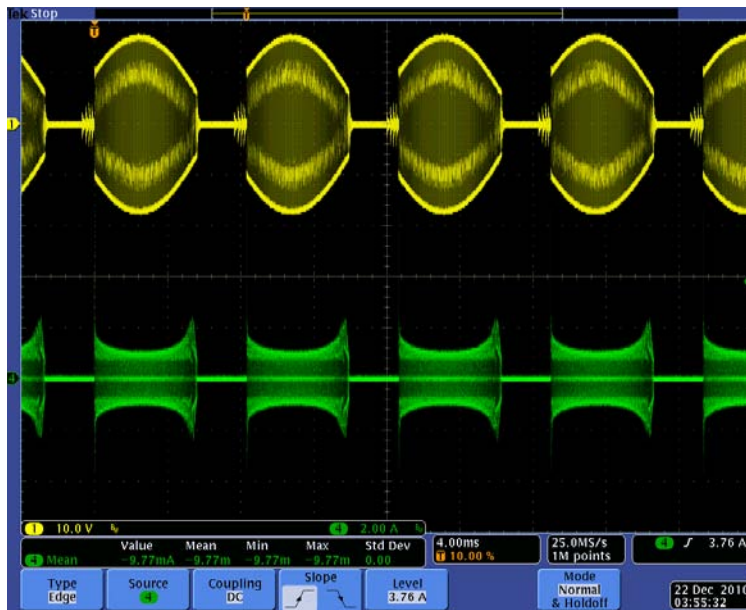

CH1 V2 Voltage, CH4 I2 Current

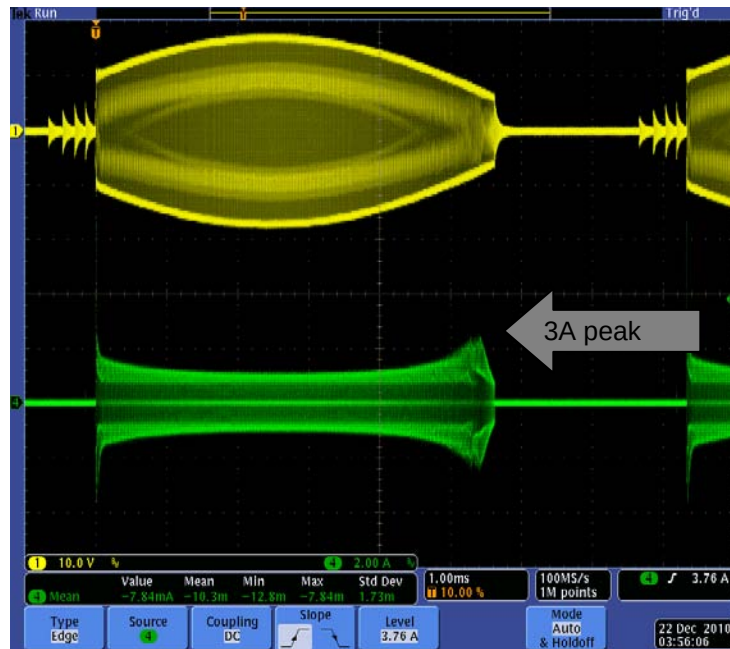


CH1 V2 Voltage, CH4 I2 Current

LM3401 Dimming Waveforms


This LM3401 evaluation board is designed to operate (flicker-free) with common Electronic Low Voltage dimmers, and Electronic Transformers.

- Dimmer Used – Lutron SELV-300P-GR
- Electronic Transformer – Lighttech LET75
- 12:1 contrast ratio


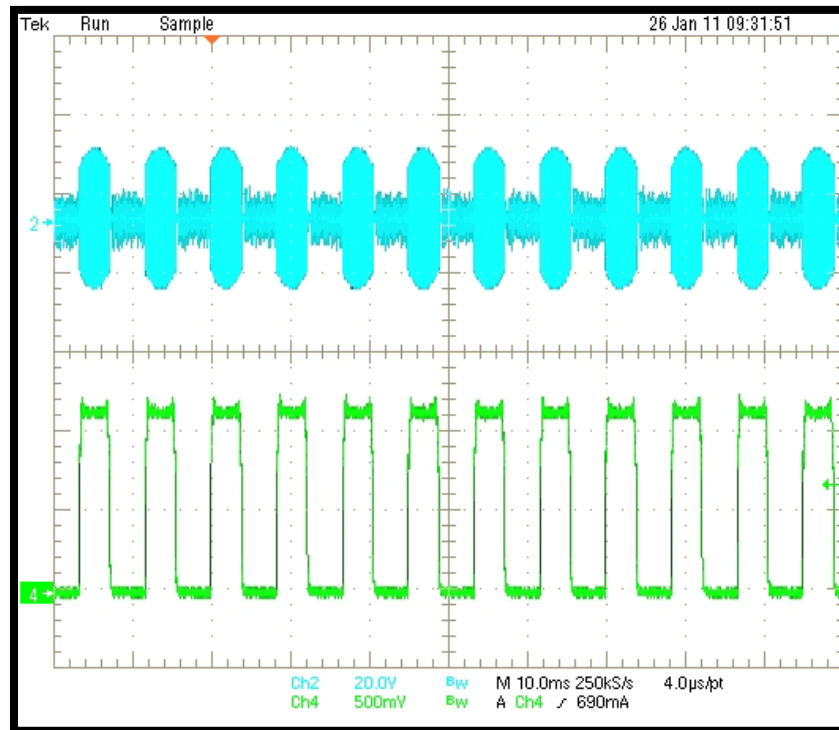
LM3401 Standard Buck - Two series connected LEDs at 1A (90° Conduction Angle)



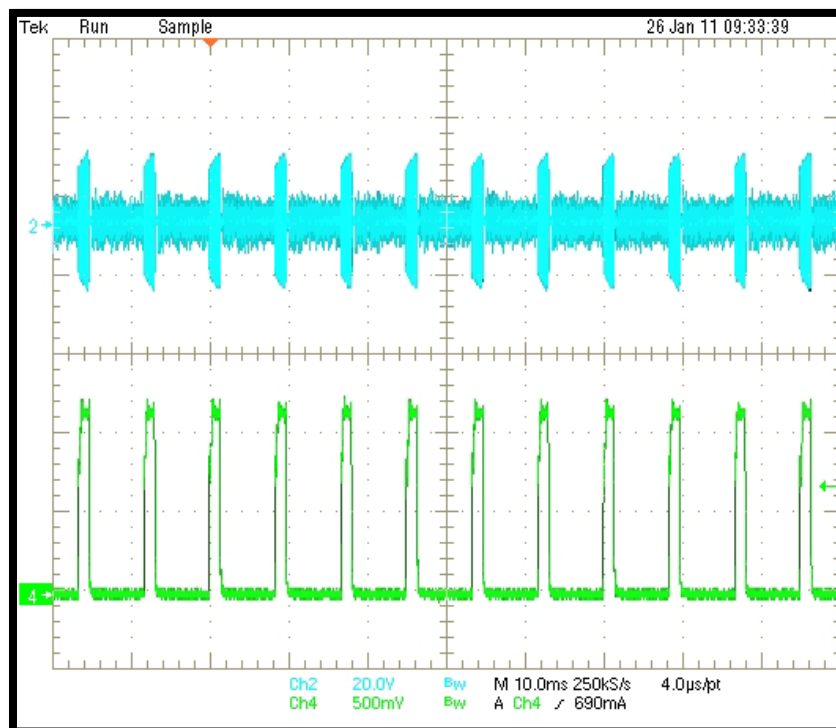LM3401 Standard Buck - Two series connected LEDs at 1A (45° Conduction Angle)



Thermal Analysis

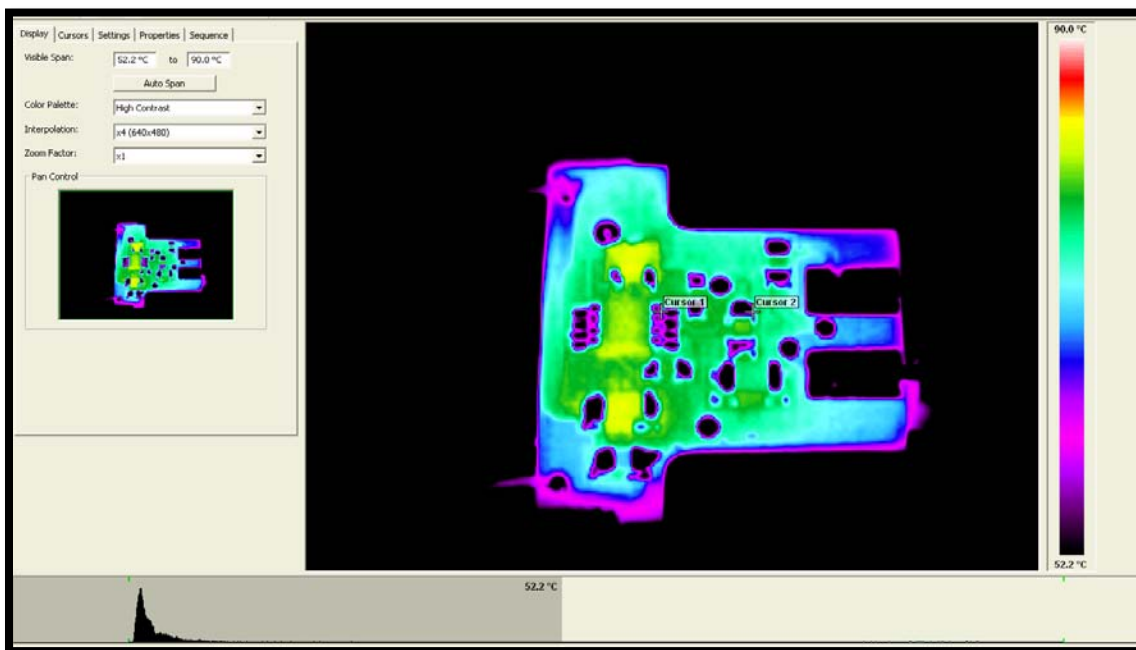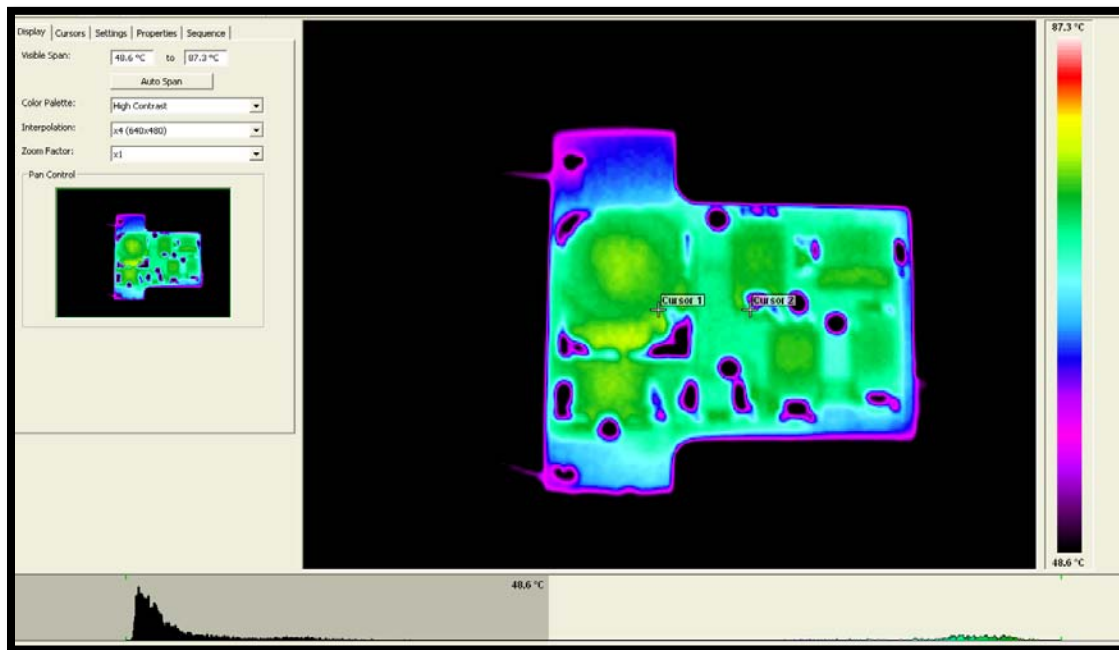

Reference Design Transformer Compatibility

The following transformers were tested with the National LED driver designs described in this document. A compatibility matrix is shown below which describes which driver/transformer combinations are suitable (i.e. no flicker, stable operation).

Electronic Transformers (120VAC to 12VAC):

Lightech, Model: LET-60, 60W

Lightech, Model: LET-75, 75W

Lightech, Model: LET-60 LW, 60W

Hatch, Model: RS12-80M, 85W

Pony, Model: PET-120-12-60, 60W

Eurofase, Model: 0084 CLASS 2, 60W



Magnetic Transformers (120VAC to 12VAC):

Hatch, Model: LS1275EN, 75VA



LM3401 Standard Reference Design (Two Series Connected LEDs @ 1.0A)

Performance without transformer

The table below compares the performance of each reference design when powered directly by a 12VAC source (i.e. no step-down transformer used).

Specs	LM3401 STD CKT 2 LEDs @ 1A	Units
V_{IN}	12.09	VAC
I_{IN}	0.777	A
P_{IN}	8.25	W
$V_{OUT}^{(1)}$	5.81	VDC
$I_{LED}^{(1)}$	1.13	A
$P_{OUT}^{(2)}$	6.94	W
Efficiency	84.1%	-
Power Factor	87.9	-

(1) This is the mean value as measured from oscilloscope waveform.

(2) This is the mean value of the instantaneous P_{OUT} waveform that was mathematically generated (i.e. $V_{OUT} * I_{LED}$) on the oscilloscope.

Performance with transformer

The table below compares the performance of each reference design when powered by a 120VAC source that is stepped down with an electronic transformer (i.e. Hatch, Model: RS12-80M). Since the transformer is not “on” during the full power cycle, power supplied to the LED driver is not constant but instead modulated “on and off” at a duty cycle that matches the “on-state” of the transformer. Operating specifications decrease compared to a system that doesn’t use an electronic transformer.

LET-75

Specs	LM3401 STD CKT 2 LEDs @ 1A	Units
V_{IN}	120.04	VAC
I_{IN}	0.079	A
P_{IN}	7.97	W
$V_{OUT}^{(1)}$	5.65	VDC (1)
$I_{LED}^{(1)}$	1.010	A (1)
$P_{OUT}^{(2)}$	6.23	W (2)
Efficiency	78.2%	-
Power Factor	84.3	-

HATCH

Specs	LM3401 STD CKT	Units
V_{IN}	120.04	VAC
I_{IN}	0.085	A
P_{IN}	8.44	W
$V_{OUT}^{(1)}$	5.79	VDC (1)
$I_{LED}^{(1)}$	1.080	A (1)
$P_{OUT}^{(2)}$	6.71	W (2)
Efficiency	79.5%	-
Power Factor	82.5	-

(1) This is the mean value as measured from oscilloscope waveform.

(2) This is the mean value of the instantaneous P_{OUT} waveform that was mathematically generated (i.e. $V_{OUT} \cdot I_{LED}$) on the oscilloscope.

LM3401 Standard Reference Design (Three Series Connected LEDs @ 600mA)

Performance without transformer

The table below compares the performance of each reference design when powered directly by a 12VAC source (i.e. no step-down transformer used).

Specs	LM3401 STD CKT 3 LEDs @ 0.7A	Units
V_{IN}	12.05	VAC
I_{IN}	0.659	A
P_{IN}	7.33	W
$V_{OUT}^{(1)}$	8.43	VDC
$I_{LED}^{(1)}$	0.700	A
$P_{OUT}^{(2)}$	6.47	W
Efficiency	88.3%	-
Power Factor	0.924	-

- (3) This is the mean value as measured from oscilloscope waveform.
- (4) This is the mean value of the instantaneous P_{OUT} waveform that was mathematically generated (i.e. $V_{OUT} \cdot I_{LED}$) on the oscilloscope.

Performance with transformer

The table below compares the performance of each reference design when powered by a 120VAC source that is stepped down with an electronic transformer (i.e. Hatch, Model: RS12-80M). Since the transformer is not “on” during the full power cycle, power supplied to the LED driver is not constant but instead modulated “on and off” at a duty cycle that matches the “on-state” of the transformer. Operating specifications decrease compared to a system that doesn’t use an electronic transformer.

LET-60

Specs	LM3401 STD CKT 3 LEDs @ 0.7A	Units
V_{IN}	119.94	VAC
I_{IN}	0.069	A
P_{IN}	6.93	W
$V_{OUT}^{(1)}$	8.19	VDC (1)
$I_{LED}^{(1)}$	0.614	A (1)
$P_{OUT}^{(2)}$	5.66	W (2)
Efficiency	81.7%	-
Power Factor	0.849	-

HATCH

Specs	LM3401 STD CKT 3 LEDs @ 0.7A	Units
V_{IN}	119.44	VAC
I_{IN}	0.072	A
P_{IN}	7.24	W
$V_{OUT}^{(1)}$	8.44	VDC (1)
$I_{LED}^{(1)}$	0.651	A (1)
$P_{OUT}^{(2)}$	6.02	W (2)
Efficiency	83.1%	-
Power Factor	0.853	-

- (3) This is the mean value as measured from oscilloscope waveform.
- (4) This is the mean value of the instantaneous P_{OUT} waveform that was mathematically generated (i.e. $V_{OUT} \cdot I_{LED}$) on the oscilloscope.

Revision History

Date	Author	Revision	Description

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated