

AN-1314 LM5020 Evaluation Board

1 Introduction

The LM5020 evaluation board is designed to provide the design engineer with a fully functional non-isolated flyback power converter to evaluate the LM5020 controller.

The performance of the evaluation board is as follows:

- Input range: 30V to 75V (100V peak)
- Output voltage: 3.3V
- Output current: 0.2 to 4.5A
- Measured efficiency: 85% at 1.5A, 83% at 4.5A
- Board size: 1.25 × 2.5 × 0.5 inches
- Load Regulation: 1.5%
- Line Regulation: 0.1%
- Line UVLO, Current Limit

The printed circuit board consists of 2 layers of 2 ounce copper on FR4 material with a total thickness of 0.050 inches. Soldermask has been omitted from some areas to facilitate cooling. The unit is designed for continuous operation at rated load at < 40°C with normal convection cooling.

2 Theory of Operation

The flyback converter is an inductive based converter in which inductive energy is stored by applying a voltage across an inductor in a similar manner to that of a boost converter. Here the similarity ends. A second coupled winding of the inductor transfers the energy to a secondary side rectifier after the voltage has been removed from the first winding. This allows the converter input and output grounds to be configured either isolated or non-isolated. There is also a voltage/current ratio change possible by altering the winding ratio between the first winding and the second winding. A semi-regulated auxiliary winding can also be provided.

The flyback transformer is actually a coupled inductor with multiple windings wound on a single core. For simplification, we will refer to the first, driven winding, as the primary and the main output winding as the secondary winding of the flyback transformer.

The transformer's primary inductance is typically made as large as is practical. However, the airgap necessary to store the cycle energy lowers the obtainable inductance. The higher the primary inductance, the less input ripple current will be generated and the less input filtering will be required.

As shown, the LM5020 directly drives a MOSFET switch to apply voltage across the primary. When the switch turns off, the secondary applies a forward current to the output rectifier and charges the output capacitor. In applications where the input voltage is considerably higher than the output voltage, the turns ratio between primary and secondary will reflect the input/output voltage ratio and the duty cycle.

The LM5020 is a full-featured controller providing an internal start-up regulator, soft start, over-current and under-voltage lockout.

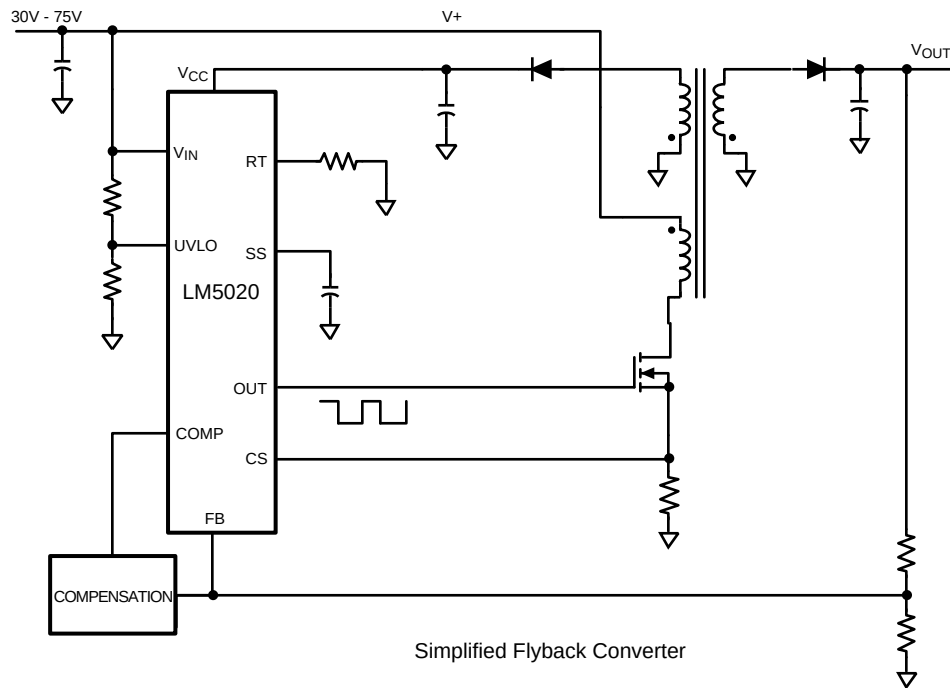


Figure 1. Simplified Flyback Converter

3 Powering and Loading Considerations

When applying power to the LM5020 evaluation board certain precautions should be followed. The LM5020 evaluation board is quite forgiving of load and input power variations. The possibility of shipping damage or infant failure is always a concern at first power-up.

4 Proper Connections

Be sure to choose the correct wire size when attaching the source supply and the load. Monitor the current into and out of the UUT. Monitor the voltages in and out directly at the terminals of the UUT. The voltage drop across the connecting wires will yield inaccurate measurements. For accurate efficiency measurements, these precautions are especially important.

5 Source Power

At low input line voltage (30V) the input current will be approximately 0.63A, while at high input line voltage the input current will be approximately 0.23. Therefore to fully test the LM5020 evaluation board a DC power supply capable of at least 75V and 1A is required. The power supply must have adjustments for both voltage and current. An accurate readout of output current is desirable since the current is not subject to loss in the cables as voltage is.

The power supply and cabling must present a low impedance to the UUT. Insufficient cabling or a high impedance power supply will cause droop during power supply application with the UUT inrush current. If large enough, this droop will cause a chattering condition upon power up. This chattering condition is an interaction with the UUT undervoltage lockout, the cabling impedance and the inrush current.

6 Loading

An appropriate electronic load specified for operation down to 2.0V is desirable. The maximum load current is specified as 4.5A. Minimum load is specified at 5% or 0.23A. The resistance of a maximum load is 0.73Ω (including cables). The resistance of a minimum load is 14.4Ω.

7 Powering Up

Using the shutdown feature provided on the UUT will allow powering up the source supply initially with a low current level. It is suggested that the load be kept reasonably low during the first power up. Set the current limit of the source supply to provide about 1½ times the wattage of the load. As you remove the connection from the shutdown pin to ground, immediately check for 3.3 volts at the output. If more than a couple of seconds pass without seeing an output voltage, remove input power.

A quick efficiency check is the best way to confirm that the UUT is operating properly. If something is amiss you can be reasonably sure that it will affect the efficiency adversely. Few parameters can be incorrect in a switching power supply without creating additional losses and potentially damaging heat. An efficiency above 80% is expected.

After the unit is verified operationally, it can be powered up without use of the shutdown pin.

8 Typical Evaluation Setup

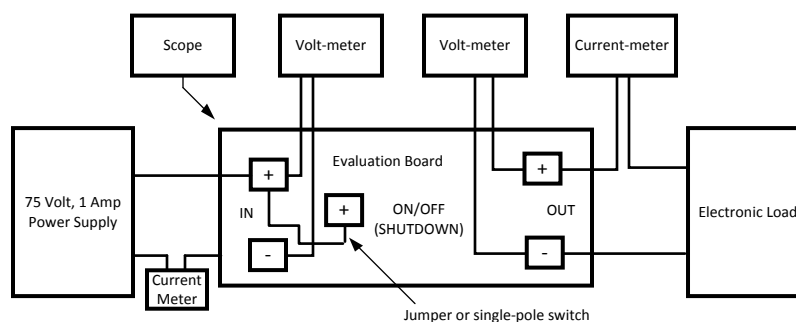



Figure 2. Typical Evaluation Setup

9 Performance Characteristics

9.1 Turn-on Waveforms


When applying power to the LM5020 evaluation board a certain sequence of events must occur. The soft-start feature allows for a minimal output voltage for a short time until the feedback loop can stabilize without overshoot. Figure 3, Figure 4, and Figure 5 show typical turn-on waveforms at no load, 5% load, and at full load. Input voltage, output voltage and output current are shown.

Figure 6 shows the initial ramp-up of the Vcc pin to 7.7 volts through the internal regulator. The auxiliary winding starts to supply a higher voltage as the output voltage rises. The resulting second ramp is shown following the soft-start delay. This sequence is nearly identical for all loads and input voltages.

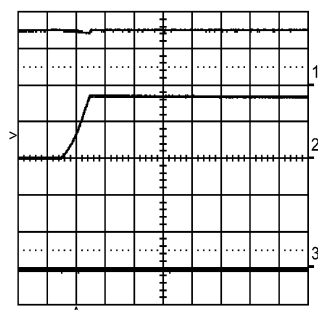


Trace 1: Input Voltage, at 30VDC. Volts/div = 20.0V Trace 2: Output Voltage, no load. Volts/div = 2.0V Trace 3: Output Current, no load. Amps/div = 100mA Horizontal Resolution = 1.0ms/div

Figure 3. Typical Turn-on Waveforms at No Load

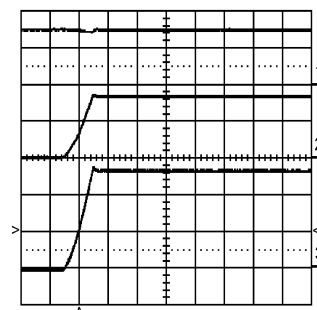


Trace 1: Input Voltage, at 30VDC. Volts/div = 20.0V Trace 2: Output Voltage, at 5% load. Volts/div = 2.0V Trace 3: Output Current, at 5% load. Amps/div = 100mA Horizontal Resolution = 1.0ms/div

Figure 4. Typical Turn-on Waveforms at 5% Load

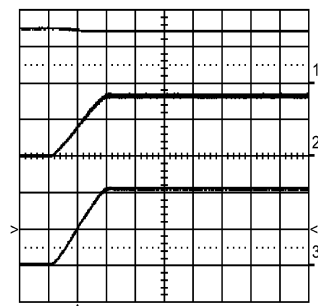

Trace 1: Input Voltage, at 30VDC. Volts/div = 20.0V Trace 2: Output Voltage, at full load. Volts/div = 2.0V Trace 3: Output Current, at full load. Amps/div = 2.0A Horizontal Resolution = 1.0ms/div

Figure 5. Typical Turn-on Waveforms at Full Load

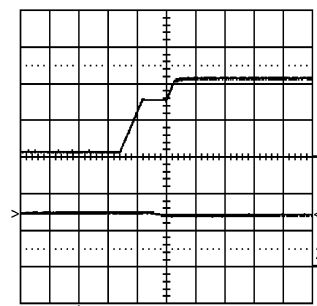

Trace 1: VCC pin with VIN = 30VDC, Load = 4.5A Volts/div = 5.0V Trace 2: VIN approaching 30VDC Volts/div = 20.0V Horizontal Resolution = 2.0ms/div


Figure 6. Initial Ramp-up of the Vcc Pin to 7.7V Through the Internal Regulator

9.2 Load Step Response

Figure 7 shows the load step response at Vin = 30VDC for an instantaneous load change from 5% to full load. The input voltage, output voltage and output current are shown.


9.3 Ripple Voltage and Ripple Current

Figure 8 shows the output ripple voltage, the output ripple current and the input ripple current relative to the LM5020 gate drive.

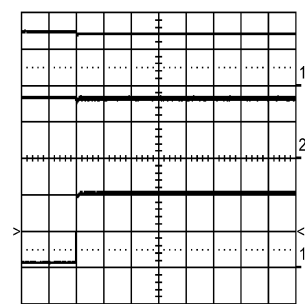

Trace 1: Input Voltage, at 30VDC Volts/div = 20.0V Trace 2: Output Voltage, at 3.3VDC Volts/div = 2.0V Trace 3: Load changing from 0.23A to 4.5A instantaneously Amps/div = 2.0A Horizontal Resolution = 1.0ms/div

Figure 7. Load Step Response at Vin = 30VDC for an Instantaneous Load Change from 5% to Full Load

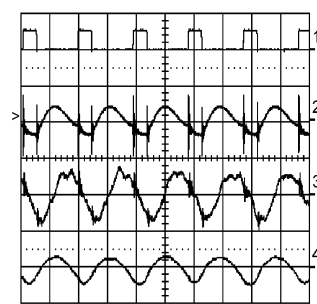


Trace 1: Q1 gate drive at Vin = 48VDC Volts/div = 20.0V Trace 2: Output ripple voltage Volts/div = 100mV Trace 3: Output ripple current Amps/div = 20.0mA Trace 4: Input ripple current Amps/div = 100mA Horizontal Resolution = 2.0μs/div

Figure 8. Output Ripple Voltage, Output Ripple Current, and Input Ripple Current

9.4 Transformer Waveforms

Figure 9, Figure 10, and Figure 11 show typical waveforms at the junction of Q1 MOSFET and the transformer primary winding. Also shown are typical waveforms at the junction of the transformer secondary and the output rectifier, D3. Figure 9 reflects an input voltage of 30VDC and a load of 4.5A. Figure 10 reflects an input voltage of 50VDC with the same load. Figure 11 reflects an input voltage of 75VDC, also at full load.

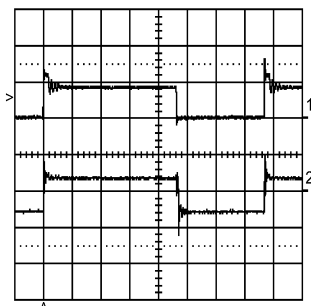


Trace 1: Drain of Q1 at $V_{in} = 30\text{VDC}$; Volts/div = 50.0V

Trace 2: Anode of D3; Volts/div = 10.0V

Horizontal Resolution = 0.5μs/div

Figure 9. Typical Waveforms

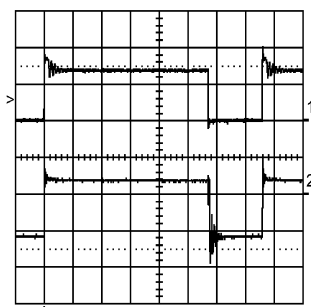


Trace 1: Drain of Q1 at $V_{in} = 50\text{VDC}$; Volts/div = 50.0V

Trace 2: Anode of D3; Volts/div = 10.0V

Horizontal Resolution = 0.5μs/div

Figure 10. Typical Waveforms

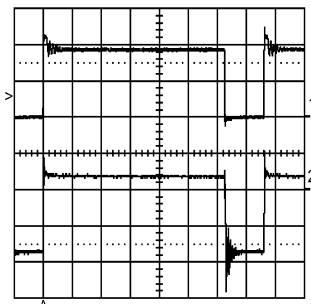

Trace 1: Drain of Q1 at $V_{in} = 75\text{VDC}$; Volts/div = 50.0V

Trace 2: Anode of D3; Volts/div = 10.0V

Horizontal Resolution = 0.5μs/div

Figure 11. Typical Waveforms

10 Bill of Materials


The Bill of Materials is listed in [Table 1](#) and includes the manufacturer and part number.

Table 1. Bill of Materials


Designator	Description	Manufacturer	Part Number
C1	2.2μF, 100V, CER, X7R, 1812	TDK	C4532X7R2A225M
C2	2.2μF, 100V, CER, X7R, 1812	TDK	C4532X7R2A225M
C3	0.01μF, 50V, CER, X7R, 0805	TDK	C2012X7R1H103K
C4	0.1μF, 100V, CER, X7R, 1206	TDK	C3216X7R2A104K
C5	0.01μF, 50V, CER, X7R, 0805	TDK	C2012X7R1H103K
C6	220pF, 50V, CER, COG, 0805	TDK	C2012COG1H221J
C7	3300pF, 50V, CER, COG, 0805	TDK	C2012COG1H332K
C8	100pF, 50V, CER, COG, 0805	TDK	C2012COG1H101J
C9	0.1μF, 50V, CER, X7R, 0805	TDK	C2012X7R1H104K
C10	4.7μF, 16V, CER, X7R, 1206	TDK	C3216X7R1C475K
C11	1000pF, 50V, CER, COG, 0805	TDK	C2012COG1H102J
C12	470pF, 50V, CER, COG, 0805	TDK	C2012COG1H471J
C13	100μF, 4V, CER, X7S, 1812	TDK	C4532X7S0G107M
C14	100μF, 4V, CER, X7S, 1812	TDK	C4532X7S0G107M
C15	270μF, 4V, ALUM ORG, 3018 PKG	KEMET	A700X277M0004AT
D1	DUAL, SIGNAL, COM CATH, SOT-23	CENTRAL SEMICONDUCTOR	CMPD2838E-NSA
D2	DUAL, SIGNAL, COM CATH, SOT-23	CENTRAL SEMICONDUCTOR	CMPD2838E-NSA
D3	SCHOTTKY RECT, 8A, 35V, D2PAK	ON SEMICONDUCTOR	MBRD835L
J1	TERMINAL BLOCK, SCREW, 2 POS	PHOENIX CONTACT	MKDS ½-3.81
J2	TERMINAL BLOCK, SCREW, 2 POS	PHOENIX CONTACT	MKDS ½-3.81
Q1	MOSFET, N-CH, 150V, 85mΩ, PWR SO8	VISHAY/SILICONIX	Si7898DP
R1	10.0Ω, 1%, THICK FILM, 1206	VISHAY	CRCW120610R0J
R2	61.9K, 1%, THICK FILM, 1206	VISHAY	CRCW12066192F
R3	2.87K, 1%, THICK FILM, 0805	VISHAY	CRCW08052871F
R4	1.00K, 1%, THICK FILM, 0805	VISHAY	CRCW08051001F
R5	15.0K, 1%, THICK FILM, 0805	VISHAY	CRCW08051502F
R6	12.4K, 1%, THICK FILM, 0805	VISHAY	CRCW08051242F
R7	100Ω, 1%, THICK FILM, 0805	VISHAY	CRCW08051000F
R8	0.47Ω, 1%, THICK FILM, 1206	VISHAY	CRCW12060R47F
R9	0.47Ω, 1%, THICK FILM, 1206	VISHAY	CRCW12060R47F
R10	10.0Ω, 1%, 1W, THICK FILM, 2512	VISHAY	CRCW251210R0J
R11	2.43K, 1%, THICK FILM, 0805	VISHAY	CRCW08052431F
R12	1.47K, 1%, THICK FILM, 0805	VISHAY	CRCW08051471F
R13	20.0Ω, 1%, THICK FILM, 0805	VISHAY	CRCW080520R0F
SD	TERMINAL, SMALL TEST POINT	KEYSTONE	5002
SYNC	TERMINAL, SMALL TEST POINT	KEYSTONE	5002
T1	TRANSFORMER, FLYBACK, EFD20	COILCRAFT	B0695-A
OR T1	TRANSFORMER, FLYBACK, EFD20	PULSE	PA0751
U1	CONTROLLER, SINGLE OUT, PWM, VSSOP-10	TEXAS INSTRUMENTS	LM5020
Z1	ZENER, 30V, SMB PKG.	ON SEMICONDUCTOR	1SMB5936B

11 PCB Layouts

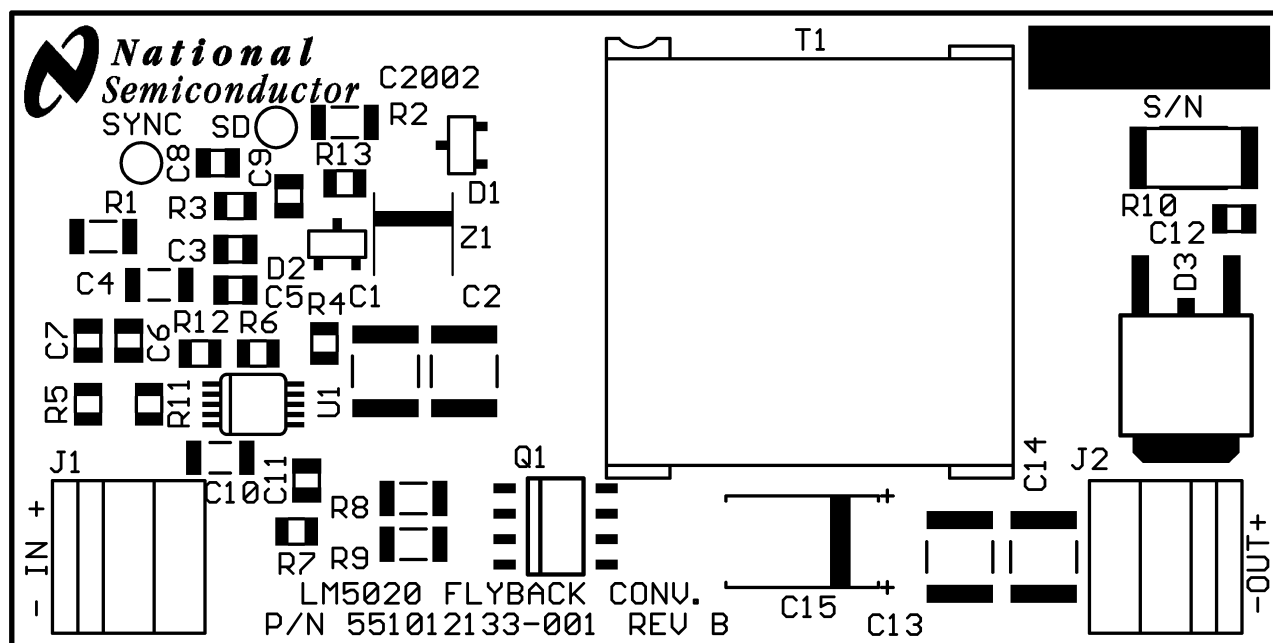
The layers of the printed circuit board are shown in top down order. View is from the top down. Scale is approximately X2.0. The printed circuit board consists of 2 layers of 2 ounce copper on FR4 material with a total thickness of 0.050 inches.




TOP SILKSCREEN

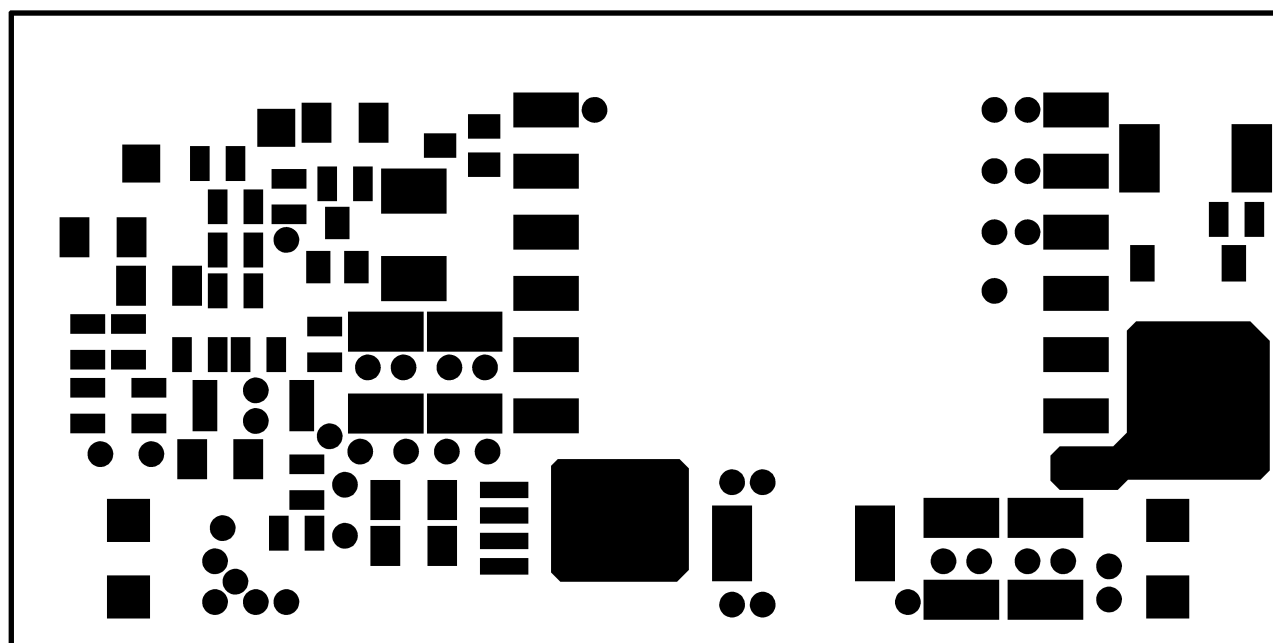


TOP SOLDERMASK

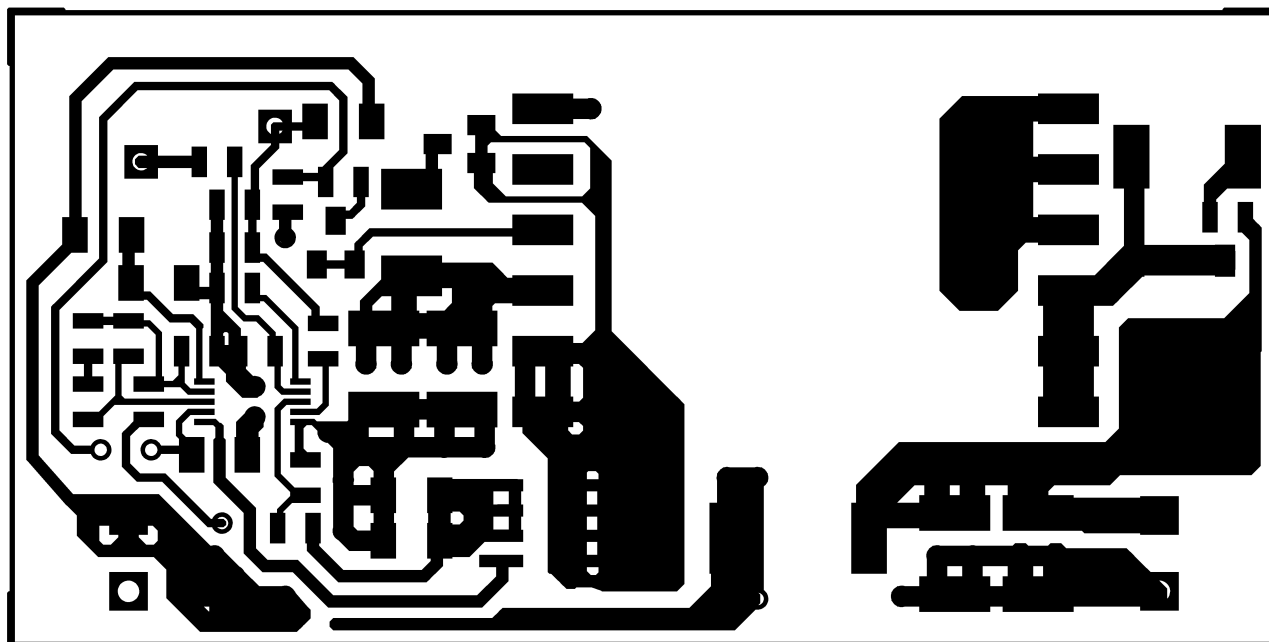

TOP COPPER

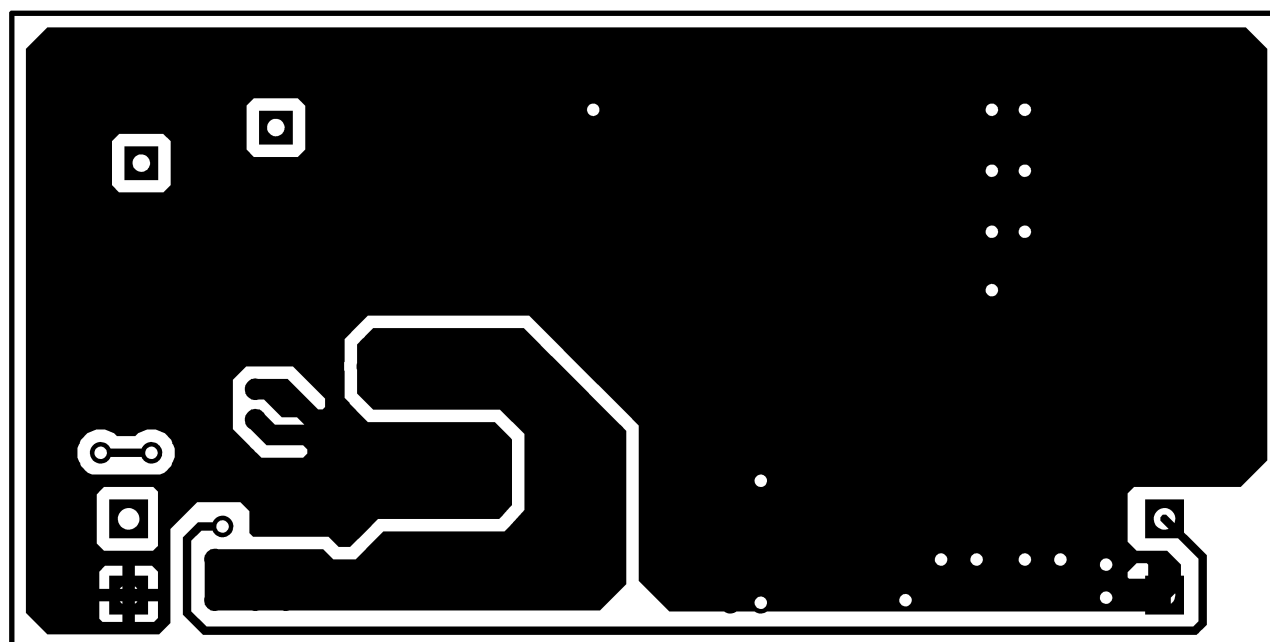

BOTTOM COPPER

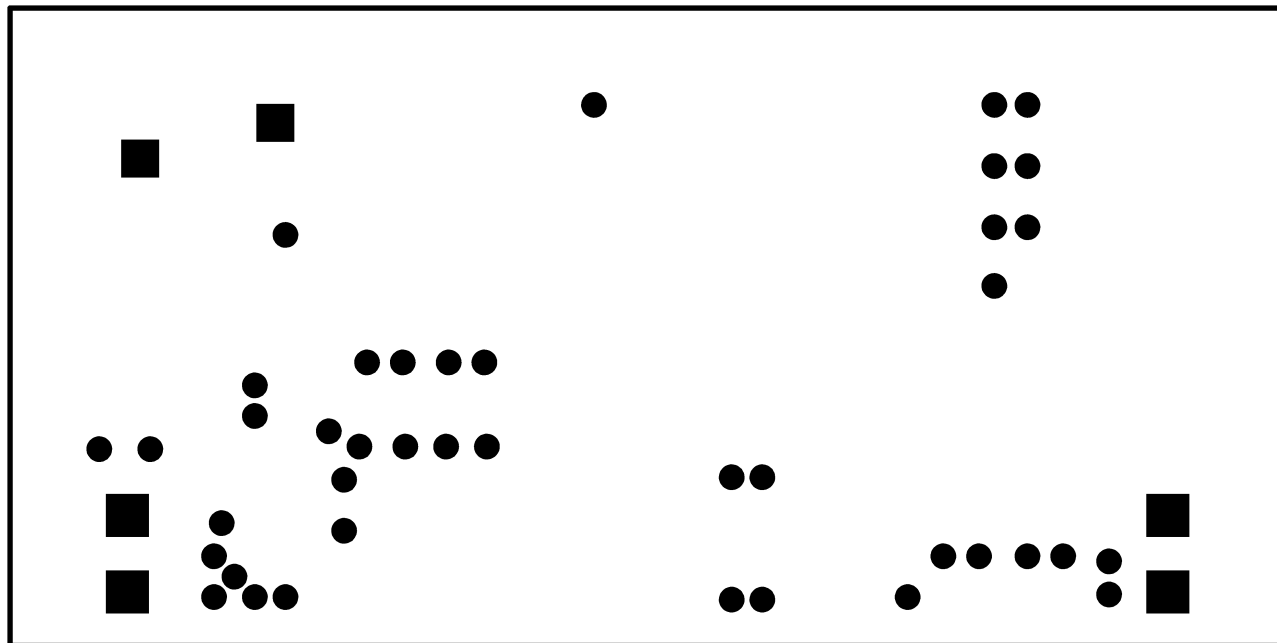

BOTTOM SOLDERMASK

The schematic diagram illustrates a power supply circuit with the following components and connections:

- Input Section:** J1 (30-75V IN) provides the input voltage V+. Input capacitors C1 (2.2 μ F) and C2 (2.2 μ F) are connected to ground. A voltage divider consisting of R2 (61.9k) and R3 (2.87k) is connected to the input, with R4 (1.00k) connected to ground. A sync input (SYNC) is connected to the COMP pin of the LM5020 via C8 (100 pF) and R5 (15.0k). R6 (12.4k) is connected to ground, and C7 (3300 pF) is connected to the input.
- Control Section:** The LM5020 controller is configured with V_{IN} at pin 1, V_{CC} at pin 4, UVLO at pin 7, OUT at pin 5, COMP at pin 3, RT at pin 9, SS at pin 10, CS at pin 8, V_{FB} at pin 2, and GND at pin 6. Feedback capacitors C4 (0.1 μ F) and C10 (4.7 μ F) are connected to ground. A resistor R1 (10) is connected to the input, and R7 (100) is connected to the CS pin. C11 (1000 pF) is connected to ground.
- Power Stage:** The MOSFET Q1 (Si7898DP) is driven by the OUT pin of the LM5020. Its gate is connected to the OUT pin, and its source is connected to ground. The drain is connected to the primary of the transformer T1. A diode D1 (CMPD2838E) is connected between the drain and the primary. A resistor R8 (0.47) is connected to ground, and R9 (0.47) is connected to the drain. A capacitor C5 (0.01 μ F) is connected to ground.
- Output Section:** The secondary of the transformer T1 is connected to a full-bridge rectifier consisting of diodes D2 and D3 (MBRD835L). The output is filtered by capacitor C12 (470 pF) and a network of capacitors C13 (100 μ F), C14 (100 μ F), and C15 (270 μ F) connected to ground. The output voltage is +3.3V, and the output current is OUT RTN. A resistor R11 (2.43k) is connected to ground, and R12 (1.47k) is connected to the output.

10 AN-1314 LM5020 Evaluation Board

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com