

AN34

Using the TC232

Author: Gary Grandbois and Wes Freeman,

Microchip Technology, Inc.

INTRODUCTION

The TC232 RS232 dual transmitter/receiver IC is specifically designed for computer and telecommunication applications in implementing the RS232 interface protocol. It operates from a single 5V supply and requires a minimum number of external components.

This application note will show how designers using the TC232 can reduce external parts count over similar 232 ICs currently on the market, and that Microchip Technology's improved processing techniques eliminate the worry of CMOS latch-up.

Basic Operation

The heart of the TC232 is the two voltage converters that allow the device to have an output swing of $\pm 10 \rm V$ while being fed from a single 5V supply. 5V is fed into pin 16, then doubled to create 10V by switched capacitor techniques (See TC962 datasheet for further information on switched capacitor charge pumps). This uses the capacitor placed between pins 1 and 3 as the switched capacitor.

The output of pin 2 is fed to a switched capacitor voltage inverter which utilizes the capacitor between pins 4 and 5 of the TC232 as its switched capacitor. The output of the inverter is filtered by a capacitor from pin 6 to ground.

Powering Other External Circuits

The convenience of having $a\pm10V$ power supply "for free" is almost too good to pass up, and designers are often tempted to use the TC232's on chip voltage converter to power more than just the 232's drivers and receivers. Succumbing to this temptation can lead to start-up problems if the additional load imposed is too great.

The structure of the TC232's DC-to-DC converter is such that with a sufficiently heavy load on the 10V output it is possible to reduce internal supply voltages to below the point where start up can begin. The graph in Figure 2 shows startup voltage vs. external load current to achieve start up for a typical TC232. For proper operation it is recommended that the combined currents taken from the outputs of the doubler (+10V) and inverter (–10V) be no greater than 6mA. If currents totalling more than 6mA are required, then ICs such as the TC962 or TC4429 should be considered for the job.

Placement of C3

A question often asked is whether C3 should be connected

between pin 2 and the 5V supply or between pin 2 and ground, as depicted in Figure 1A. For the TC232 it makes no difference. However, this is not the case for all 232 ICs.

While the best connection for C3 is to ground, users of the first 232 ICs on the market discovered that start-up problems would occur under certain conditions. Investigation showed that if the 5V power supply came "on" abruptly, the voltage converter would stall or latch up. By boot strapping the 10V output to the 5V supply rail this problem could be avoided and subsequent data sheets and application notes showed C3 connected in this manner. The drawback to this configuration is the transference of system noise from the 5V supply to the 10V output through C3.

Microchip Technology has taken special care to avoid this problem, in both the circuit's design and processing used to produce the TC232. The result is a device which is very resistant to latch-up and operates quite well in either configuration.

Deleting the 10V Filtering Capacitor

A unique feature of the TC232's voltage converter is its ability to operate with only three capacitors, instead of the usual four. In those applications where the TC232 power supply outputs (10V) are not required to supply external circuits it is possible to eliminate the 10V filter capacitor, on pin 2, and still obtain satisfactory performance for most 232 interfaces.

Figures 3 through 8 show performance comparisons of the TC232 with and without the filtering capacitor for various load conditions. Notice that while removing the filtering capacitor on pin 2 increases the 10V output's ripple, it does not effect the data outputs enough to cause noise problems for most 232 applications.

In applications where the 10V is used for other external circuits the decoupling capacitor for the circuit can be combined so that it is still not necessary to have a capacitor specifically for the 10V output.

Latch-Up Proof Design

One of the advantages of the TC232 over other CMOS 232 interface ICs is its immunity to CMOS latch-up. This prevents "mysterious" failures of the interface ICs due to transient currents flowing between the two different grounds of the two systems that the ICs are interfacing.

The latch-up ability also allows "hot switching" that is, the ability to change a board in a system without having to shut down the system. Most CMOS ICs will latch-up if this is done resulting in the destruction of the devices and/or the inability of the system to operate.

For further information on latch-up see Application Note 31.

AN34

CONCLUSION

It is possible to eliminate one additional capacitor in many designs when using the TC232. This can help save parts cost as well as board space.

Microchip Technology's processing eliminates the designer's worry about latch-up, resulting in improved system operation and reliability.

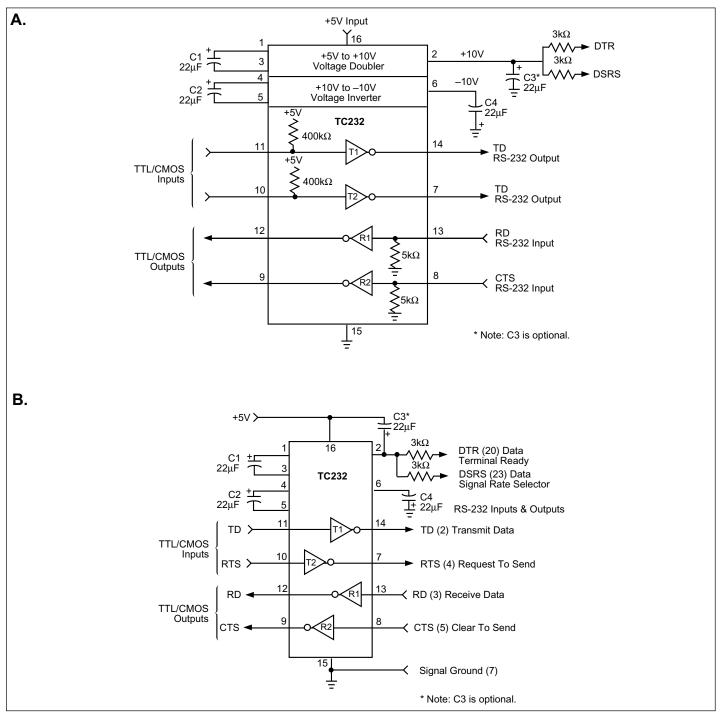


FIGURE 1: Typical application.

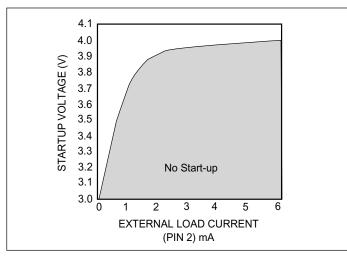


FIGURE 2: Startup voltage vs. external (pin 2) load.

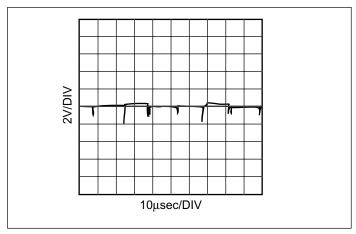


FIGURE 6: RS232 output high, no C3, $R_L = 3k\Omega$.

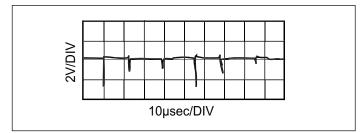


FIGURE 3: 10V output ripple, no C3, no load.

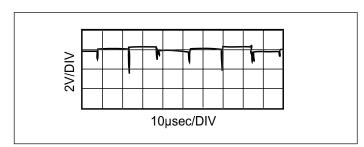


FIGURE 4: 10V output ripple, no C3, $I_{LOAD} = 6mA$.

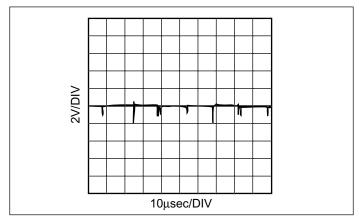


FIGURE 5: RS232 output high, C3 = $10\mu F$, $R_L = 3k\Omega$.

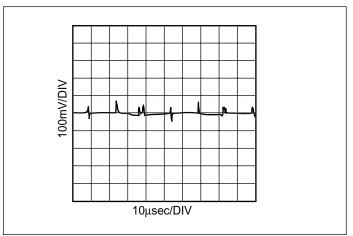


FIGURE 7: RS232 output low, C3 = $10\mu F$, $R_L = 3k\Omega$.

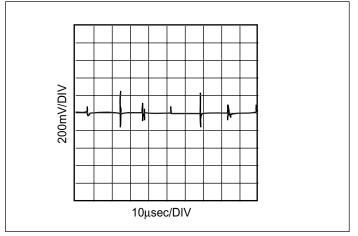


FIGURE 8: RS232 output low, no C3, $R_L = 3k\Omega$.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks


The Microchip name and logo, the Microchip logo, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, KEELOQ, SEEVAL, MPLAB and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Total Endurance, ICSP, In-Circuit Serial Programming, Filter-Lab, MXDEV, microID, *Flex*ROM, *fuzzy*LAB, MPASM, MPLINK, MPLIB, PICC, PICDEM, PICDEM.net, ICEPIC, Migratable Memory, FanSense, ECONOMONITOR, Select Mode and microPort are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Term Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

 © 2001, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.





Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEEL.OQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200 Fax: 480-792-7277 Technical Support: 480-792-7627 Web Address: http://www.microchip.com

Rocky Mountain

2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B Atlanta, GA 30350 Tel: 770-640-0034 Fax: 770-640-0307

Austin - Analog

13740 North Highway 183 Building J, Suite 4 Austin, TX 78750

Tel: 512-257-3370 Fax: 512-257-8526

Boston

2 Lan Drive, Suite 120 Westford, MA 01886 Tel: 978-692-3848 Fax: 978-692-3821

Boston - Analog

Unit A-8-1 Millbrook Tarry Condominium 97 Lowell Road Concord, MA 01742 Tel: 978-371-6400 Fax: 978-371-0050

Chicago

333 Pierce Road, Suite 180

Itasca, IL 60143 Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160 Addison, TX 75001 Tel: 972-818-7423 Fax: 972-818-2924

Dayton

Two Prestige Place, Suite 130 Miamisburg, OH 45342 Tel: 937-291-1654 Fax: 937-291-9175

Detroit

Tri-Atria Office Building 32255 Northwestern Highway, Suite 190 Farmington Hills, MI 48334 Tel: 248-538-2250 Fax: 248-538-2260

Los Angeles

18201 Von Karman, Suite 1090 Irvine, CA 92612

Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202 Hauppauge, NY 11788 Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc. 2107 North First Street, Suite 590 San Jose, CA 95131 Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108 Mississauga, Ontario L4V 1X5, Canada Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd Suite 22, 41 Rawson Street Epping 2121, NSW Australia

Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai) Co., Ltd., Beijing Liaison Office

Bei Hai Wan Tai Bldg. No. 6 Chaoyangmen Beidajie Beijing, 100027, No. China Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai) Co., Ltd., Chengdu Liaison Office

Rm. 2401, 24th Floor, Ming Xing Financial Tower No. 88 TIDU Street

Chengdu 610016, China Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai) Co., Ltd., Fuzhou Liaison Office Rm. 531, North Building Fujian Foreign Trade Center Hotel 73 Wusi Road

Fuzhou 350001, China

Tel: 86-591-7557563 Fax: 86-591-7557572

China - Shanghai

Microchip Technology Consulting (Shanghai) Co., Ltd.

Room 701, Bldg. B Far East International Plaza No. 317 Xian Xia Road Shanghai, 200051

Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai) Co., Ltd., Shenzhen Liaison Office Rm. 1315, 13/F, Shenzhen Kerry Centre, Renminnan Lu Shenzhen 518001, China

Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd. Unit 901-6, Tower 2, Metroplaza 223 Hing Fong Road Kwai Fong, N.T., Hong Kong Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc. India Liaison Office Divyasree Chambers 1 Floor, Wing A (A3/A4) No. 11, O'Shaugnessey Road Bangalore, 560 025, India Tel: 91-80-2290061 Fax: 91-80-2290062 Japan

Microchip Technology Japan K.K. Benex S-1 6F 3-18-20, Shinyokohama Kohoku-Ku, Yokohama-shi Kanagawa, 222-0033, Japan

Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea 168-1, Youngbo Bldg. 3 Floor Samsung-Dong, Kangnam-Ku Seoul, Korea 135-882

Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd. 200 Middle Road

#07-02 Prime Centre

Singapore, 188980 Tel: 65-334-8870 Fax: 65-334-8850

Taiwan

Microchip Technology Taiwan 11F-3, No. 207 Tung Hua North Road Taipei, 105, Taiwan

Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Denmark ApS Regus Business Centre Lautrup hoj 1-3 Ballerup DK-2750 Denmark Tel: 45 4420 9895 Fax: 45 4420 9910

France

Arizona Microchip Technology SARL Parc d'Activite du Moulin de Massy 43 Rue du Saule Trapu Batiment A - Ier Etage 91300 Massy, France Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Arizona Microchip Technology GmbH Gustav-Heinemann Ring 125 D-81739 Munich, Germany Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Germany - Analog

Lochhamer Strasse 13 D-82152 Martinsried, Germany Tel: 49-89-895650-0 Fax: 49-89-895650-22

Arizona Microchip Technology SRL Centro Direzionale Colleoni Palazzo Taurus 1 V. Le Colleoni 1 20041 Agrate Brianza

Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd. 505 Eskdale Road Winnersh Triangle Wokingham Berkshire, England RG41 5TU

Tel: 44 118 921 5869 Fax: 44-118 921-5820

08/01/01