

VDSL2 Line Side Protection

ITU-T Solution

Solution Products



TBU-CA050-500-WH



2031-15T-SM-RPLF

Design Kit



PN-DESIGNKIT-18

Objective

VDSL2 provides high-speed data rates of up to 30 MHz over twisted pair copper cable. The solution protects these ports against surge and power contact threats.

Solution

1 TBU® High-Speed Protector:

TBU-CA050-500-WH

1 GDT: 2031-15T-SM-RPLF

Compliance

ITU-T Basic K.20, K.21, K.45

ITU-T Enhanced K.20, K.21, K.45

(with properly selected transformer and capacitors)


Alternate Recommendations

Other PortNote® Solutions:

• VDSL Driver Side Protection - ITU-T Solution
Variations of this circuit are available depending on specific design constraints; contact your local Bourns technical representative for more information.

Benefit

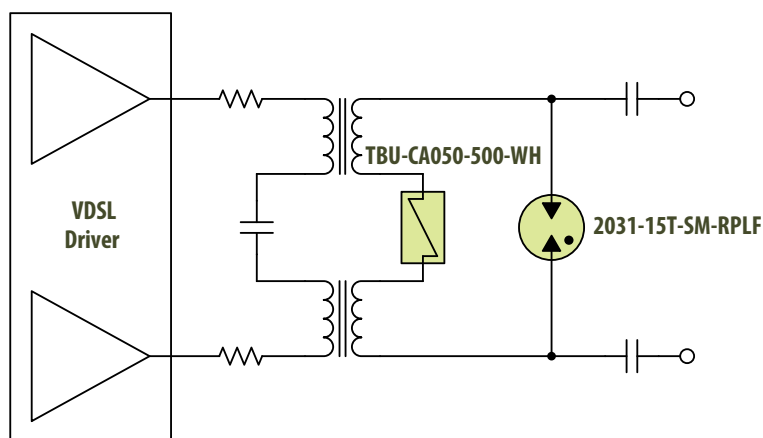This solution provides protection on the line (input) side of the circuit without impairing the VDSL 30 MHz signal.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

BOURNS®

Americas: Tel +1-951 781-5500
Fax +1-951 781-5700

Europe: Tel +41-(0)41 768 55 55
Fax +41-(0)41 768 55 10

Asia-Pacific: Tel +886-2 256 241 17
Fax +886-2 256 241 16

Bourns® PortNote® solutions provide protection recommendations for typical port threats.

For more information, go to:

www.bourns.com

or email: protection@bourns.com