

AN-1962 LM5032 Interleaved Boost Evaluation Board

The LM5032 dual current mode PWM controller contains all the features needed to control an interleaved boost converter. The two outputs operate 180 degrees out of phase and have separate current limit inputs for each channel. In addition to a high input voltage range, the controller contains all the auxiliary features needed to control a complete converter.

1 Introduction

A basic boost converter converts a DC voltage to a higher DC voltage. Interleaving adds additional benefits such as reduced ripple currents in both the input and output circuits. Higher efficiency is realized by splitting the output current into two paths, substantially reducing I^2R losses and inductor AC losses. [Figure 1](#) shows the basic interleaved boost topology.

When Q1 turns on, current ramps up in L1 with a slope depending on the input voltage, storing energy in L1. D1 is off during this time since the output voltage is greater than the input voltage. Once Q1 turns off, D1 conducts delivering part of its stored energy to the load and the output capacitor. Current in L1 ramps down with a slope dependent on the difference between the input and output voltage. One half of a switching period later, Q2 also turns on completing the same cycle of events. Since both power channels are combined at the output capacitor, the effective ripple frequency is twice that of a conventional single channel boost regulator.

 


Figure 1. Interleaved Boost Basic Diagram

2 Modes of Operation

The mode of operation can be analyzed based on one channel. Since both power channels share current and because both inductors are identical, each power channel behaves identically. Based on the amount of energy that is delivered to the load during each switching period, the boost converter can be classified into continuous or discontinuous conduction mode. If all the energy stored in the inductor is delivered to the load during each switching cycle, the mode of operation is classified as discontinuous conduction mode (DCM). In this mode the inductor current ramps down to zero during the switch off-time. If only part of the energy is delivered to the load, then the converter is said to be operating in continuous conduction mode (CCM). Figure 2 shows the inductor current waveforms for both modes of operation.

The mode of operation is a fundamental factor in determining the electrical characteristics of the converter. The characteristics vary significantly from one mode to the other.

 


Figure 2. Inductor Current (I_L) Waveforms

3 Continuous Versus Discontinuous Mode

Both modes of operation have advantages and disadvantages. The main disadvantages in using CCM is the inherent stability problems caused by the right-half-plane zero in the transfer function. However, the switch and output diode peak currents are larger when the converter is operating in the DCM mode. Larger peak currents necessitate using larger current and power dissipation rated switches and diodes. Also, the larger peak currents cause greater EMI/RFI problems. Most modern designs use CCM because higher power densities are possible. For these reasons, this design is based on continuous conduction mode.

4 Selection of Boost Power Stage Components

The interleaved boost converter design involves the selection of the inductors, the input and output capacitors, the power switches and the output diodes. Both the inductors and diodes should be identical in both channels of an interleaved design. In order to select these components, it is necessary to know the duty cycle range and peak currents. Since the output power is channeled through two power paths, a good starting point is to design the power path components using half the output power. Basically, the design starts with a single boost converter operating at half the power. However, a trade-off exists which will depend on the goals of the design. The designer may use smaller components since currents are smaller in each phase. Or, larger components may be selected to minimize losses. Specifically, this design uses the criteria of room temperature operation over the entire input voltage range without the requirement of airflow. Obviously, there are many trade-offs possible, such as requiring external airflow which would allow the use of smaller components and more power per watt.

Knowing the maximum and minimum input voltages, the output voltage, and the voltage drops across the output diode and switch, the maximum and minimum duty cycles are calculated. Next, the average inductor current can be estimated from the load current and duty cycle. Assuming the peak to peak inductor current ripple to be a certain percentage of the average inductor current, the peak inductor current can be estimated. The inductor value is then calculated using the ripple current, switching frequency, input voltage, and duty cycle information. Finally, the boundary between CCM and DCM is determined which will determine the minimum load current.

Once the inductor value has been chosen and the peak currents have been calculated, the other components may be selected. Selection of the input and output capacitors differ from a single phase design because of the reduced ripple and increased effective frequency.

5 Inductor Selection

$$D_{\max} = \frac{V_{\text{OUT}} + V_d - V_{\text{IN(MIN)}}}{V_{\text{OUT}} + V_d - V_{\text{(ON)}}} \quad (1)$$

$$D_{\min} = \frac{V_{\text{OUT}} + V_d - V_{\text{IN(MAX)}}}{V_{\text{OUT}} + V_d - V_{\text{(ON)}}} \quad (2)$$

Where V_{OUT} is the output voltage, V_d is the forward voltage drop of the output diode, and $V_{\text{(ON)}}$ is the on stage voltage of the switching MOSFET. $V_{\text{IN(MAX)}}$ is the maximum input voltage, and $V_{\text{IN(MIN)}}$ is the minimum input voltage.

The average inductor current (maximum) per phase can be calculated knowing the output current, I_{OUT} , remembering that the current per phase is one-half the total current. This is the origin of the 0.5 term in the numerator below.

$$I_{\text{L(avg)}} = \frac{0.5 \times I_{\text{OUT}}}{1 - D_{\text{MAX}}} \quad (3)$$

As a starting point assume the peak inductor current ripple per phase, ΔI_L to be a certain percentage of the average inductor current calculated in equation (3). A good starting value of ΔI_L is about 40% or the output current which is 20% of the individual phase current. Inductor ripple will also determine the minimum output current for continuous mode operation, so some iteration may be necessary in choosing this parameter. The peak inductor current per phase is given by:

$$I_{\text{PEAK}} = I_{\text{L(avg)}} + \frac{\Delta I_L}{2} \quad (4)$$

Knowing the switching frequency, f_s the required inductance value per phase can be selected using:

$$L_{\text{(MIN)}} = \frac{(V_{\text{IN(MIN)}} - V_{\text{(ON)}}) \times D_{\text{MAX}}}{f_s \times \Delta I_L} \quad (5)$$

At the boundary between CCM and DCM modes of operation, the peak inductor current per phase, I_{PEAK} is the same as the peak to peak inductor current ripple per phase, ΔI_L , as shown in [Figure 2](#). Therefore, the average inductor current at the boundary is given by:

$$I_{\text{L(avg-critical)}} = \frac{\Delta I_{\text{PEAK}}}{2} \quad (6)$$

From equations (3) and (6)

$$I_{\text{PEAK}} = \frac{I_{\text{OUT}}}{1 - D_{\text{MAX}}} \quad (7)$$

The critical value of the inductance per phase to maintain the converter in continuous mode related to output current is given by equations (5) and (7).

$$L_{\text{(crit)}} = \frac{(V_{\text{IN(MIN)}} - V_{\text{(ON)}}) \times D_{\text{MAX}} \times (1 - D_{\text{MAX}})}{f_s \times I_{\text{OUT}}} \quad (8)$$

Knowing the minimum load current in a particular design L can be chosen. Obviously, there are trade-offs between minimum load current, percent ripple, and inductor size. Increasing the frequency helps in reducing inductor size.

6 Output Capacitor

In a boost converter, the output capacitor must be chosen to withstand relatively high ripple current compared to an equivalent power buck regulator. The high ripple current flows through the equivalent series resistance (ESR) of the capacitor. ESR increases the capacitor temperature and increases ripple voltage. First calculate the worst case duty cycle for ripple which is usually the maximum duty cycle (refer to [Figure 3](#) for this value). Then read the y axis value or normalized rms ripple in the output capacitor from [Figure 3](#) using the two phase graphs.

 


Figure 3. Normalized Output Capacitor Ripple Current

Then, multiply the output current by this number to get the actual RMS output capacitor ripple. Using the actual ripple, the capacitor can be selected. The capacitor must be chosen to withstand this RMS ripple current at extreme operating conditions. Frequently several capacitors in parallel can be selected. Next use equation (9) to determine the capacitance necessary to insure a given voltage ripple. In this case the ESR will be the dominate term which will determine the capacitor's value. Both conditions, RMS rating and ESR value must be met. In equation (9), f_s is double the frequency of an individual phase, since both phases are combined at the output capacitor.

$$\Delta V_{OUT} = \frac{I_{OUT(MAX)} \times (1 - D_{MIN})}{f_s \times C_{OUT}} + I_{PEAK} \times ESR \quad (9)$$

It is interesting to observe from [Figure 3](#) the reduction in RMS (and peak to peak) ripple by using a two phase converter vs. a single phase solution. At 50% duty cycle, ripple is nearly perfectly canceled, which occurs when V_{IN} is twice V_{OUT} .

7 Input Capacitor Selection

Because an inductor is in series with the input supply in a boost converter, input capacitor selection is less severe than the output capacitor. In a two-phase design, there is a further reduction in input ripple due to ripple cancellation, allowing a smaller input capacitor than in a single phase design. The input ripple can be read from the graph in [Figure 4](#). This graph is normalized according to

$$I_{RIPPLE(Normalized)} = \frac{V_{IN}}{L \times f_s} \quad (10)$$

where f_s is the switching frequency per phase.

 


Figure 4. Normalized Input Capacitor Ripple Current

This normalization keeps the y axis of the graph in reasonable limits and results in an easier to read graph. As in the output capacitor case, determine the worst case duty cycle for a given design and read the normalized ripple current from the two-phase graph. Then convert the normalized ripple current to actual ripple current by multiplying by the normalization factor. Then size the input capacitor to handle this rms ripple value.

8 Power Switches Selection

Each MOSFET should be selected based on several parameters. The drain-source breakdown should be greater than the maximum input voltage plus some margin for ringing. The $R_{DS(ON)}$ value will determine conduction losses and must low enough to keep junction temperatures within specifications at the maximum drain current condition. Gate to source and gate to drain changes will contribute to AC losses. The thermal resistance rating will determine heatsink and airflow requirements. A more detailed calculation for the power dissipated in each MOSFET is given by:

$$P_{MOSFET} = \left(\frac{I_{OUT(MAX)}}{2 \times (1 - D)} \right) \times R_{DS(ON)} \times D \times 1.3 + V_{IN(MAX)} \times Q_g \times f_s + \frac{0.5 \times V_{IN(MAX)} \times I_{OUT} \times f_s \times (t_g + t_f)}{(1 - D)} \quad (11)$$

The first term is the I^2R term. The $1-D$ term in the denominator relates the output current to inductor current. The 2 in the denominator is necessary to get current per phase. The second term is the AC gate charge loss term which depends on phase frequency and the third term represents conduction switching loss.

9 Output Diode Selection

The output diode selection is based on voltage and current ratings, and reverse recovery time. The voltage rating should be V_{OUT} plus some margin for ringing. V_F should be as low as possible at the maximum output current specification to minimize conduction losses. Reverse recovery time t_{rr} should be as low as possible to minimize switching losses. Chose a Schottky rectifier if voltage ratings permit, otherwise an ultra-fast rectifier is required.

10 Compensation Components Selection

Compensation is similar to an equivalent power single phase boost regulator with the same inductor value. There is a right-half-plane zero in the continuous conduction mode which will influence loop bandwidth. A conservative approach is to insure the loop gain crosses zero at lower than $\frac{1}{4}$ the switching (per phase) frequency. The frequency of the right-half-plane zero is given by:

$$f_{RHPZ} = \frac{R_{LOAD} \times (1 - D)^2}{2 \times \pi \times L} = \frac{R_{LOAD} \times V_{IN}^2}{2 \times \pi \times L \times V_{OUT}^2} \quad (12)$$

11 Evaluation Board

A prototype was constructed using the LM5032 as the controller. The design goal was an interleaved converter with high efficiency and operation at full power without air or a heatsink at room temperature environment. Power was designed around a limit of about 14 amps of input current, allowing the use of off the shelf surface mount inductors. Specifically, the specifications are:

$$V_{IN} = 18 \text{ to } 45 \text{ volts}$$

$$V_{OUT} = 48 \text{ volts}$$

$$I_{OUT} = 4.0 \text{ amps}$$

$$V_{RIPPLE-OUT} < 50 \text{ mV}$$

Refer to Figure 5 for a complete schematic of the evaluation board.

The circuit is built around the LM5032, a 2 phase PWM controller with separate inputs for current limit and compensation for each channel. The separate inputs for the PWM comparator are combined in this design since we are implementing a two-phase, single output converter, not two independent converters. The two current limit inputs are used, since this insures current balance in each phase. Each output phase drives its own power channel consisting of switching FETs Q1 and Q2, Inductors L2 and L3, and output dual diode D2. The two power outputs are combined at the output capacitors C15-C20. The IC is internally configured to drive its two outputs 180 degrees out of phase.

 


Figure 5. Schematic of Evaluation Board

A single feedback network consisting of error amplifier U4 and associated passive components drives both comp inputs which are tied together at the IC.

In order to reduce the sense resistor losses, a DC offset circuit was constructed to offset the current sense inputs by 185 mV. This allowed the use of lower value sense resistors in each phase, reducing I^2R losses. The circuit of [Figure 6](#) illustrates the DC offset circuit.

 


Figure 6. Current Sense DC Offset Circuit

Since U3 is already in use as the error amplifier reference, the circuit only adds a few low current resistors. Resistors R23, R10, and the current sense resistors form a voltage divider from the 2 volt reference. With the values from [Figure 1](#), the DC offset is 0.185 volts, effectively reducing the current limit threshold of 0.5 volts by that amount. As long as R23 is much larger than R10 and with R10 much larger than the sense resistors, the DC offset will not adversely interact with the actual sensed current waveform. More offset could be used, consistent with compressing the actual current signal vs. noise.

In order to further reduce losses, a switching bias supply was constructed with adjustable controller U2, an LM5009. As can be seen from the photograph of the actual prototype in [Figure 7](#), this circuit is very small and offers a good solution for a bias supply. If a linear regulator or zener diode were used, it would be necessary to drop about 31 volts from the input supply at $V_{in(max)}$. With an overhead current of 500 mA, a loss of about 16 watts was avoided. Diode D3 prevents the error amplifier from holding the comp pin of U1 high during startup, converting the error amplifier to a sink only configuration. The LM5032 contains an internal 5K pull-up resistor.


 



Figure 7. Photographs of the Evaluation Board

Referring to the left photograph in [Figure 7](#), the two power inductors occupy the top part of the left photograph, with rectification accomplished with the common cathode Schottky diode located just below the inductors. The LM5032 PWM controller is located in the lower left portion of the board. On the bottom side of the board the bias supply is located near the upper right, with the two switching FETs at center right. The error amplifier is located near the top left of the board. No heat-sinking other than the copper in the PCB is used. A four layer board was used for compactness of design and heat dissipation properties.

 


TOP (.CMP) LAYER AS VIEWED FROM TOP
880600338-001 rev A

Figure 8. Top Layer

 


TOP SILKSCREEN (.PLC) LAYER AS VIEWED FROM TOP
880600338-001 rev A

Figure 9. Top Silk Layer

 

BOTTOM SILKSCREEN (.BPL) LAYER AS VIEWED FROM TOP
880600338-001 rev A

Figure 10. Bottom Silk Layer

 

BOTTOM (.SOL) LAYER AS VIEWED FROM TOP
880600338-001 rev A

Figure 11. Bottom Layer



 


Figure 12. Fab Drawing

 

LAYER 2 (.LY2) AS VIEWED FROM TOP
880600338-001 rev A

Figure 13. Layer 2

 

LAYER 3 (.LY3) AS VIEWED FROM TOP
880600338-001 rev A

Figure 14. Layer 3

12 Performance

 


Figure 15. Efficiency

 


Figure 16. Output Ripple

Referring to the plots in [Figure 15](#) taken at the DCM/CM boundary, efficiencies range from 95% to 98% up to the full 4 amps of output current, and over a 3.5:1 input voltage range. The very low current region where overhead bias currents dominate does have less efficiency, but this is true of all regulators. These plots illustrate the possibility of building a compact, high power boost converter without sacrificing excellent efficiency. Although the evaluation will function down to 12V V_{in} , it is specified from $V_{in} = 18 - 48V$.

Input and output ripple reduction are some of the benefits of an interleaved converter. Since the output ripple is double the frequency of the individual phases and at a lower RMS current value, the designer has the choice of smaller output capacitors with the same ripple as a single phase converter, or using larger capacitors to achieve even lower output ripple. Effective ripple is a function of duty cycle. [Figure 3](#) and [Figure 4](#) illustrates the input and output ripple currents vs. duty cycle relationships. [Figure 16](#) shows the output ripple of the prototype which is less than the 50mV target. Since ripple reduction is a function of duty cycle, the degree of ripple overlap is also a function of duty cycle. There is near perfect cancellation of ripple at 50% duty cycle. This opens the intriguing possibility of building a converter with little to no output ripple if the designer can limit V_{in} to the proper value for 50% duty cycle. In the more general case, ripple is reduced by as much as 50% compared to an equivalent power single phase converter. Likewise, inductor selection is flexible with the two phase design. One-half the single phase inductor value can be chosen, which will make each inductor smaller, but results in the same ripple currents as the single phase design. Or the inductors can remain the same value as in the single phase design, reducing the ripple by one-half. The proper trade-offs will depend on the overall design goal. Attention to ESR requirements will keep capacitors within temperature ratings and the output voltage ripple within specifications.

13 Bill of Materials

Table 1. Bill of Materials

Qty	Reference	Value	Description	Part Number	Manufacturer
7	C1, C2, C3, C4, C17, C18, C19	2.2 uF	CAP, CER, 2.2uF, 50V, X7R, 10%, 1210	C3225X7R1H225K	TDK
3	C11, C13, C14	100 pF	CAP, CER, 100pF, 50V, COG, 5%, 0805	C2012COG1H101J	TDK
2	C15, C16	150 uF	CAP, ELEC, 150uF, 63V, FK, SMD	EEV-FK1J151Q	PANASONIC
1	C20	0.1 uF	CAP, CER, 0.1uF, 100V, X7R, 10%, 1206	C3216X7R2A104K	TDK
1	C24	470 pF	CAP, CER, 470pF, 50V, COG, 5%, 0805	GRM2165C1H471JA01D	MURATA
8	C5, C6, C10, C12, C21, C22, C23, C25	0.1 uF	CAP, CER, 0.1uF, 100V, X7R, 10%, 0805	C2012X7R2A104K	TDK
2	C7, C8	0.01 uF	CAP, CER, .01uF, 50V, X7R, 10%, 0805	08055C103KAT2A	AVX
1	C9	22 uF	CAP, CER, 22uF, 10V, X7R, 10%, 1210	GRM32ER71A226KE20L	MURATA
1	D1	ZHCS506TA	DIODE, SCHOTTKY, 60V, 0.5A, SOT-23	ZHCS506TA	ZETEX
1	D2	MBRB1560	DIODE, SCHOTTKY, 60V, 15A, CC, D2PAK	MBRB1560CT/31	VISHAY
1	D4	CMDD4448	DIODE, HS SWITCHING, SOD-323	CMDD4448	CENTRAL SEMI
4	J1, J2, J3, J4	I/O	TERM, SCREW, VERT, SNAP IN	7693	KEYSTONE
3	J5, J6, J7	TP	TEST POINT, PC, WHT	5012	KEYSTONE
1	L1	330 uH	INDUCTOR, 330uH, Pb FREE	SDR0503-331KL	BOURNS
2	L2, L3	15 uH	INDUCTOR, 15uH, 2.3mOHM, 28A	SER2807H-153KL	COILCRAFT
2	Q1, Q2	SUD50N06-9L	N-CHANNEL MOSFET, 60V, 50A, DPAK	SUD50N06-09L-E3	VISHAY
1	R1	160k	RES, 160K, 1/8W, 1%, 0805, SMD	CRCW0805160KFKEA	VISHAY
2	R12, R13	0.02	RES .02 OHM 2W 1% 0830 SMD	RL7520WT-R020-F	SUSUMU
1	R2	110k	RES, 110K, 1/8W, 1%, 0805, SMD	CRCW0805110KFKEA	VISHAY
2	R23, R24	10.0k	RES 10.0K OHM 1/8W 1% 0805 SMD	CRCW080510K0FKEA	VISHAY
1	R25	4.75k	RES 4.75K OHM 1/8W 1% 0805 SMD	CRCW08054K75FKEA	VISHAY
1	R26	30.1k	RES 30.1K OHM 1/8W 1% 0805 SMD	CRCW080530K1FKEA	VISHAY
1	R27	10	RES 10.0 OHM 1/8W 1% 0805 SMD	CRCW080510R0FKEA	VISHAY
1	R28	24.9k	RES 24.9K OHM 1/8W 1% 0805 SMD	CRCW080524K9FKEA	VISHAY
1	R29	1.10k	RES ANTI-SULFUR 1.1K OHM 1% 0805	ERJ-S06F1101V	PANASONIC
1	R3	22.1k	RES 22.1K OHM 1/8W 1% 0805 SMD	CRCW080522K1FKEA	VISHAY
1	R4	7.32k	RES 7.32K OHM 1/8W 1% 0805 SMD	CRCW08057K32FKEA	VISHAY
1	R5	4.02	RES 4.02K OHM 1/8W 1% 0805 SMD	CRCW08054K02FKEA	VISHAY
1	R6	17.4k	RES 17.4K OHM 1/8W 1% 0805 SMD	CRCW080517K4FKEA	VISHAY
3	R7, R10, R11	1.00k	RES 1.00K OHM 1/8W 1% 0805 SMD	CRCW08051K00FKEA	VISHAY
2	R8, R22	2.00k	RES 2.00K OHM 1/8W 1% 0805 SMD	CRCW08052K00FKEA	VISHAY
2	R9, R30	69.8k	RES 69.8K OHM 1/8W 1% 0805 SMD	CRCW080569K8FKEA	VISHAY
1	U1	LM5032	DUAL INTERLEAVED CM CONTROLLER	LM5032	Texas Instruments
1	U2	LM5009	100V STEP DOWN SW REGULATOR	LM5009	Texas Instruments
1	U3	LM4040	MICROPOWER SHUNT REFERENCE	LM4040	Texas Instruments

Table 1. Bill of Materials (continued)

Qty	Reference	Value	Description	Part Number	Manufacturer
1	U4	LM8261	OP-AMP RR I/O HIGH CURRENT	LM8261	Texas Instruments

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com