

AN-1985 LM3429 Buck-Boost Evaluation Board

1 Introduction

This wide range evaluation board showcases the LM3429 NFET controller used with a buck-boost current regulator. It is designed to drive 4 to 8 LEDs at a maximum average LED current of 1A from a DC input voltage of 10 to 70V.

The evaluation board showcases most features of the LM3429 including PWM dimming, overvoltage protection and input under-voltage lockout. It also has a right angle connector (J7) which can mate with an external LED load board allowing for the LEDs to be mounted close to the driver. Alternatively, the LED+ and LED- banana jacks can be used to connect the LED load.

The buck-boost circuit can be easily redesigned for different specifications by changing only a few components (see [Alternate Designs](#)). Note that design modifications can change the system efficiency for better or worse. See the *LM3429 LM3429Q1 N-Channel Controller for Constant Current LED Drivers* ([SNVS616](#)) data sheet for a comprehensive explanation of the device and application information.

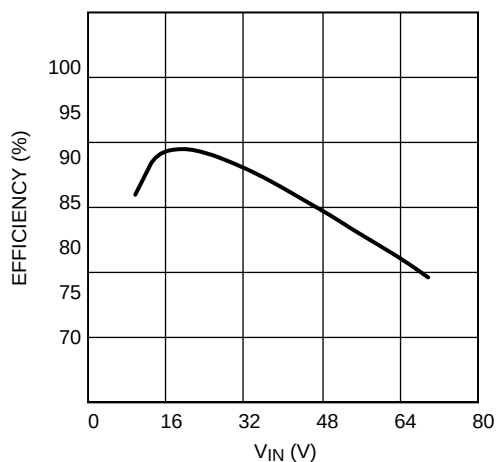


Figure 1. Efficiency with 6 Series LEDs AT 1A

2 Schematic

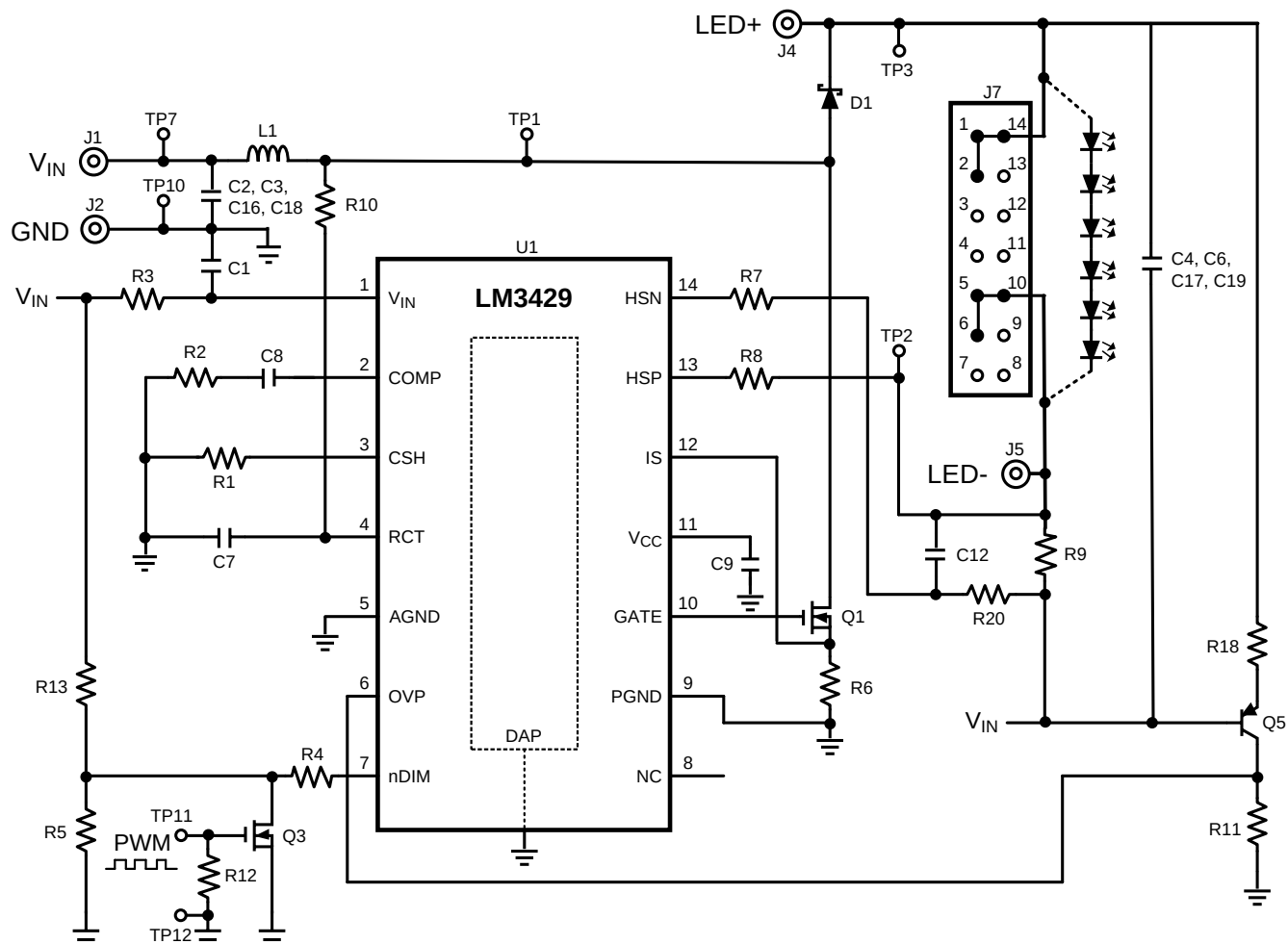


Figure 2. Board Schematic

3 Pin Descriptions

Pin	Name	Description	Application Information
1	V _{IN}	Input Voltage	Bypass with 100 nF capacitor to AGND as close to the device as possible in the circuit board layout.
2	COMP	Compensation	Connect a capacitor to AGND.
3	CSH	Current Sense High	Connect a resistor to AGND to set the signal current. For analog dimming, connect a controlled current source or a potentiometer to AGND as detailed in the <i>Analog Dimming</i> section.
4	RCT	Resistor Capacitor Timing	Connect a resistor from the switch node and a capacitor to AGND to set the switching frequency.
5	AGND	Analog Ground	Connect to PGND through the DAP copper circuit board pad to provide proper ground return for CSH, COMP, and RCT.
6	OVP	Over-Voltage Protection	Connect to a resistor divider from V _O to program output over-voltage lockout (OVLO). Turn-off threshold is 1.24V and hysteresis for turn-on is provided by 20 μ A current source.
7	nDIM	Not DIM input	Connect a PWM signal for dimming as detailed in the <i>PWM Dimming</i> section and/or a resistor divider from V _{IN} to program input under-voltage lockout (UVLO). Turn-on threshold is 1.24V and hysteresis for turn-off is provided by 20 μ A current source.
8	NC	No Connection	Leave open.
9	PGND	Power Ground	Connect to AGND through the DAP copper circuit board pad to provide proper ground return for GATE.
10	GATE	Gate Drive Output	Connect to the gate of the external NFET.
11	V _{CC}	Internal Regulator Output	Bypass with a 2.2 μ F–3.3 μ F, ceramic capacitor to PGND.
12	IS	Main Switch Current Sense	Connect to the drain of the main N-channel MosFET switch for R _{DS-ON} sensing or to a sense resistor installed in the source of the same device.
13	HSP	High-Side LED Current Sense Positive	Connect through a series resistor to the positive side of the LED current sense resistor.
14	HSN	High-Side LED Current Sense Negative	Connect through a series resistor to the negative side of the LED current sense resistor.
DAP (15)	DAP	Thermal pad on bottom of IC	Star ground, connecting AGND and PGND.

4 Bill of Materials

Qty	Part ID	Part Value	Manufacturer	Part Number
2	C1, C4	0.1 μ F X7R 10% 100V	TDK	C2012X7R2A104K
4	C2, C3, C16, C18	4.7 μ F X7R 10% 100V	MURATA	GRM55ER72A475KA01L
3	C6, C17, C19	2.2 μ F X7R 10% 100V	TDK	C4532X7R2A225K
1	C7	1000 pF COG/NPO 5% 50V	MURATA	GRM2165C1H102JA01D
1	C8	1 μ F X7R 10% 16V	MURATA	GRM21BR71C105KA01L
1	C9	2.2 μ F X7R 10% 16V	MURATA	GRM21BR71C225KA12L
1	C12	0.1 μ F X7R 10% 25V	MURATA	GRM21BR71E104KA01L
1	D1	Schottky 100V 12A	VISHAY	12CWQ10FNPBF
4	J1, J2, J4, J5	banana jack	KEYSTONE	575-8
1	J7	2 x 7 shrouded header	SAMTEC	TSSH-107-01-SDRA
1	L1	33 μ H 20% 6.3A	COILCRAFT	MSS1278-333MLB
1	Q1	NMOS 100V 40A	VISHAY	SUD40N10-25
1	Q3	NMOS 60V 260 mA	ON-SEMI	2N7002ET1G
1	Q5	PNP 150V 600 mA	FAIRCHILD	MMBT5401
1	R1	12.4 k Ω 1%	VISHAY	CRCW080512k4FKEA
1	R2	0 Ω 1%	VISHAY	CRCW08050000Z0EA
2	R3, R20	10 Ω 1%	VISHAY	CRCW080510R0FKEA
1	R4	16.9 k Ω 1%	VISHAY	CRCW080516k9FKEA
1	R5	1.43 k Ω 1%	VISHAY	CRCW08051k43FKEA
1	R6	0.05 Ω 1% 1W	VISHAY	WSL2512R0500FEA
2	R7, R8	1.0 k Ω 1%	VISHAY	CRCW08051k00FKEA
1	R9	0.1 Ω 1% 1W	VISHAY	WSL2512R1000FEA
1	R10	35.7 k Ω 1%	VISHAY	CRCW080535k7FKEA
1	R11	15.8 k Ω 1%	VISHAY	CRCW080515k8FKEA
2	R12, R13	10.0 k Ω 1%	VISHAY	CRCW080510k0FKEA
1	R18	750 k Ω 1%	VISHAY	CRCW0805750kFKEA
7	TP1, TP2, TP3, TP7, TP10, TP11, TP12	turret	KEYSTONE	1502-2
1	U1	Buck-boost controller	TI	LM3429

5 PCB Layout

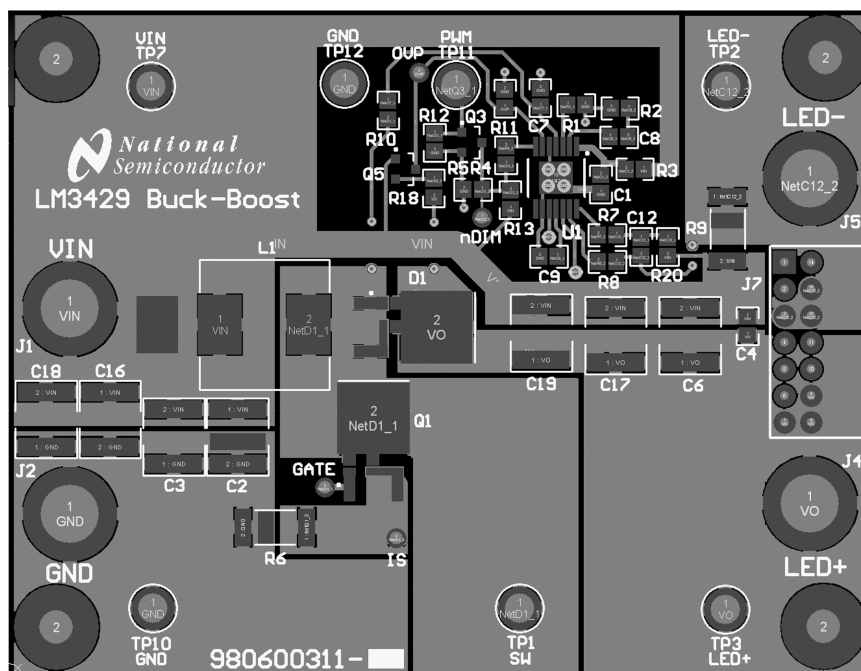


Figure 3. Top Layer

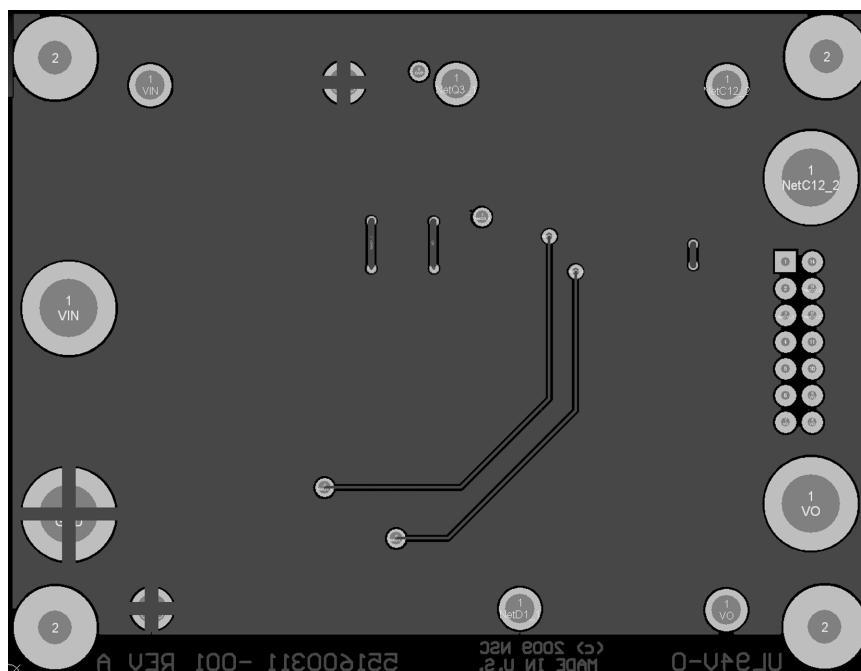


Figure 4. Bottom Layer

6 Design Procedure

Refer to the *LM3429 LM3429Q1 N-Channel Controller for Constant Current LED Drivers* ([SNVS616](#)) data sheet for design considerations.

6.1 Specifications

$$N = 6$$

$$V_{LED} = 3.5V$$

$$r_{LED} = 325 \text{ m}\Omega$$

$$V_{IN} = 24V$$

$$V_{IN-MIN} = 10V; V_{IN-MAX} = 70V$$

$$f_{SW} = 700 \text{ kHz}$$

$$V_{SNS} = 100 \text{ mV}$$

$$I_{LED} = 1A$$

$$\Delta i_{L-PP} = 500 \text{ mA}$$

$$\Delta i_{LED-PP} = 50 \text{ mA}$$

$$\Delta v_{IN-PP} = 100 \text{ mV}$$

$$I_{LIM} = 5A$$

$$V_{TURN-ON} = 10V; V_{HYS} = 3V$$

$$V_{TURN-OFF} = 60V; V_{HYSO} = 15V$$

6.2 Operating Point

Solve for V_O and r_D :

$$V_O = N \times V_{LED} = 6 \times 3.5V = 21V \quad (1)$$

$$r_D = N \times r_{LED} = 6 \times 325 \text{ m}\Omega = 1.95\Omega \quad (2)$$

Solve for D , D' , D_{MAX} , and D_{MIN} :

$$D = \frac{V_O}{V_O + V_{IN}} = \frac{21V}{21V + 24V} = 0.467 \quad (3)$$

$$D' = 1 - D = 1 - 0.467 = 0.533 \quad (4)$$

$$D_{MIN} = \frac{V_O}{V_O + V_{IN-MAX}} = \frac{21V}{21V + 70V} = 0.231 \quad (5)$$

$$D_{MAX} = \frac{V_O}{V_O + V_{IN-MIN}} = \frac{21V}{21V + 10V} = 0.677 \quad (6)$$

6.3 Switching Frequency

Assume $C7 = 1 \text{ nF}$ and solve for $R10$:

$$R10 = \frac{25}{f_{SW} \times C7} = \frac{25}{700 \text{ kHz} \times 1 \text{ nF}} = 35.7 \text{ k}\Omega \quad (7)$$

The closest standard resistor is actually $35.7 \text{ k}\Omega$ therefore the f_{SW} is:

$$f_{SW} = \frac{25}{R10 \times C7} = \frac{25}{35.7 \text{ k}\Omega \times 1 \text{ nF}} = 700 \text{ kHz} \quad (8)$$

The chosen components from step 2 are:

$$\begin{aligned} C7 &= 1 \text{ nF} \\ R10 &= 35.7 \text{ k}\Omega \end{aligned}$$

(9)

6.4 Average LED Current

Solve for R9:

$$R9 = \frac{V_{SNS}}{I_{LED}} = \frac{100 \text{ mV}}{1 \text{ A}} = 0.1 \Omega \quad (10)$$

Assume R1 = 12.4 k Ω and solve for R8:

$$R8 = \frac{I_{LED} \times R1 \times R9}{1.24 \text{ V}} = \frac{1 \text{ A} \times 12.4 \text{ k}\Omega \times 0.1 \Omega}{1.24 \text{ V}} = 1.0 \text{ k}\Omega \quad (11)$$

The closest standard resistor for R9 is 0.1 Ω and the closest for R8 (and R7) is actually 1 k Ω therefore I_{LED} is:

$$I_{LED} = \frac{1.24 \text{ V} \times R8}{R9 \times R1} = \frac{1.24 \text{ V} \times 1.0 \text{ k}\Omega}{0.1 \Omega \times 12.4 \text{ k}\Omega} = 1.0 \text{ A} \quad (12)$$

The chosen components from step 3 are:

$$\begin{aligned} R9 &= 0.1 \Omega \\ R1 &= 12.4 \text{ k}\Omega \\ R8 &= R7 = 1 \text{ k}\Omega \end{aligned}$$

(13)

6.5 Inductor Ripple Current

Solve for L1:

$$L1 = \frac{V_{IN} \times D}{\Delta I_{L-PP} \times f_{SW}} = \frac{24 \text{ V} \times 0.467}{500 \text{ mA} \times 700 \text{ kHz}} = 32 \mu\text{H} \quad (14)$$

The closest standard inductor is 33 μH therefore the actual ΔI_{L-PP} is:

$$\Delta I_{L-PP} = \frac{V_{IN} \times D}{L1 \times f_{SW}} = \frac{24 \text{ V} \times 0.467}{33 \mu\text{H} \times 700 \text{ kHz}} = 485 \text{ mA} \quad (15)$$

Determine minimum allowable RMS current rating:

$$\begin{aligned} I_{L-RMS} &= \frac{I_{LED}}{D'} \times \sqrt{1 + \frac{1}{12} \times \left(\frac{\Delta I_{L-PP} \times D'}{I_{LED}} \right)^2} \\ I_{L-RMS} &= \frac{1 \text{ A}}{0.533} \times \sqrt{1 + \frac{1}{12} \times \left(\frac{485 \text{ mA} \times 0.533}{1 \text{ A}} \right)^2} \\ I_{L-RMS} &= 1.88 \text{ A} \end{aligned} \quad (16)$$

The chosen component from step 4 is:

$$L1 = 33 \mu\text{H}$$

(17)

6.6 Output Capacitance

Solve for C_O:

$$\begin{aligned} C_O &= \frac{I_{LED} \times D}{r_D \times \Delta I_{LED-PP} \times f_{SW}} \\ C_O &= \frac{1 \text{ A} \times 0.467}{1.95 \Omega \times 50 \text{ mA} \times 700 \text{ kHz}} = 6.84 \mu\text{F} \end{aligned} \quad (18)$$

A total value of 6.6 μF (using 3 2.2 μF X7R ceramic capacitors) is chosen therefore the actual ΔI_{LED-PP} is:

$$\Delta I_{LED-PP} = \frac{I_{LED} \times D}{r_D \times C_O \times f_{SW}}$$

$$\Delta I_{LED-PP} = \frac{1A \times 0.467}{1.95\Omega \times 6.6 \mu F \times 700 \text{ kHz}} = 52 \text{ mV}$$
(19)

Determine minimum allowable RMS current rating:

$$I_{CO-RMS} = I_{LED} \times \sqrt{\frac{D_{MAX}}{1 - D_{MAX}}} = 1A \times \sqrt{\frac{0.677}{1 - 0.677}} = 1.45A$$
(20)

The chosen components from step 5 are:

$$C6 = C17 = C19 = 2.2 \mu F$$
(21)

6.7 Peak Current Limit

Solve for R6:

$$R6 = \frac{245 \text{ mV}}{I_{LIM}} = \frac{245 \text{ mV}}{5A} = 0.049\Omega$$
(22)

The closest standard resistor is 0.05 Ω therefore I_{LIM} is:

$$I_{LIM} = \frac{245 \text{ mV}}{R6} = \frac{245 \text{ mV}}{0.05\Omega} = 4.9A$$
(23)

The chosen component from step 6 is:

$$R6 = 0.05\Omega$$
(24)

6.8 Loop Compensation

ω_{P1} is approximated:

$$\omega_{P1} = \frac{1 + D}{r_D \times C_O} = \frac{1.467}{1.95\Omega \times 6.8 \mu F} = 110k \frac{\text{rad}}{\text{sec}}$$
(25)

ω_{Z1} is approximated:

$$\omega_{Z1} = \frac{r_D \times D'^2}{D \times L1} = \frac{1.95\Omega \times 0.533^2}{0.467 \times 33 \mu H} = 36k \frac{\text{rad}}{\text{sec}}$$
(26)

T_{U0} is approximated:

$$T_{U0} = \frac{D' \times 620V}{(1 + D) \times I_{LED} \times R6} = \frac{0.533 \times 620V}{1.467 \times 1A \times 0.05\Omega} = 4510$$
(27)

To ensure stability, calculate ω_{P2} :

$$\omega_{P2} = \frac{\min(\omega_{P1}, \omega_{Z1})}{5 \times T_{U0}} = \frac{\omega_{Z1}}{5 \times 4510} = \frac{36k \frac{\text{rad}}{\text{sec}}}{5 \times 4510} = 1.596 \frac{\text{rad}}{\text{sec}}$$
(28)

Solve for C8:

$$C8 = \frac{1}{\omega_{P2} \times 5e^6\Omega} = \frac{1}{1.596 \frac{\text{rad}}{\text{sec}} \times 5e^6\Omega} = 0.13 \mu F$$
(29)

Since PWM dimming can be evaluated with this board, a much larger compensation capacitor C8 = 1.0 μF is chosen.

To attenuate switching noise, calculate ω_{P3} :

$$\omega_{P3} = \max(\omega_{P1}, \omega_{Z1}) \times 10 = \omega_{P1} \times 10$$

$$\omega_{P3} = 110k \frac{\text{rad}}{\text{sec}} \times 10 = 1.1M \frac{\text{rad}}{\text{sec}} \quad (30)$$

Assume $R_{20} = 10\Omega$ and solve for C_{12} :

$$C_{12} = \frac{1}{10\Omega \times \omega_{P3}} = \frac{1}{10\Omega \times 1.1M \frac{\text{rad}}{\text{sec}}} = 0.091 \mu\text{F} \quad (31)$$

The chosen components from step 7 are:

$$\begin{aligned} C_8 &= 1.0 \mu\text{F} \\ R_{20} &= 10\Omega \\ C_{12} &= 0.1 \mu\text{F} \end{aligned}$$

(32)

6.9 Input Capacitance

Solve for the minimum C_{IN} :

$$C_{IN} = \frac{I_{LED} \times D}{\Delta V_{IN-PP} \times f_{SW}} = \frac{1A \times 0.467}{100 \text{ mV} \times 700 \text{ kHz}} = 6.66 \mu\text{F} \quad (33)$$

To minimize power supply interaction a 3x larger capacitance of approximately 20 μF is used, therefore the actual ΔV_{IN-PP} is much lower. Since high voltage ceramic capacitor selection is limited, four 4.7 μF X7R capacitors are chosen.

Determine minimum allowable RMS current rating:

$$I_{IN-RMS} = I_{LED} \times \sqrt{\frac{D_{MAX}}{1 - D_{MAX}}} = 1A \times \sqrt{\frac{0.677}{1 - 0.677}} = 1.45A \quad (34)$$

The chosen components from step 8 are:

$$C_2 = C_3 = C_{16} = C_{18} = 4.7 \mu\text{F}$$

(35)

6.10 NFET

Determine minimum Q1 voltage rating and current rating:

$$V_{T-MAX} = V_{IN-MAX} + V_O = 70V + 21V = 91V \quad (36)$$

$$I_{T-MAX} = \frac{0.677}{1 - 0.677} \times 1A = 2.1A \quad (37)$$

A 100V NFET is chosen with a current rating of 40A due to the low $R_{DS-ON} = 50 \text{ m}\Omega$. Determine I_{T-RMS} and P_T :

$$I_{T-RMS} = \frac{I_{LED}}{D'} \times \sqrt{D} = \frac{1A}{0.533} \times \sqrt{0.467} = 1.28A \quad (38)$$

$$P_T = I_{T-RMS}^2 \times R_{DS-ON} = 1.28A^2 \times 50 \text{ m}\Omega = 82 \text{ mW} \quad (39)$$

The chosen component from step 9 is:

$$Q1 \rightarrow 40A, 100V, \text{ DPAK}$$

(40)

6.11 Diode

Determine minimum D1 voltage rating and current rating:

$$V_{RD-MAX} = V_{IN-MAX} + V_O = 70V + 21V = 91V \quad (41)$$

$$I_{D-MAX} = I_{LED} = 1A \quad (42)$$

A 100V diode is chosen with a current rating of 12A and $V_D = 600 \text{ mV}$. Determine P_D :

$$P_D = I_D \times V_{FD} = 1A \times 600 \text{ mV} = 600 \text{ mW} \quad (43)$$

The chosen component from step 10 is:

$$D1 \rightarrow 12A, 100V, \text{ DPAK} \quad (44)$$

6.12 Input UVLO

Since PWM dimming will be evaluated, a three resistor network will be used. Assume $R_{13} = 10 \text{ k}\Omega$ and solve for R_5 :

$$R_5 = \frac{1.24V \times R_{13}}{V_{\text{TURN-ON}} - 1.24V} = \frac{1.24V \times 10 \text{ k}\Omega}{10V - 1.24V} = 1.42 \text{ k}\Omega \quad (45)$$

The closest standard resistor is $1.43 \text{ k}\Omega$ therefore $V_{\text{TURN-ON}}$ is:

$$V_{\text{TURN-ON}} = \frac{1.24V \times (R_5 + R_{13})}{R_5}$$

$$V_{\text{TURN-ON}} = \frac{1.24V \times (1.43 \text{ k}\Omega + 10 \text{ k}\Omega)}{1.43 \text{ k}\Omega} = 9.91V \quad (46)$$

Solve for R_4 :

$$R_4 = \frac{R_5 \times (V_{\text{HYS}} - 20 \mu\text{A} \times R_{13})}{20 \mu\text{A} \times (R_5 + R_{13})}$$

$$R_4 = \frac{1.43 \text{ k}\Omega \times (2.9V - 20 \mu\text{A} \times 10 \text{ k}\Omega)}{20 \mu\text{A} \times (1.43 \text{ k}\Omega + 10 \text{ k}\Omega)} = 16.9 \text{ k}\Omega \quad (47)$$

The closest standard resistor is $16.9 \text{ k}\Omega$ making V_{HYS} :

$$V_{\text{HYS}} = \frac{20 \mu\text{A} \times R_4 \times (R_5 + R_{13})}{R_5} + 20 \mu\text{A} \times R_{UV2}$$

$$V_{\text{HYS}} = \frac{20 \mu\text{A} \times 16.9 \text{ k}\Omega \times (1.43 \text{ k}\Omega + 10 \text{ k}\Omega)}{1.43 \text{ k}\Omega} + 20 \mu\text{A} \times 10 \text{ k}\Omega = 2.9V \quad (48)$$

The chosen components from step 11 are:

$$\begin{aligned} R_5 &= 1.43 \text{ k}\Omega \\ R_{13} &= 10 \text{ k}\Omega \\ R_4 &= 16.9 \text{ k}\Omega \end{aligned} \quad (49)$$

6.13 Output OVLO

Solve for R_{18} :

$$R_{18} = \frac{V_{\text{HYSO}}}{20 \mu\text{A}} = \frac{15V}{20 \mu\text{A}} = 750 \text{ k}\Omega \quad (50)$$

The closest standard resistor is $750 \text{ k}\Omega$ therefore V_{HYSO} is:

$$V_{\text{HYSO}} = R_{18} \times 20 \mu\text{A} = 750 \text{ k}\Omega \times 20 \mu\text{A} = 15V \quad (51)$$

Solve for R_{11} :

$$R_{11} = \frac{1.24V \times R_{18}}{V_{\text{TURN-OFF}} - 1.24V} = \frac{1.24V \times 750 \text{ k}\Omega}{60V - 1.24V} = 15.8 \text{ k}\Omega \quad (52)$$

The closest standard resistor is $15.8 \text{ k}\Omega$ making $V_{\text{TURN-OFF}}$:

$$V_{\text{TURN-OFF}} = \frac{1.24\text{V} \times (R11 + R18)}{R11}$$

$$V_{\text{TURN-OFF}} = \frac{1.24\text{V} \times (15.8 \text{ k}\Omega + 750 \text{ k}\Omega)}{15.8 \text{ k}\Omega} = 60\text{V} \quad (53)$$

The chosen components from step 12 are:

R11 = 15.8 kΩ R18 = 750 kΩ

(54)

7 Typical Waveforms

$T_A = +25^\circ\text{C}$, $V_{IN} = 24\text{V}$ and $V_O = 21\text{V}$.

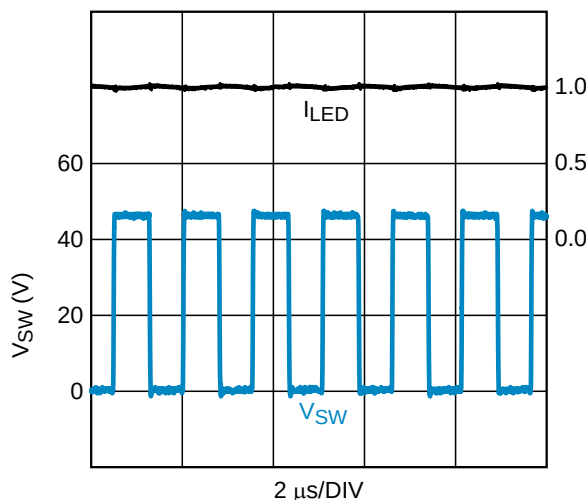


Figure 5. Standard Operation
TP1 Switch Node Voltage (V_{SW})
LED Current (I_{LED})

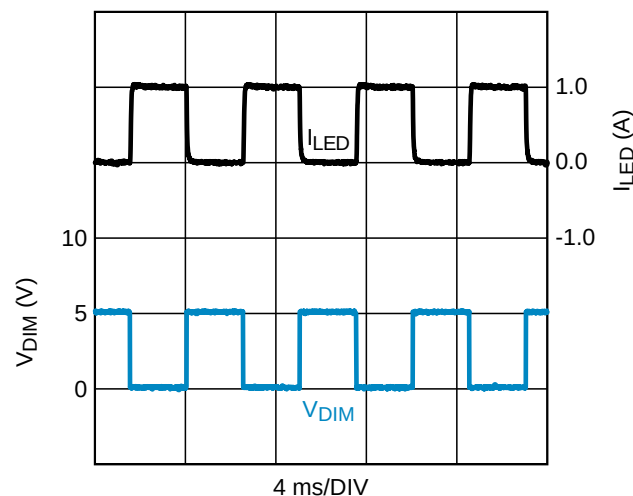


Figure 6. 200Hz 50% PWM Dimming
TP11 Dim Voltage (V_{DIM})
LED Current (I_{LED})

8 Alternate Designs

Alternate designs with the LM3429 evaluation board are possible with very few changes to the existing hardware. The evaluation board FETs and diodes are already rated higher than necessary for design flexibility. The input UVLO, output OVP, input and output capacitance can remain the same for the designs shown below. These alternate designs can be evaluated by changing only R9, R10, and L1.

The table below gives the main specifications for four different designs and the corresponding values for R9, R10, and L1. PWM dimming can be evaluated with any of these designs.

Table 1. Alternate Design Specification

Specification / Component	Design 1	Design 2	Design 3	Design 4
V_{IN}	10V - 45V	15V - 50V	20V - 55V	25V - 60V
V_O	14V	21V	28V	35V
f_{SW}	600kHz	700kHz	500kHz	700kHz
I_{LED}	2A	500mA	2.5A	1.25A
R9	0.05Ω	0.2Ω	0.04Ω	0.08Ω
R10	41.2 kΩ	35.7 kΩ	49.9 kΩ	35.7 kΩ
L1	22μH	68μH	15μH	33μH

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com