

Application Note

AN-SMPS-ICE2xXXX-1

CoolSET™

ICE2xXXX for OFF – Line Switch Mode Power Supply (SMPS)

Authors: Harald Zöllinger

Rainer Kling

Published by Infineon Technologies AG

<http://www.infineon.com>

Power Management & Supply



Never stop thinking

Contents:

OPERATING PRINCIPLES	3
PROTECTION FUNCTIONS.....	9
OVERLOAD AND OPEN-LOOP PROTECTION (FIG. 6).....	11
OVERVOLTAGE PROTECTION DURING SOFT START (FIG. 7).....	12
FREQUENCY REDUCTION.....	13
DESIGN PROCEDURE.....	14
<i>Input Diode Bridge (BR1):</i>	15
<i>Determine Input Capacitor (C3):</i>	15
<i>Transformer Design (TR1):</i>	17
SENSE RESISTOR	18
<i>Winding Design:</i>	19
<i>Output Rectifier (D1):</i>	21
<i>Output Capacitors (C5, C9):</i>	22
<i>Output Filter (L3, C23):</i>	23
<i>RC-Filter at Feedback Pin</i>	23
<i>Soft-start capacitor</i>	24
<i>VCC Capacitor:</i>	25
<i>Start-up Resistor (R6, R7):</i>	25
CLAMPING NETWORK:.....	26
CALCULATION OF LOSSES:	27
<i>Switching losses:</i>	28
<i>Conduction losses:</i>	28
REGULATION LOOP:	29
<i>Regulation Loop Elements:</i>	30
<i>Zeros and Poles of transfer characteristics:</i>	31
<i>Calculation of transient impedance Z_{PWM} of ICE2Axxx</i>	32
<i>Transfer characteristics:</i>	33
CONTINUOUS CONDUCTION MODE (CCM)	36
TRANSFORMER CALCULATION:.....	36
SLOPE COMPENSATION.....	37
TRANSFORMER CONSTRUCTION	38
LAYOUT RECOMMENDATION:.....	39
OUTPUT POWER TABLE	40
SUMMARY OF USED NOMENCLATURE.....	41
REFERENCES.....	42

Operating Principles

The **ICE2AXXX** is designed for a current-mode flyback configuration in **discontinuous (DCM) or continuous conduction (CCM)** mode.

The control circuit has a fixed frequency. The duty cycle (D) of the integrated CoolMOS Transistor is controlled to maintain a constant output voltage (V_{OUT}).

Fig. 1 shows the input voltage ($V_{DC IN}$), the primary current (I_{LPK}), and the secondary (I_{SEC}) transformer current of the flyback converter depicted on p. 3

When the CoolMOS Transistor is switched on, the initial state of all windings on the transformer is at positive potential.

The rectifier diode (D1) on the secondary side is reverse biased and therefore does not conduct. Consequently no current flows in the secondary winding. During this phase, energy is stored in the inductance of the primary winding and the transformer can be treated as a simple series inductor.

Fig. 1 shows that there is a linear increase of the primary current (I_{PRI}) while the CoolMOS Transistor is on.

When the CoolMOS Transistor is switched off, the voltage reverses on all transformer windings (flyback action) until it is clamped by rectifier diode on the secondary side. Now the secondary rectifier diode (D1) is conducting, and the magnetizing energy stored in the transformer core is transferred to the secondary side during the reset interval.

In the **discontinuous conduction mode DCM** the secondary current (I_{SEC}) decreases from its peak value to zero (Fig. 1). During this period the whole energy stored in the primary inductance is transferred to the secondary side (neglecting losses and energy stored in the primary leakage inductance), then the next storage cycle starts. Taking into account the transformer turns ratio, the secondary voltage (V_{SEC}) is “reflected” back (V_R) to the primary winding and adds to the input voltage ($V_{DC IN} + V_R$). An additional transient voltage may appear on the primary winding due to energy stored in the uncoupled “leakage” inductance in the primary winding. This voltage is not clamped by the secondary side winding. If the flyback current (I_{LPK} and I_{SEC}) does not reach zero before the next “on” – cycle the converter is operating in **continuous conduction mode** (Fig. 2).

Note:

When the system shifts to continuous conduction operation, its transfer function is changed to a two pole system with low output impedance. In this case additional design rules have to be taken into account including different loop compensation and slope compensation on the primary side.

Voltage and current waveforms in **discontinuous conduction mode (DCM)** operation:

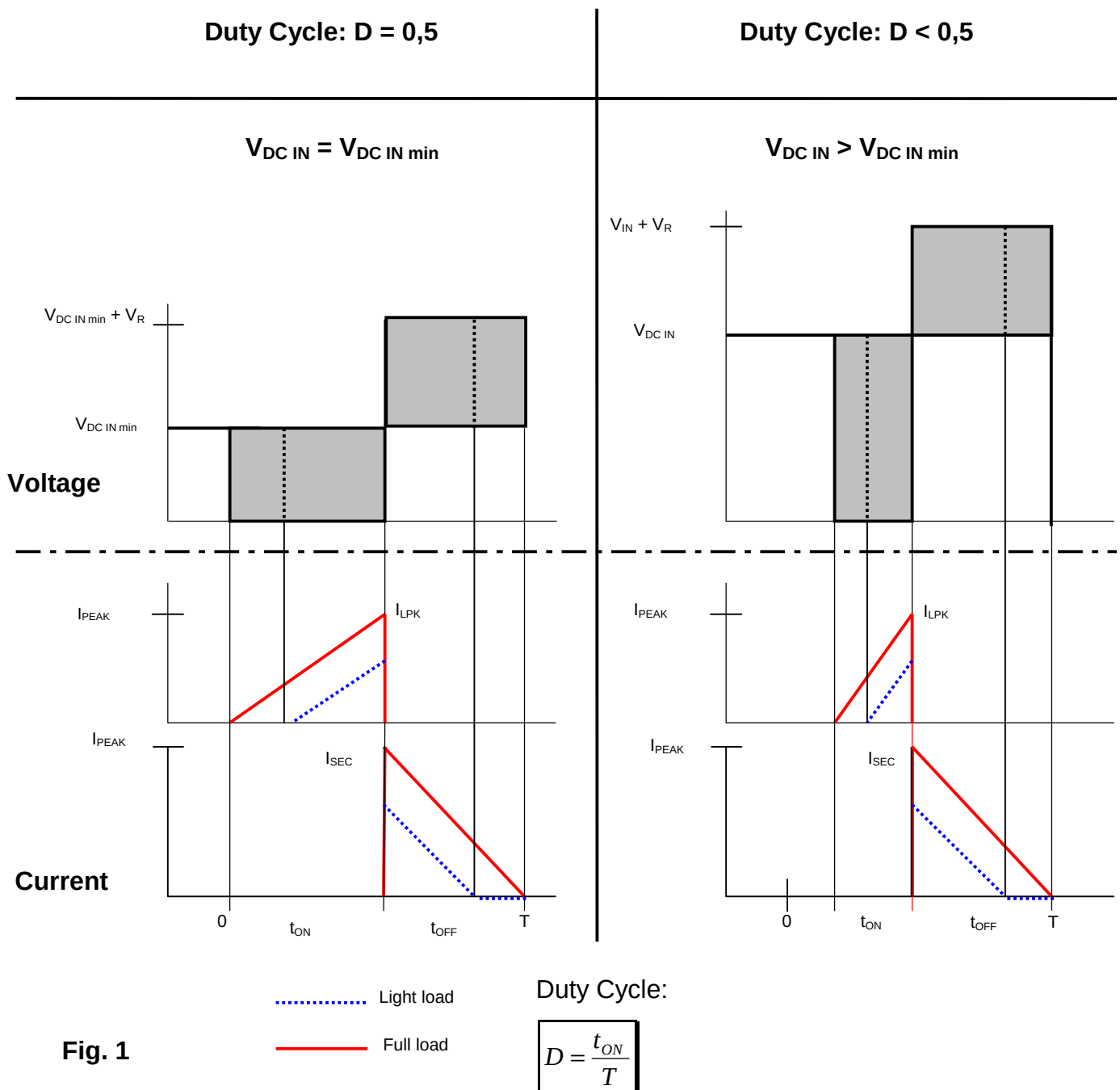


Fig. 1

Comparison of **continuous conduction** (CCM) and **discontinuous conduction** (DCM) mode.

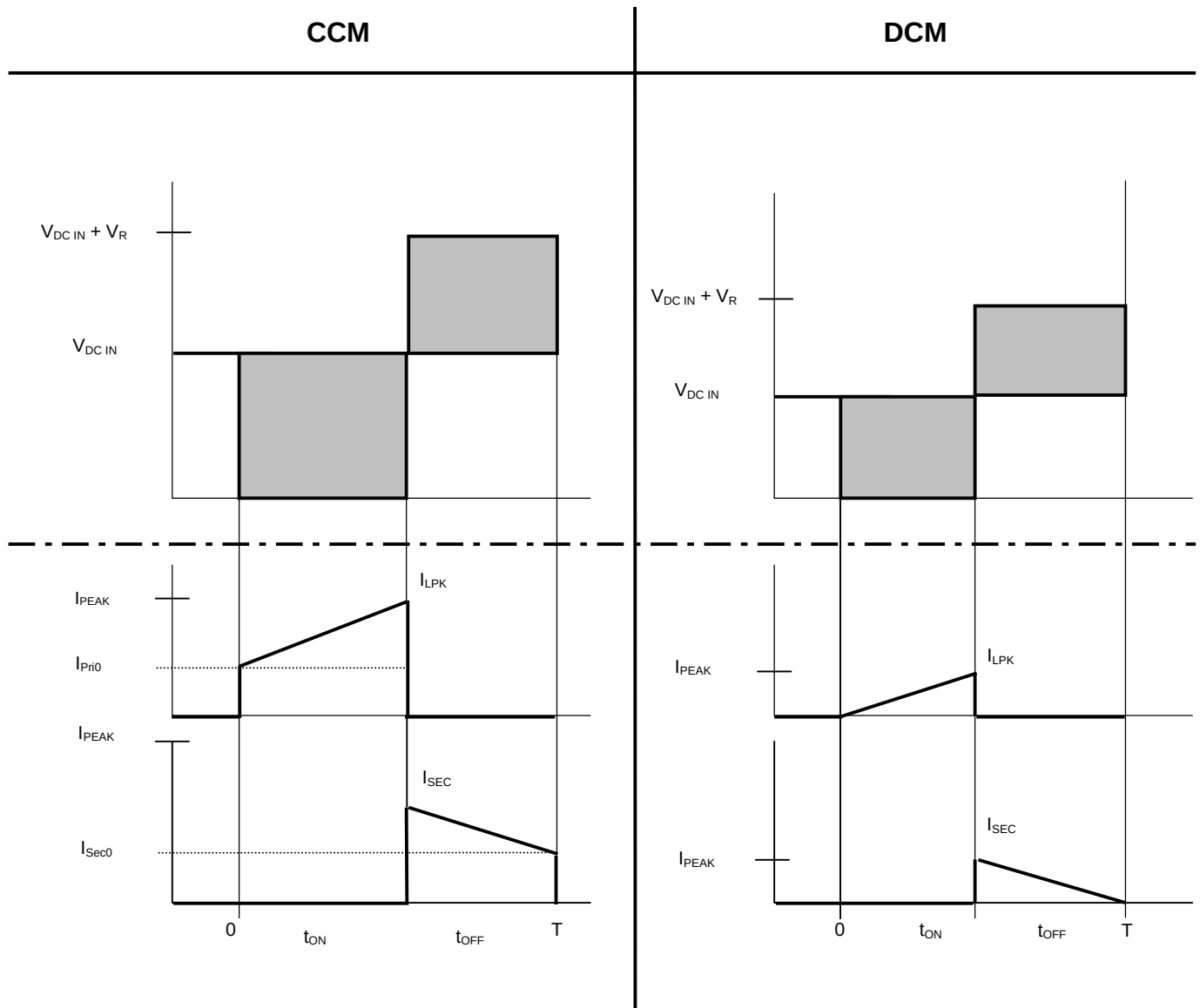


Fig. 2

Input stage

As shown in Fig. 3 the AC input power is rectified and filtered by the bridge rectifier (BR1) and the bulk capacitor C3. This creates a DC high voltage bus which is connected to the primary winding of the transformer (TR1). The transformer is driven by the CoolSET integrated high voltage, avalanche rugged CoolMOS transistor, with an external sense resistor (R17) for precision current measurement.

Output stage

The secondary winding power is rectified and filtered by a diode (D1), capacitors (C5, C9 and C20). The output LC-filter (L3, C23) reduces the output voltage ripple.

Other output voltages

Other output voltages can be realized by adjusting the transformer turn ratio and the output stage.

Chip supply

The current in the bias winding is rectified and filtered by a diode (D2) and a resistor (R8) in order to charge the supply capacitor (C4). This creates a bias voltage that powers the CoolSET ICE 2AXXX. The resistors R6 and R7 charge the VCC Cap and supply the chip during startup. The Zener diode (D4) clamps the chip supply voltage (Vcc) in order to protect the chip in case of an over-voltage condition. Capacitor C13 filters high frequency ripples on the chip supply voltage (Vcc).

Soft-Start

A soft-start function is activated during start-up, and can be adjusted by capacitor C14. In addition to start-up, soft-start is activated at each restart attempt during auto-restart and when restarting after one of the several protection functions are activated. This effectively minimizes current and voltage stresses on the CoolMOS MOSFET, the snubber network, and the output rectifier during start-up. The soft-start feature further helps to minimize output overshoot and prevents saturation of the transformer during start-up.

Clamping network

The clamping network which consists of a diode (D3), a resistor (R10) and a capacitor (C12) clamps the voltage spike caused by the transformer leakage inductance to a safe value this limits the avalanche losses of the CoolMOS transistor.

Control Loop

The resistors R1 and R2 represent the voltage divider for the reference diode TL431CLP (IC2). R4 supplies the TL431CLP reference diode with a minimum current and R3 the LED of the optocoupler. The network which consists of capacitors C1 and C2 determines the corner frequencies f_{g1} and f_{g2} . R5 sets the gain of the control loop.

Slope Compensation

The current mode controller becomes unstable whenever the steady – state duty cycle D is larger than 0.5. In order to realize a design with a duty cycle greater 0.5, the slope of the current needs to be compensated. The slope compensation is realized by the network consisting of capacitor C17, C18 and the resistor R19.

Ripple Reduction

Inductor L5 and capacitor C23 attenuate the differential – mode emission currents caused by the fundamental and harmonic frequencies of the primary current waveform.

SMPS Calculation Software FLYCAL

FLYCAL is an EXCEL spread sheet with all Equations needed for the easy calculaton of your SMPS. FLYCAL corresponds with the calculaton example in this application note. You only have to enter the main parameters of your application in FLYCAL and to follow step by step the principle outlined in the calculation example. FLYCAL contains all equations used in the example with the same consecutive numbering.

Circuit Diagram:

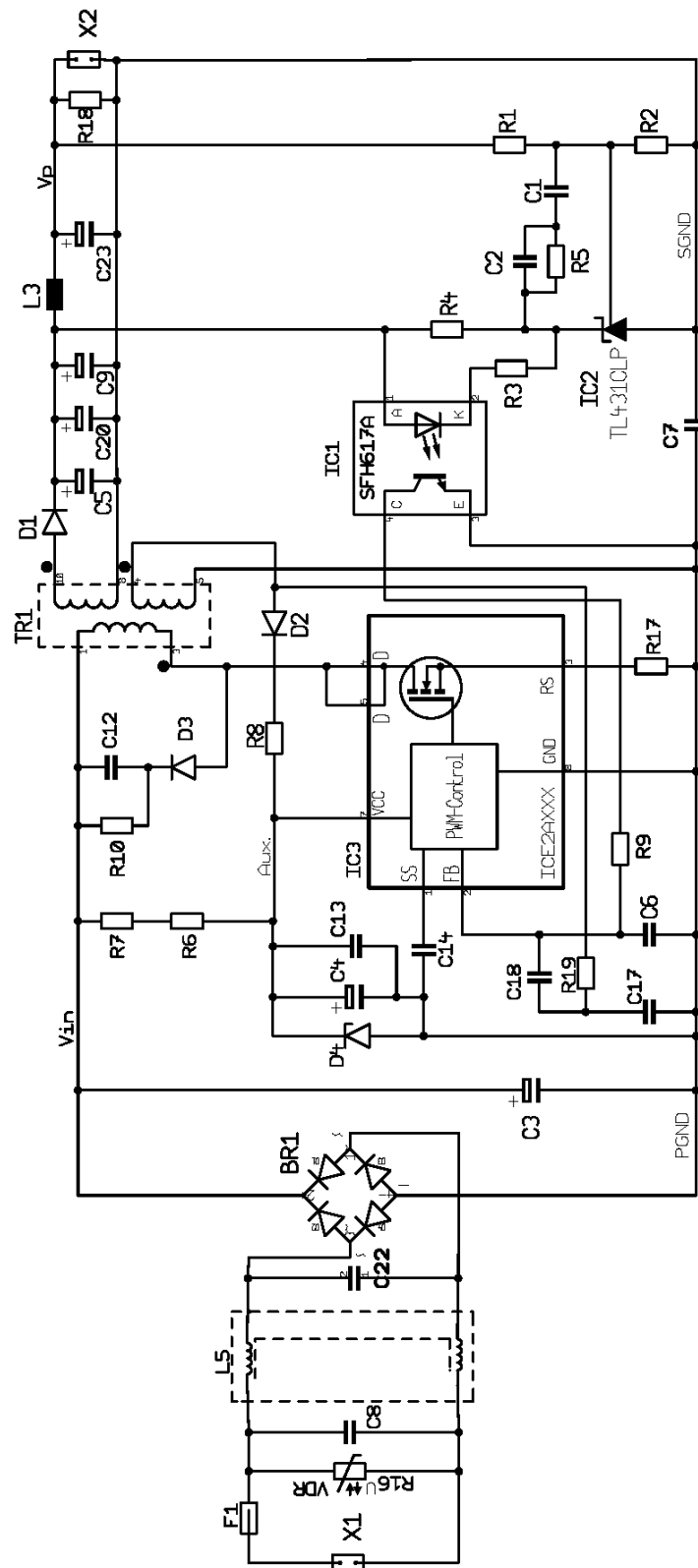


Fig. 3

Protection Functions

The block diagram displayed in Fig. 4 shows the internal functions of the protection unit. The comparators C1, C2, C3 and C4 compare the soft-start and feedback-pin voltages. Logic gates connected to the comparator outputs ensure the combination of the signals and enables the setting of the “Error-Latch”.

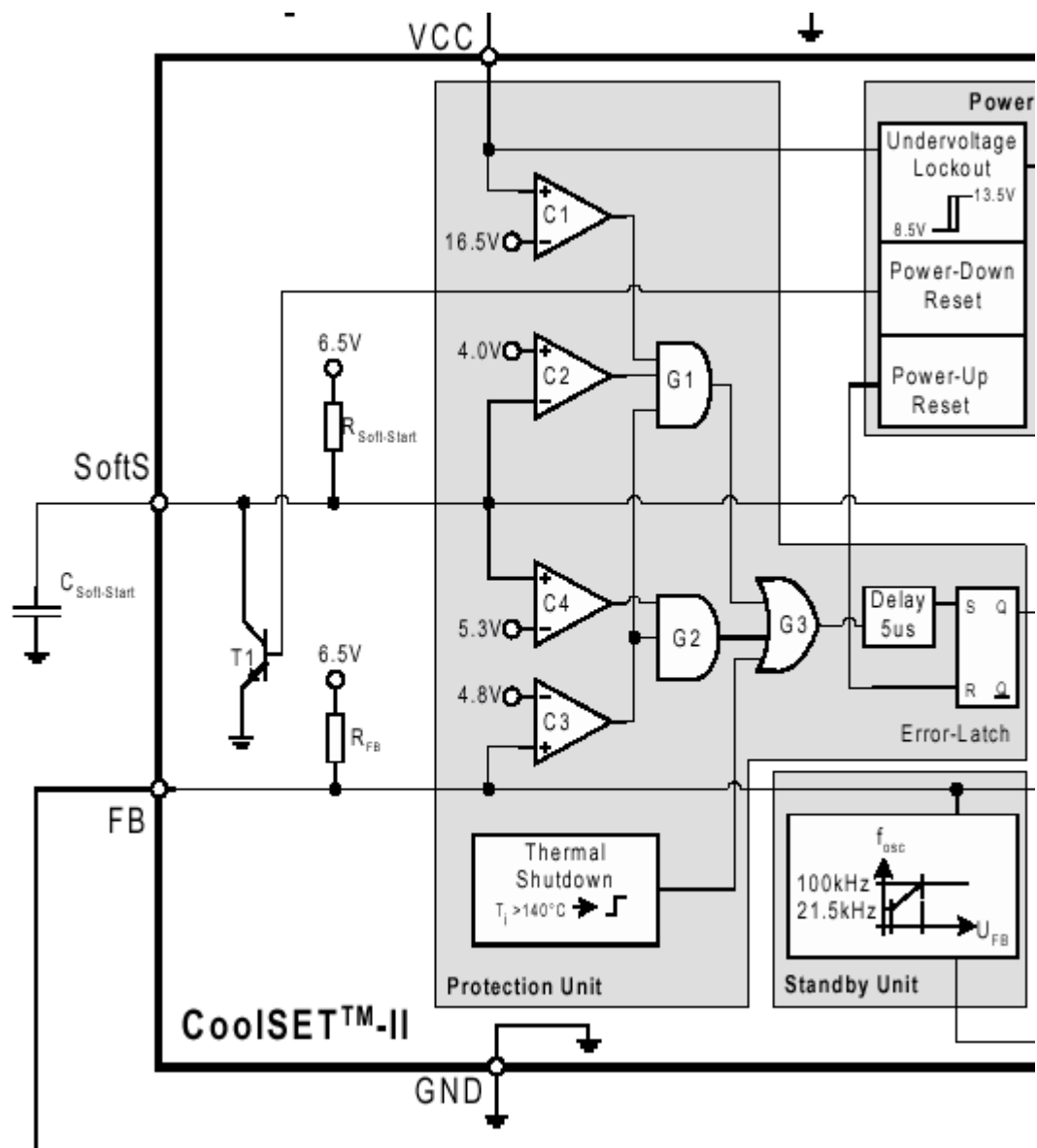


Fig. 4

Fig. 5 shows the relation between the voltages at the soft start (V_{SS}) and the feedback pins (V_{FB}) of **ICE2AXXX**, as a function of the supply voltage (V_{CC}) during an overvoltage condition at CoolSET soft start.

Depending on the voltage levels at the inputs, the overvoltage and (V_{CC} – PIN 7) and overload (V_{FB} – PIN 2) protection functions are activated.

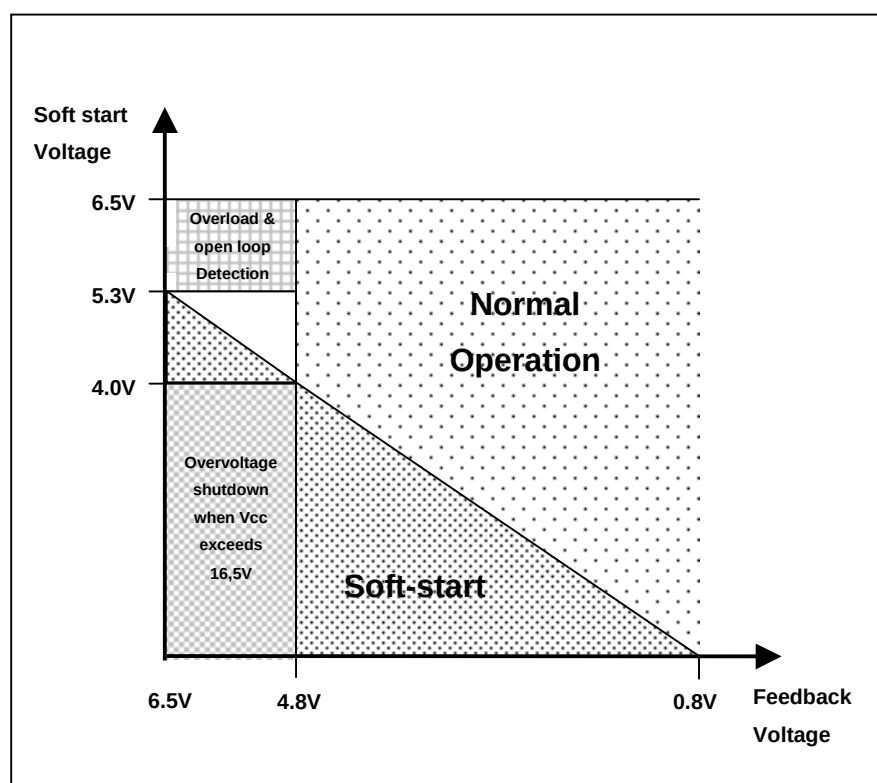


Fig. 5

Overload and Open-Loop Protection

- Feedback voltage (**VFB**) exceeds 4.8V and soft start voltage (**VSS**) is above 5.3V (soft start is completed) (**t1**)
- After a 5 μ s delay the **CoolMOS** is switched off (**t2**)
- Voltage at Vcc – Pin (**VCC**) decreases to 8.5V (**t2**)
- Control logic is switched off (**t3**)
- Start-up resistor charges Vcc capacitor (**t3**)
- Operation starts again with soft start after Vcc voltage has exceeded 13.5V (**t4**)

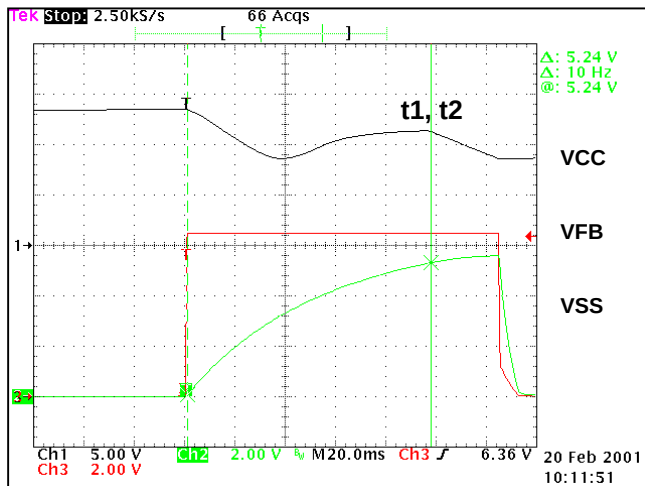


Fig. 7

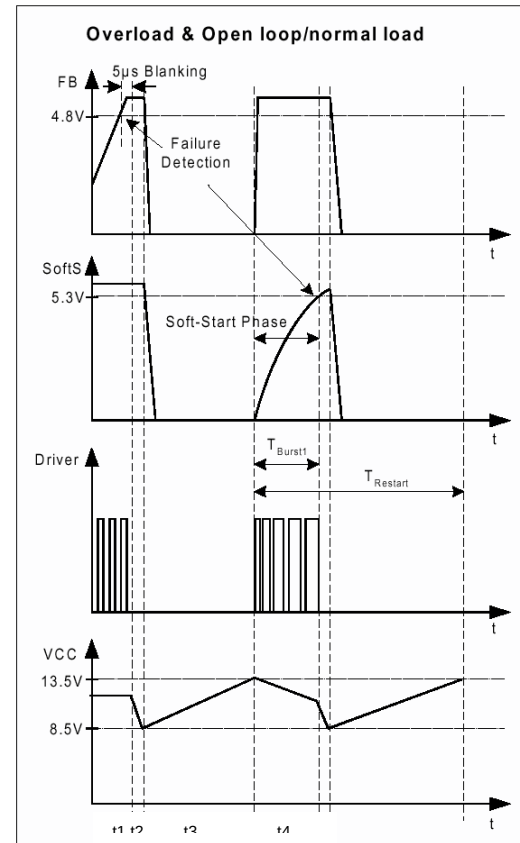


Fig. 6

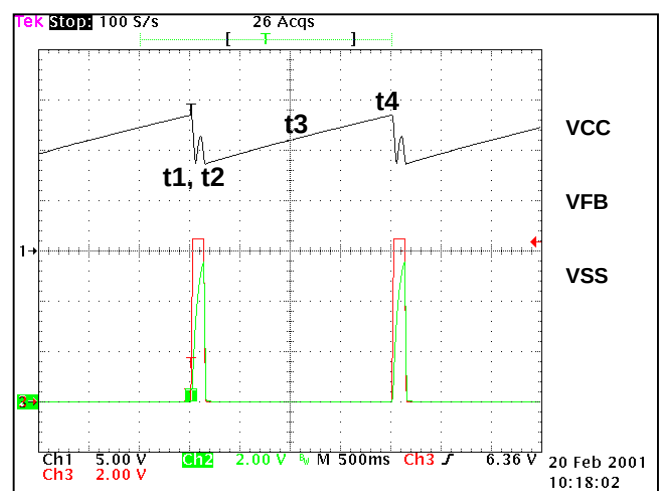


Fig. 8

Overvoltage Protection During Soft Start

- Feedback voltage (**VFB**) exceeds 4.8V and soft-start voltage (**VSS**) is below 4.0V (soft start phase) (**t1**)
- Voltage at Vcc pin (**VCC**) exceeds 16.5V (**t2**)
- CoolMOS transistor is immediately switched off (**t2**)
- Voltage at VCC pin decreases to 8.5V (**t3**)
- Control logic is switched off (**t3**)
- Start-up resistor charges VCC capacitor (**t4**)
- Operation starts again with soft start after VCC voltage has exceeded 13.5V (**t5**)

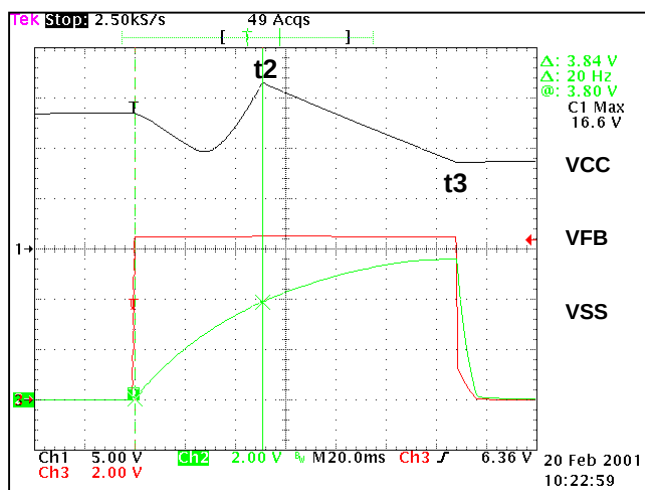


Fig. 10

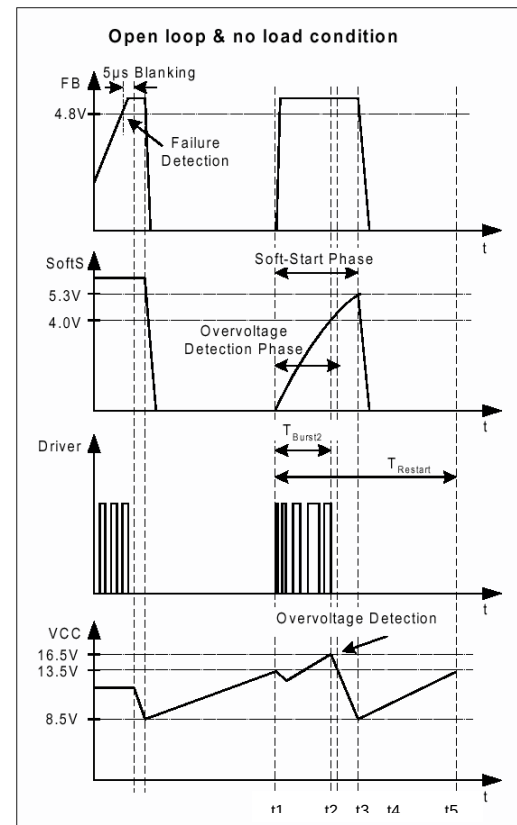


Fig. 9

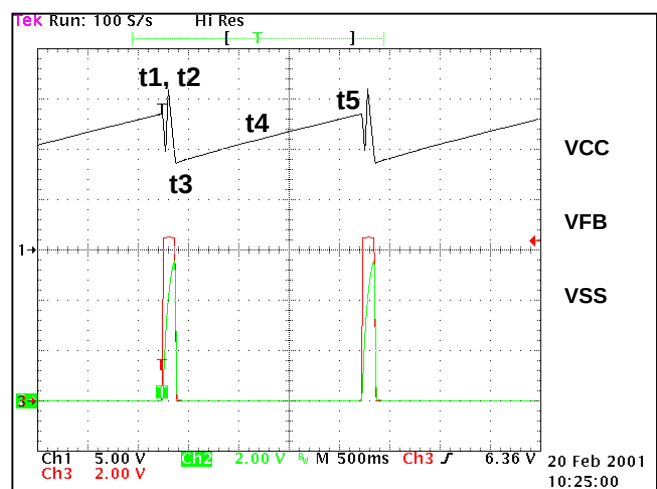


Fig. 11

Frequency Reduction

The frequency of the oscillator depends on the voltage at pin FB.

Below a voltage of typ. 1.75V the frequency decreases down to 21.5 kHz.

Due to this frequency reduction the power losses in low load condition can be reduced very effectively.

This dependency is shown in Fig. 12

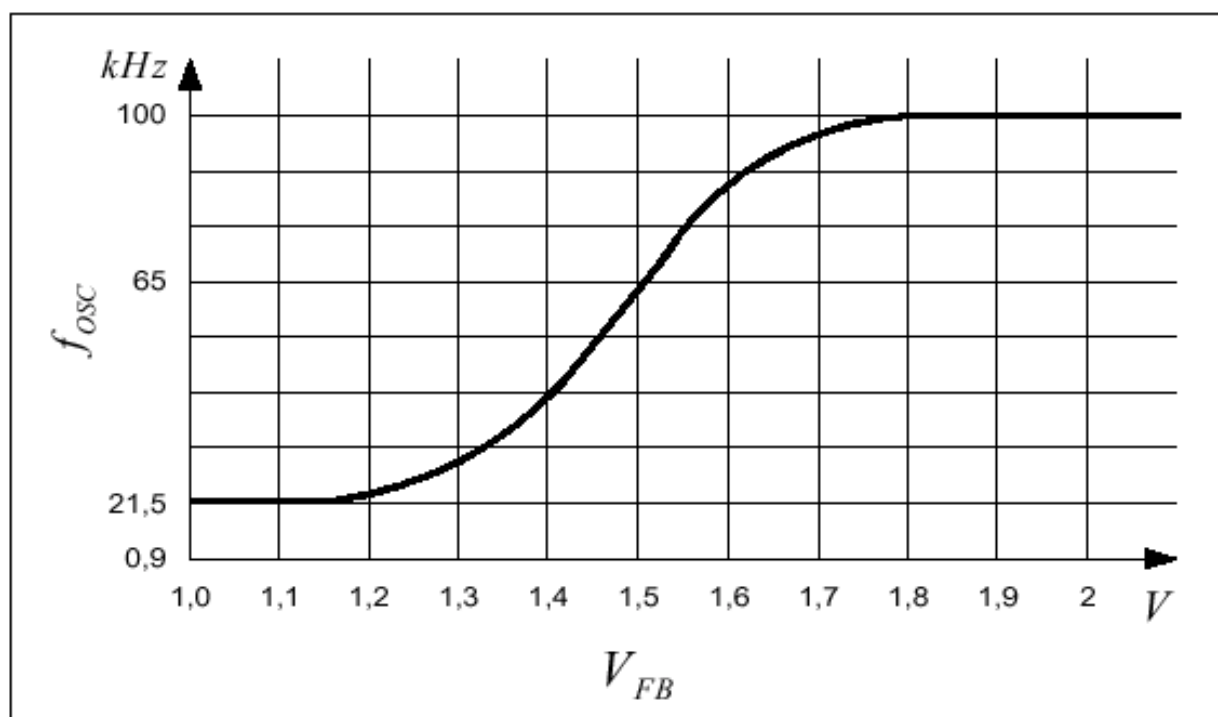


Fig. 12

Design Procedure

for fixed frequency Flyback Converter with **ICE2Axxx** operating in **discontinuous** current mode.

Procedure		Example
Define input Parameters:		
Minimal AC input voltage:	$V_{AC \min}$	90V
Maximal AC input voltage:	$V_{AC \max}$	264V
Line frequency:	f_{AC}	50Hz
Max. output power:	$P_{OUT \max}$	50W
Nom. output power:	$P_{OUT \text{ nom}}$	40W
Min. output power:	$P_{OUT \min}$	0,5W
Output voltage:	V_{OUT}	16V
Output ripple voltage:	$V_{OUT \text{ Ripple}}$	0,05V
Reflection voltage:	V_{Rmax}	120V
Estimated efficiency:	η	0,85
DC ripple voltage:	$V_{DC \text{ IN Ripple}}$	30V
Auxiliary voltage:	V_{Aux}	12V
Optocoupler gain:	G_C	1
Used CoolSET		ICE2A365
There are no special requirements imposed on the input rectifier and storage capacitor in the flyback converter. The components will be selected to meet the power rating and hold-up requirements.		
Maximum input power:		
$P_{IN \max} = \frac{P_{OUT \max}}{\eta} \quad (\text{Eq 1})$		$P_{IN \max} = \frac{50W}{0,85} = 59W$

Input Diode Bridge (BR1):

$$I_{ACRMS} = \frac{P_{IN\ MAX}}{V_{AC\ min} \cdot \cos \varphi} \quad (\text{Eq 2})$$

$$I_{ACRMS} = \frac{59W}{90V \cdot 0,6} = 1,09A$$

Maximum DC IN voltage

$$V_{DC\ max\ PK} = V_{AC\ max} \cdot \sqrt{2} \quad (\text{Eq 3})$$

$$V_{DC\ max\ PK} = 264V \cdot \sqrt{2} = 373V$$

Determine Input Capacitor (C3):

Minimum peak input voltage at "no load" condition

$$V_{DC\ min\ PK} = V_{AC\ min} \cdot \sqrt{2} \quad (\text{Eq 4})$$

$$V_{DC\ min\ PK} = 90V \cdot \sqrt{2} = 127V$$

$$V_{DC\ min} = V_{DC\ min\ PK} - V_{Ripple} \quad (\text{Eq 5})$$

we choose a ripple voltage of 30V

$$V_{DC\ min} = 127V - 30V = 97V$$

Calculation of discharging time at each half-line cycle:

$$T_D = 5ms \cdot \left(1 + \frac{\arcsin \frac{V_{DC\ min}}{V_{DC\ min\ PK}}}{90} \right) \quad (\text{Eq 6})$$

$$T_D = 5ms \cdot \left(1 + \frac{\arcsin \frac{97V}{127V}}{90} \right) = 7,7ms$$

Required energy at discharging time of C3:

$$W_{IN} = P_{IN\ max} \cdot T_D \quad (\text{Eq 7})$$

$$W_{IN} = 59W \cdot 7,7ms = 0,46Ws$$

Calculation of input capacitor value C_{IN} :

$$C_{IN} = \frac{2 \cdot W_{IN}}{V_{DC\ min\ PK}^2 - V_{DC\ min}^2} \quad (\text{Eq 8})$$

$$C_{IN} = \frac{2 \cdot 0,46Ws}{16129V^2 - 9409V^2} = 136,9\mu F$$

Alternatively a rule of thumb for choosing C_{IN} can be applied:

Input voltage	C_{IN}
115V	$2\mu F/W$
230V	$1\mu F/W$
85V ...270V	$2 \dots 3\mu F/W$

$$59W \cdot 3 \frac{\mu F}{W} = 177\mu F$$

Recalculation of input Capacitor:

Select a capacitor from the Epcos Databook of **Aluminium Electrolytic Capacitors**.

The following types are **preferred**:

For 85°C Applications:

Series B43303-.....	2000h life time
B43501-.....	10000h life time

For 105°C Applications:

Series B43504 -.....	3000h life time
B43505-.....	5000h life time

We choose 150μF 400V (based on Eq 8)

$$V_{DC \min} = \sqrt{V_{DC \min PK}^2 - \frac{2 \cdot W_{IN}}{C_{IN}}} \quad \text{(Eq 9)}$$

$$V_{DC \min} = \sqrt{16129V^2 - \frac{2 \cdot 0,46Ws}{150\mu F}} = 100V$$

Note that special requirements for hold up time, including cycle skip/dropout, or other factors which affect the resulting minimum DC input voltage and capacitor time should be considered at this point also.

Transformer Design (TR1):

Calculation of peak current of primary inductance:

$$D_{\max} = \frac{V_{R\max}}{V_{R\max} + V_{DC\min}} \quad (\text{Eq 10a})$$

$$I_{LPK} = \frac{2 \cdot P_{IN\max}}{V_{DC\min} \cdot D_{\max}} \quad (\text{Eq 10b})$$

$$I_{LRMS} = I_{LPK} \cdot \sqrt{\frac{D_{\max}}{3}} \quad (\text{Eq 11})$$

Calculation of primary inductance within the limit of **maximum Duty-Cycle** :

$$L_P = \frac{D_{\max} \cdot V_{DC\min}}{I_{LPK} \cdot f} \quad (\text{Eq 12})$$

Select core type and inductance factor (A_L) from **Epcos**

„**Ferrite Databook**“ or CD-ROM

„**Passive Components**“.

Fix maximum flux density:

$B_{\max} \approx 0,2T \dots 0,3T$ for ferrite cores depending on core material.

We choose 0,2T for material N27

The number of primary turns can be calculated as:

$$N_P = \sqrt{\frac{L_P}{A_L}} \quad (\text{Eq 13})$$

The number of secondary turns can be calculated as:

$$N_S = \frac{N_P \cdot (V_{OUT} + V_{F\text{DIODE}})}{V_{R\max}} \quad (\text{Eq 14})$$

The number of auxiliary turns can be calculated as:

$$N_{Aux} = \frac{N_S \cdot (V_{Aux} + V_{F\text{DIODE}})}{V_{R\max}} \quad (\text{Eq 15})$$

$$D_{\max} = \frac{120V}{120V + 100V} = 0,55$$

$$I_{LPK} = \frac{2 \cdot 59W}{100V \cdot 0,55} = 2,16A$$

$$I_{LRMS} = 2,16A \cdot \sqrt{\frac{0,55}{3}} = 0,92A$$

$$L_P = \frac{0,55 \cdot 100V}{2,16A \cdot 100 \cdot 10^3 \text{ Hz}} = 253\mu H$$

Selected core: **E 25/13/7**

Material = N27

$A_L = 111 \text{ nH}$

$s = 0,75 \text{ mm}$

$A_e = 52 \text{ mm}^2$

$A_N = 61 \text{ mm}^2$

$l_N = 57,5 \text{ mm}$

$$N_P = \sqrt{\frac{253\mu H}{111nH}} = 47,7 \text{ turns}$$

we choose $N_P = 46$ turns

$$N_S = \frac{46 \cdot (16V + 0,8V)}{120V} = 6,46$$

we choose $N_S = 7$ turns

$$N_S = \frac{46 \cdot (12V + 0,7V)}{120V} = 5,6$$

we choose $N_{Aux} = 5$ turns

Verification of primary inductance, primary peak current, max. duty cycle, flux density and gap:

$$L_P = N_P^2 \cdot A_l \quad (\text{Eq 16})$$

$$L_P = 46^2 \cdot 111\text{nH} = 235\mu\text{H}$$

$$I_{LPK} = \sqrt{\frac{P_{IN\max}}{0,5 \cdot L_P \cdot f}} \quad (\text{Eq 17})$$

$$I_{LPK} = \sqrt{\frac{59\text{W}}{0,5 \cdot 235\mu\text{H} \cdot 100 \cdot 10^3 \text{Hz}}} = 2,24\text{A}$$

$$V_R = \frac{(V_{OUT} + V_{FDIODE}) \cdot N_P}{N_S} \quad (\text{Eq 18})$$

$$V_R = \frac{(16\text{V} + 0,8\text{V}) \cdot 46}{7} = 110\text{V}$$

$$D_{\max} = \frac{L_P \cdot I_{LPK} \cdot f}{V_{DC\min}} \quad (\text{Eq 19})$$

$$D_{\max} = \frac{235\mu\text{H} \cdot 2,24\text{A} \cdot 100\text{kHz}}{100\text{V}} = 0,53$$

$$D'_{\max} = \frac{L_P \cdot I_{LPK} \cdot f}{V_R} \quad (\text{Eq 20})$$

$$D'_{\max} = \frac{235\mu\text{H} \cdot 2,24\text{A} \cdot 100\text{kHz}}{110\text{V}} = 0,47$$

$$B_{\max} = \frac{L_P \cdot I_{LPK}}{N_P \cdot A_e} \quad (\text{Eq 21})$$

$$B_{\max} = \frac{235\mu\text{H} \cdot 2,24\text{A}}{46 \cdot 52\text{mm}^2} = 210\text{mT}$$

$$s = \frac{4 \cdot \pi \cdot 10^{-7} \cdot N_P^2 \cdot A_e}{L_P} \quad (\text{Eq 22})$$

$$s = \frac{4 \cdot \pi \cdot 10^{-7} \cdot 46^2 \cdot 52\text{mm}^2}{235\mu\text{H}} = 0,588\text{mm}$$

Sense resistor

The sense resistance R_{Sense} can be used to individually define the maximum peak current and thus the maximum power transmitted.

Caution:

When calculating the maximum peak current, short term peaks in output-power must also be taken into consideration.

$V_{\text{csth}} = 1.0\text{V typ.}$ (taken from data sheet)

$$R_{\text{Sense}} = \frac{V_{\text{csth}}}{I_{LPK}} \quad (\text{Eq23})$$

$$R_{\text{Sense}} = \frac{1,0\text{V}}{2,24\text{A}} = 0,45\Omega$$

we select $0,43\Omega$

$$I_{LPK} = 2,33\text{A}$$

$$P_{\text{OUTmax}} = 54\text{W}$$

Winding Design:

see also page 38

Transformer Construction

The primary winding of 46 turns has to be divided into 23+23 turns in order to get the best coupling between primary and secondary winding.

The effective bobbin width and winding cross section can be calculated as:

$$BW_e = BW - 2 \cdot M \quad (\text{Eq 24})$$

$$A_{Ne} = \frac{A_N \cdot BW_e}{BW} \quad (\text{Eq 25})$$

Calculate copper section for **primary and secondary** winding:

The winding cross section A_N has to be subdivided according to the number of windings.

Primary winding	0,5
Secondary winding	0,45
Auxiliary winding	0,05

Copper space factor f_{Cu} :0,20,4

$$A_p = \frac{0,5 \cdot A_N \cdot f_{Cu} \cdot BW_e}{N_p \cdot BW} \quad (\text{Eq 26})$$

$$AWG = 9,97 \cdot (1,8277 - (2 \cdot \log(d))) \quad (\text{Eq 27})$$

From bobbin datasheet E25/13/7: BW = 15,6mm

Margin determined: M = 0mm

we use triple insulated wire for secondary winding

$$BW_e = 15,6mm$$

$$A_{Ne} = 61mm^2$$

We calculate the **available area** for each winding:

Used for calculation: $f_{Cu} = 0,3$

$$A_p = \frac{0,5 \cdot 61mm^2 \cdot 0,3}{46} = 0,2mm^2$$

diameter dp $\approx$ 0,5mm **25 AWG**

$$A_s = \frac{0,45 \cdot A_N \cdot f_{Cu} \cdot BW_e}{N_s \cdot BW}$$

(Eq 28)

$$A_s = \frac{0,45 \cdot 61mm^2 \cdot 0,3}{7} = 1,18mm^2$$

diameter ds 2 x 0,8mm **2 x 20 AWG**

$$A_{aux} = \frac{0,05 \cdot A_N \cdot f_{Cu} \cdot BW_e}{N_{aux} \cdot BW}$$

(Eq 29)

$$A_{aux} = \frac{0,05 \cdot 61mm^2 \cdot 0,3}{5} = 0,18mm^2$$

diameter da ≈ 0,5mm **25 AWG**

With the effective bobbin width we check the number of turns per layer:

$$N_p = \frac{BWe}{d_p}$$

(Eq 30)

$$N_p = \frac{15,6mm}{0,46mm} = 31 \text{ turns per layer}$$

2 layer needed

Secondary:

$$N_s = \frac{15,6mm}{2 \cdot 1,21mm} = 6 \text{ turns per layer}$$

2 layer needed

Auxiliary:

1 layer !

Output Rectifier (D1):

The output rectifier diodes in flyback converters are subjected to a large PEAK and RMS current stress. The values depend on the load and operating mode. The voltage requirements depend on the output voltage and the transformer winding ratio.

Calculation of the maximum reverse voltage:

$$V_{RDiode} = V_{OUT} + \left(V_{DC \max PK} \cdot \frac{N_S}{N_P} \right) \quad (\text{Eq 31}) \quad V_{RDiode} = 16V + \left(373V \cdot \frac{7}{46} \right) = 72,8V$$

Calculation of the maximum current on secondary side:

$$I_{SPK} = I_{LPK} \cdot \frac{N_P}{N_S} \quad (\text{Eq 32}) \quad I_{SPK} = 2,33A \cdot \frac{46}{7} = 15,3A$$

$$I_{SRMS} = I_{SPK} \cdot \sqrt{\frac{1}{3} \cdot D'_{\max}} \quad (\text{Eq 33}) \quad I_{SRMS} = 15,3A \cdot \sqrt{\frac{1}{3} \cdot 0,47} = 5,9A$$

Output Capacitors (C5, C9):

Output capacitors are highly stressed in flyback converters. Normally the capacitor will be selected for **3 major parameters: capacitance value, low ESR and ripple current rating.**

Max. voltage overshoot: ΔV_{OUT}

Number of clock periods: n_{CP}

$$C_{OUT} = \frac{I_{OUT\max} \cdot n_{CP}}{\Delta V_{OUT} \cdot f} \quad (\text{Eq 34})$$

$$I_{OUT} = \frac{P_{OUT\max}}{V_{OUT}} \quad (\text{Eq 34a})$$

$$I_{Ripple} = \sqrt{I_{SRMS}^2 - I_{OUT}^2} \quad (\text{Eq 34b})$$

Select a capacitor out of **Epcos** Databook for **Aluminium Electrolytic Capacitors.**

The following types are **preferred**:

For 105°C Applications low impedance:
Series B41856-..... 4000h life time

For 105°C Applications lowest impedance:
Series B41859-..... 4000h life time

To calculate the output capacitor, it is necessary to set the maximum voltage overshoot in case of switching off @ maximum load condition.

After switching off the load, the control loop needs about 10...20 internal clock periods to reduce the duty cycle.

$$\Delta V_{OUT} = 0,5V$$

$$n_{CP} = 20$$

$$C_{OUT} = \frac{3,1A \cdot 20}{0,5V \cdot 100 \cdot 10^3 \text{ Hz}} = 1250\mu F$$

$$I_{OUT} = \frac{50W}{16V} = 3,1A$$

$$I_{Ripple} = \sqrt{5,9A^2 - 3,1A^2} = 5,0A$$

We select 1000μF 35V (based on Eq 34):

B41859-F7108-M

$$ESR \approx Z_{max} = 0,034\Omega @ 100kHz$$

$$I_{acR} = 1,94A$$

we need 2 capacitors in parallel

Output Filter (L3, C23):

The output filter consists of one capacitor (C23) and one inductor (L3) in a L-C filter topology.

Zero frequency of output capacitor (C5,C9, C20) and associated ESR:

$$f_{ZCOUT} = \frac{1}{2 \cdot \pi \cdot R_{ESR} \cdot C_{OUT}} \quad (\text{Eq 35})$$

$$f_{ZCOUT} = \frac{1}{2 \cdot \pi \cdot 0,034\Omega \cdot 1000\mu F} = 4,7\text{kHz}$$

Calculation of the inductance (L3) needed for the substitution of the zero caused by the output capacitors:

We use C_{LC} (C23) 470uF

$$L_{OUT} = \frac{(C_{OUT} \cdot R_{ESR})^2}{C_{LC}} \quad (\text{Eq 36})$$

$$L_{OUT} = \frac{(1000\mu F \cdot 0,034\Omega)^2}{470\mu F} = 2,5\mu H$$

RC-Filter at Feedback Pin (C6, R9)

The RC Filter at the Feedback pin is designed to suppress any noise which may be coupled in on this track.

Typical values:

C6 : 1...4,7nF

R9 : 22 Ohm

Note that the value of C6 interacts with the internal pullup (3,7k typical) to create a filter.

Soft-start capacitor

(C14)

The voltage at the soft-start pin together with feedback voltage controls the overvoltage, open loop and overcurrent protection functions.

The softstart capacitor must be calculated in such a way that the output voltage and thus the feedback voltage is within the working range ($V_{FB} < 4.8V$) before the over-current threshold (typ. 5.3V) is reached.

$R_{soft\ start} = 50k\Omega$ typ (from datasheet).

$$t_{Sstart} = V_o^2 \cdot \frac{C_{out}}{P_{OUT\ max} - P_{OUTnom}} \quad (\text{Eq37})$$

$$t_{Sstart} = 16V^2 \cdot \frac{2470\mu F}{54W - 40W} = 45ms$$

$$C_{SS} = t_{Sstart} \cdot \frac{1}{-R_{Soft-Start} \cdot \ln(1 - \frac{V_{Soft-Start1}}{V_{REF}})} \quad (\text{Eq38})$$

$$C_{SS} = 45ms \cdot \frac{1}{-50k\Omega \cdot \ln(1 - \frac{5,1V}{6,5V})} = 586nF$$

choose 560nF

VCC Capacitor:

(C4, C13)

The VCC capacitor needs to ensure the power supply of the IC until the power can be provided by the auxiliary winding.

In parallel with the VCC Capacitor it is recommended to use a 100nF ceramic capacitor very close between pin 7 & 8. Alternatively, an HF type electrolytic with low ESR and ESL may be used.

$$C_{VCC} = \frac{I_{VCC3} \cdot t_{softstart}}{V_{CCHY}} \cdot \frac{2}{3} \quad (\text{Eq 39})$$

$$C_{VCC} = \frac{8,2mA \cdot 45ms}{5V} \cdot \frac{2}{3} = 49\mu F$$

we choose 47uF

Start-up Resistor (R6, R7):

I_{VCC1} = max. quiescent current (Control IC)

I_{LoadC} = VCC-Capacitor load-current (C4)

C_{VCC} = Value of VCC-capacitor (C4)

$$R_{Start} = \frac{V_{DC\ min}}{I_{VCC1} + I_{LoadC}} \quad (\text{Eq 40})$$

$$I_{CCLmax} = 55\mu A$$

$$I_{LoadC} = 70\mu A$$

$$R_{Start} = \frac{100V}{(55 + 70)\mu A} = 801k\Omega$$

$$R6 = R7 = 1/2 R_{Start} = 400k\Omega$$

Choose 2 with value: 390kΩ

Start up Time t_{Start} :

$$t_{Start} = \frac{C_{VCC} \cdot V_{CCon}}{I_{LoadC}} \quad (\text{Eq 41})$$

$$t_{Start} = \frac{47\mu F \cdot 13,5V}{73\mu A} = 8,7s$$

Note:

Before the IC can be plugged into the application board, the VCC capacitor must be always **discharged!**

Clamping Network:

(R10/C12/D3)

$$V_{Clamp} = V_{(BR)DSS} - V_{DC\max} - V_R \quad (\text{Eq 42})$$

$$V_{Clamp} = 650V - 373V - 110V = 166V$$

For calculating the clamping network it is necessary to know the leakage inductance. The most common way is to have the value of the leakage inductance (L_{LK}) given in percentage of the primary inductance (L_p). If it is known that the transformer construction is very consistent, measuring the primary leakage inductance by shorting the secondary windings will give an exact number (assuming the availability of a good LCR analyser).

In our example we choose 5% of the primary inductance for leakage inductance.

$$L_{LK} = L_p \cdot x\%$$

$$L_{LK} = 235\mu H \cdot 5\% = 11,8\mu H$$

$$C_{Clamp} = \frac{I_{LPK}^2 \cdot L_{LK}}{(V_R + V_{Clamp}) \cdot V_{Clamp}} \quad (\text{Eq 43})$$

$$C_{Clamp} = \frac{(2,24A)^2 \cdot 11,8\mu H}{(110V + 166V) \cdot 166V} = 1,2nF \approx$$

we choose 1,5nF

$$R_{Clamp} = \frac{(V_{Clamp} + V_R)^2 - V_R^2}{0,5 \cdot L_{LK} \cdot I_{LPK}^2 \cdot f} \quad (\text{Eq 44})$$

$$R_{Clamp} = \frac{(166V + 110V)^2 - 110V^2}{0,5 \cdot 11,8\mu H \cdot (2,24A)^2 \cdot 100 \cdot 10^3 Hz} = 23,9k\Omega$$

we choose 22kΩ

Calculation of Losses:

Input diode bridge (BR1):

$$P_{DIN} = I_{ACRMS} \cdot V_F \cdot 2 \quad (\text{Eq 45}) \quad P_{DIN} = 1,1A \cdot 1V \cdot 2 = 2,2W$$

Calculation of copper resistance R_{Cu} :

Copper resistivity p_{100} @ 100°C = 0,0172Ωmm²/m

$$R_{PCu} = \frac{l_N \cdot N_P \cdot p_{100}}{A_p} \quad (\text{Eq 46}) \quad R_{PCu} = \frac{0,0644m \cdot 46 \cdot 17,2m\Omega mm^2 / m}{0,46mm^2} = 277,1m\Omega$$

$$R_{SCu} = \frac{0,0644m \cdot 7 \cdot 17,2m\Omega mm^2 / m}{2,10mm^2} = 6,6m\Omega$$

Calculation of copper losses (TR1):

$$P_{PCu} = I_{LPK}^2 \cdot D_{MAX} \cdot \frac{1}{3} \cdot R_{PCu} \quad (\text{Eq 47}) \quad P_{PCu} = (2,33A)^2 \cdot 0,53 \cdot \frac{1}{3} \cdot 277,1m\Omega = 225,7mW$$

$$P_{SCu} = I_{SPK}^2 \cdot D'_{MAX} \cdot \frac{1}{3} \cdot R_{SCu} \quad P_{SCu} = (15,3A)^2 \cdot 0,47 \cdot \frac{1}{3} \cdot 2,01m\Omega = 227,4mW$$

$$P_{Cu} = 225,7mW + 227,4mW = 453,1mW$$

Output rectifier diode (D1):

$$P_{DDIODE} = I_{SPK} \cdot \sqrt{\frac{D'_{max}}{3}} \cdot V_{FDDIODE} \quad (\text{Eq 48}) \quad P_{DDIODE} = 15,3A \cdot \sqrt{\frac{0,47}{3}} \cdot 0,8V = 5W$$

COOLMOS TRANSISTOR:

ICE2A365 $C_{O(er)} = 30\text{pF}$

Calculated @ $V_{DCmin} = 100\text{V}$

$C_O \approx 80\text{pF}$ ($C_O = C_{O(er)} + C_{Extern}$)

$R_{DS(on)} = 1,1\Omega$ (@ 125°C)

Switching losses:

(see also ICE2AXXX Data Sheet)

$$P_{SON} = \frac{1}{2} \cdot C_O \cdot V_{DCmin}^2 \cdot f \quad (\text{Eq 49})$$

$$P_{SON} = \frac{1}{2} \cdot 80\text{pF} \cdot 100\text{V}^2 \cdot 100 \cdot 10^3\text{Hz} = 40\text{mW}$$

Conduction losses:

$$P_D = \frac{1}{3} \cdot R_{DS(on)} \cdot I_{LPK}^2 \cdot D_{max} \quad (\text{Eq 50})$$

$$P_D = \frac{1}{3} \cdot 1\Omega \cdot (2,33\text{A})^2 \cdot 0,53 = 0,95\text{W}$$

Summary of Losses:

$$P_{Losses} = P_{SON} + P_D \quad (\text{Eq 51})$$

$$P_{Losses} = 40\text{mW} + 950\text{mW} = 0,99\text{W}$$

Thermal Calculation:

Table of typical thermal Resistance [$\frac{K}{W}$]:

Heatsink	DIP8	DIP7	TO220
No	90	96	74
3 cm ²	64	72	
6 cm ²	56	65	

$$dT = P_{Losses} \cdot R_{th} \quad (\text{Eq 52})$$

$$dT = 0,99\text{W} \cdot 56 \frac{K}{W} = 55,4\text{K}$$

$$T_j = dT + T_a \quad (\text{Eq 53})$$

$$T_j = 55,4\text{K} + 50^\circ\text{C} = 115,4^\circ\text{C}$$

Regulation Loop:

Reference: TL431 (IC2)

$V_{REF} = 2,5V$

$I_{KAmin} = 1mA$

Optocoupler: SFH617-3 (IC1)

$G_c = 1 \dots 2 \equiv CTR 100\% \dots 200\%$

$V_{FD} = 1,2V$

$I_{Fmax} = 20mA$ (maximum current limit)

Primary side:

Feedback voltage:

Values from **ICE2AXXX** datasheet

$V_{Ref int} = 6,5V$ typ.

$V_{FBmax} = 4,5V$

$A_v = 3,65$

$R_{FB} = 3,7k$ typ.

$$I_{FBmax} = \frac{V_{Ref int}}{R_{FB}} \quad (Eq 54)$$

$$I_{FBmin} = \frac{V_{Ref int} - V_{FBmax}}{R_{FB}} \quad (Eq 55)$$

Secondary side:

$$R_1 = R_2 \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \quad (Eq 56)$$

the value of R2 can be fixed at 4,3k

$$R_3 \geq \frac{(V_{OUT} - (V_{FD} + V_{REF}))}{I_{Fmax}} \quad (Eq 57)$$

$$R_4 \leq \frac{V_{FD} + \left(R_3 \cdot \frac{I_{FBmin}}{G_c} \right)}{I_{KAmin}} \quad (Eq 58)$$

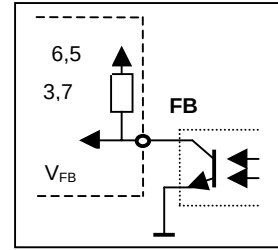


Fig. 13

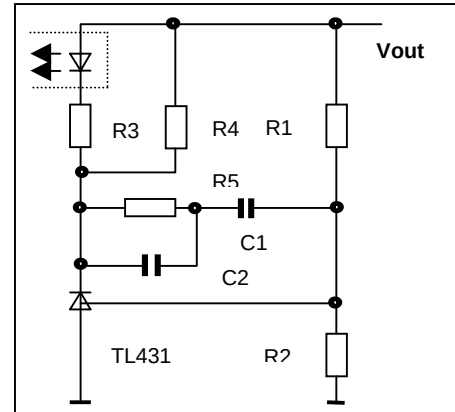


Fig. 14

$$I_{FBmax} = \frac{6,5V}{3,7k\Omega} = 1,76mA$$

$$I_{FBmin} = \frac{6,5V - 4,6V}{3,7k\Omega} = 0,5mA$$

$$R_1 = 4,3k \cdot \left(\frac{16V}{2,5V} - 1 \right) = 23,22k$$

$$R_3 \geq \frac{(16V - (1,2V + 2,5V))}{20mA} = 0,74k \approx 0,75k$$

$$R_4 \leq \frac{1,2V + 0,75k \cdot \left(\frac{0,5mA}{1} \right)}{1mA} = 1,58k \approx 1,5k$$

Regulation Loop Elements:

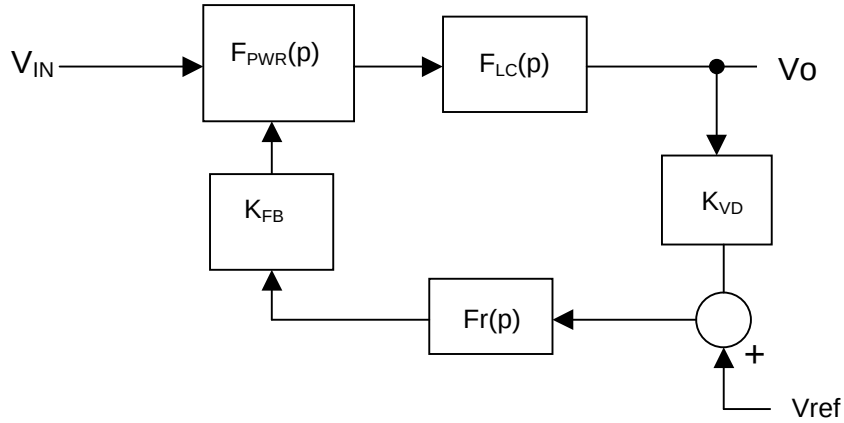


Fig. 15

Transfer Characteristics of Regulation Loop Elements:

$$K_{FB} = \frac{G_C \cdot 3k7}{R3} \quad (\text{Eq 59}) \quad \text{Feedback}$$

$$K_{VD} = \frac{R2}{R1 + R2} = \frac{V_{REF}}{V_{OUT}} \quad (\text{Eq 60}) \quad \text{VoltageDivider}$$

$$F_{PWR}(p) = \frac{1}{Z_{PWM}} \cdot \sqrt{\frac{R_L \cdot L_P \cdot f \cdot \eta}{2}} \cdot \left(\frac{(1 + p \cdot R_{ESR} \cdot C_5)}{\left(1 + p \cdot \left(\frac{R_L}{2} + R_{ESR} \right) \cdot C_5 \right)} \right) \quad (\text{Eq 61}) \quad \text{Powerstage}$$

$$Z_{PWM} = \text{Transimpedance } \Delta V_{FB} / \Delta I_D$$

$$F_{LC}(p) = \frac{1 + p \cdot R_{ESR} \cdot C_9}{1 + p \cdot R_{ESR} \cdot C_9 + p^2 \cdot L \cdot C_9} \quad (\text{Eq 62}) \quad \text{Output filter}$$

$$Fr(p) = \frac{1 + p \cdot R5 \cdot (C1 + C2)}{p \cdot \frac{R1 \cdot R2}{R1 + R2} \cdot C1 \cdot (1 + p \cdot R5 \cdot C2)} \quad (\text{Eq 63}) \quad \text{Regulator}$$

Zeros and Poles of transfer characteristics:

Poles of powerstage @ min. and max. load:

$$R_{LH} = \frac{V_{OUT}^2}{P_{OUT \max}} = \frac{16V^2}{54W} = 4,9\Omega \quad (\text{Eq 64}) \quad R_{LL} = \frac{V_{OUT}^2}{P_{OUT \min}} = \frac{16V^2}{0,5W} = 512\Omega \quad (\text{Eq 65})$$

$$f_{OH} = \frac{1}{\pi \cdot R_{LH} \cdot C5} \quad f_{OH} = \frac{1}{\pi \cdot 4,9\Omega \cdot 2000\mu F} = 31,1Hz \quad (\text{Eq 66})$$

$$f_{OL} = \frac{1}{\pi \cdot R_{LL} \cdot C5} \quad f_{OL} = \frac{1}{\pi \cdot 512\Omega \cdot 2000\mu F} = 0,31Hz \quad (\text{Eq 67})$$

We use the gain (G_C) of the optocoupler stage K_{FB} and the voltage divider K_{VD} as a constant.

$$K_{FB} = \frac{G_C \cdot 3k7}{R3} \quad K_{FB} = 4,9 \quad G_{FB} = 13,9db$$

$$K_{VD} = \frac{R2}{R1 + R2} = \frac{V_{REF}}{V_{OUT}} \quad K_{VD} = 0,15 \quad G_{VD} = -16,4db$$

With adjustment of the transfer characteristics of the regulator we want to reach equal gain within the operating range and to compensate the pole **fo** of the powerstage $F_{PWR}(\omega)$.

Because of the compensation of the output capacitor's zero (see page 22 Eq35, Eq36) we neglect it as well as the LC-Filter pole.

Consequently the transfer characteristic of the power stage is reduced to a single-pole response.

In order to calculate the gain of the open loop we have to select the cross-over frequency.

We calculate the gain of the Power-Stage with max. output power at the selected cross-over frequency

fg = 3kHz:

Calculation of transient impedance Z_{PWM} of ICE2AXXX

The transient impedance defines the direct relationship between the level of the peak current and the feedback pin voltage. It is required for the calculation of the power stage amplification.

PWM-Op gain $-A_v = 3,65$ (according to datasheet)

$$Z_{PWM} = \frac{\Delta V_{FB}}{\Delta I_{pk}} = A_v \cdot \frac{R_{sense}}{V_{csth}} \quad (\text{Eq 68})$$

$$Z_{PWM} = \frac{\Delta V_{FB}}{\Delta I_{pk}} = 3,65 \cdot \frac{0,43\Omega}{1,00V} = 1,57 \frac{V}{A}$$

Gain @ crossover frequency:

$$|F_{PWR}(fg)| = \frac{1}{Z_{PWM}} \cdot \sqrt{\frac{R_L \cdot L_p \cdot f \cdot \eta}{2}} \cdot \left(\frac{1}{\sqrt{1 + \left(\frac{fg}{fo}\right)^2}} \right) \quad (\text{Eq 69})$$

$$|F_{PWR}(3kHz)| = \frac{1}{1,7} \cdot \sqrt{\frac{5,1R \cdot 235\mu H \cdot 100kHz \cdot 0,8}{2}} \cdot \left(\frac{1}{\sqrt{1 + \left(\frac{3000}{31,1}\right)^2}} \right) = 0,05$$

$$G_{PWR}(3kHz) = -26,2db$$

Transfer characteristics:

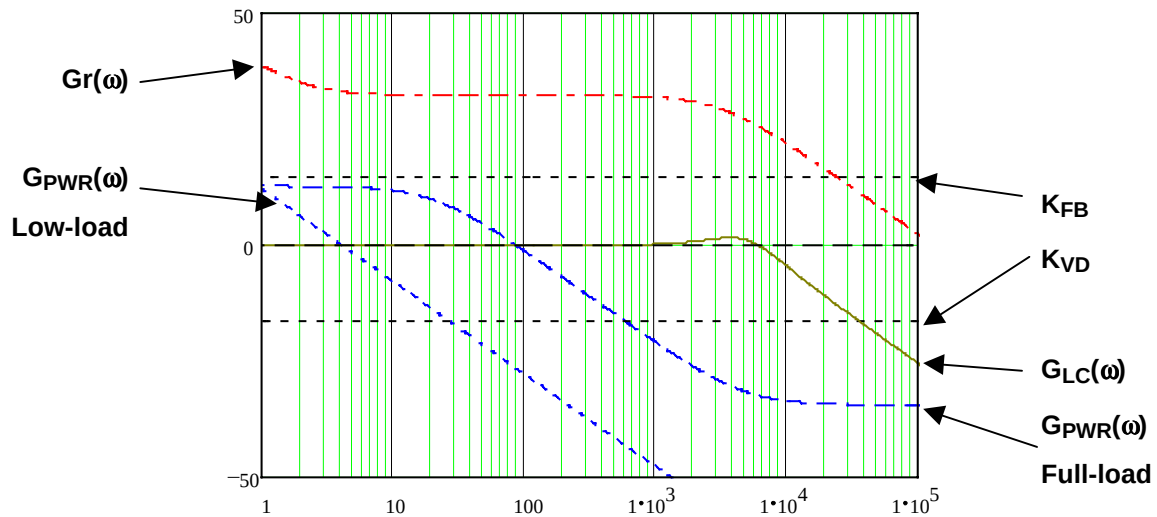


Fig. 16

At the crossover frequency (f_g) we calculate the open loop gain:

$$G_{ol}(\omega) = G_s(\omega) + G_r(\omega) = 0.$$

With the equations for the transfer characteristics we calculate the gain of the regulation loop @ f_g .

For the gain of the regulation loop we calculate:

$$G_s = G_{FB} + G_{PWR} + G_{VD} = 13,9\text{db} - 26,2\text{db} - 16,4\text{db}$$

$$G_s = -28,7\text{db}$$

We calculate the separate components of the regulator:

$$G_s(\omega) + G_r(\omega) = 0 \quad G_r = 0 - (-28,7\text{db}) = \mathbf{28,7\text{db}}$$

$$Fr(p) = \frac{1 + p \cdot R5 \cdot (C1 + C2)}{p \cdot \frac{R1 \cdot R2}{R1 + R2} \cdot C1 \cdot (1 + p \cdot R5 \cdot C2)}$$

$$Gr = 20 \cdot \log \frac{R5 \cdot (R1 + R2)}{R1 \cdot R2}$$

$$R5 = 10^{\frac{Gr}{20}} \cdot \frac{R1 \cdot R2}{R1 + R2}$$

$$R5 = 10^{\frac{32,2}{20}} \cdot 3,65k = 99,15k \approx \mathbf{100k} \quad (\text{Eq 70})$$

$$fp = \frac{1}{2 \cdot \pi \cdot R5 \cdot C2}$$

$$C2 = \frac{1}{2 \cdot \pi \cdot R5 \cdot fg}$$

$$C2 = \frac{1}{2 \cdot \pi \cdot 100k \cdot 3kHz} = 530pF \approx \mathbf{560pF} \quad (\text{Eq 71})$$

In order to have enough phase margin @ low load condition we select the zero frequency of the compensation network to be at the middle between the min. and max. load poles of the power stage.

$$f_{om} = f_{oh} \cdot 10^{0,5 \cdot \log \frac{f_{ol}}{f_{oh}}}$$

$$f_{om} = 31,1Hz \cdot 10^{0,5 \cdot \log \frac{0,15}{31,1}} = 3,2Hz$$

$$fz = \frac{1}{2 \cdot \pi \cdot R5 \cdot (C1 + C2)}$$

$$C1 = \frac{1}{2 \cdot \pi \cdot R5 \cdot f_{om}} - C2$$

$$C1 = \frac{1}{2 \cdot \pi \cdot 100k \cdot 3,2Hz} - 560pF = 492nF \approx \mathbf{470nF} \quad (\text{Eq 72})$$

Open Loop Gain

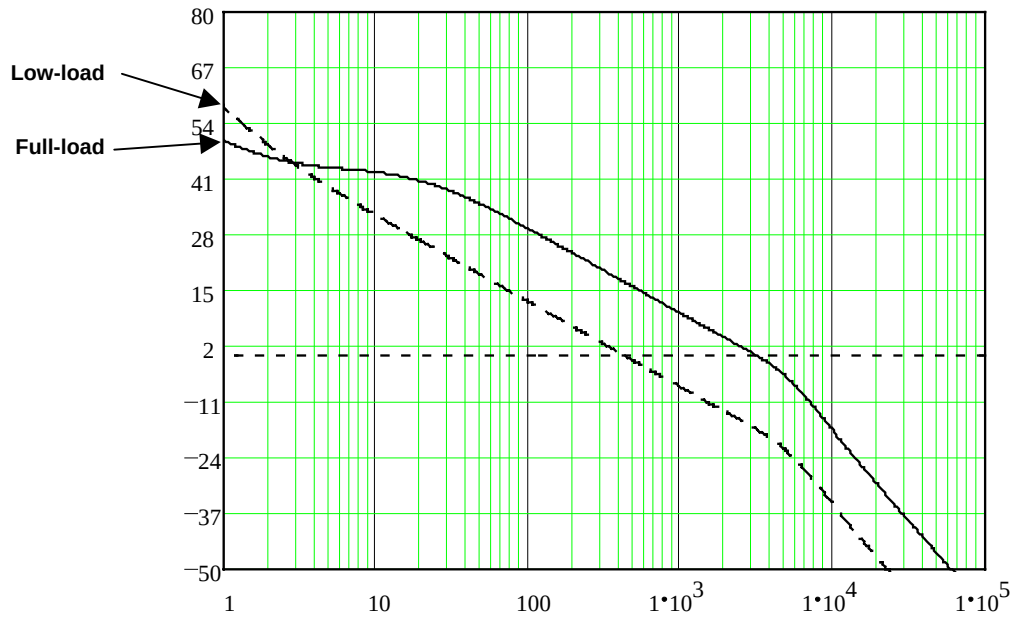


Fig. 17

Open Loop Phase

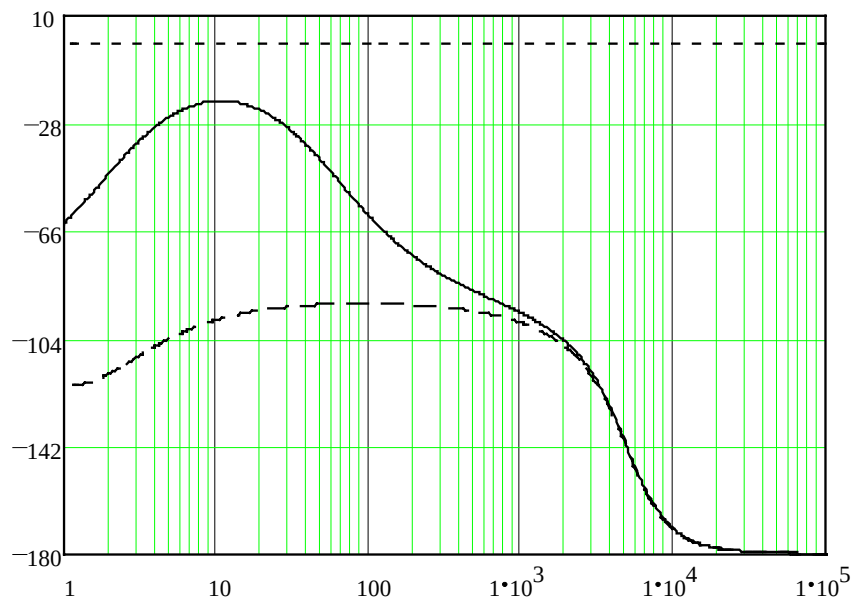


Fig. 18

Continuous Conduction Mode (CCM)

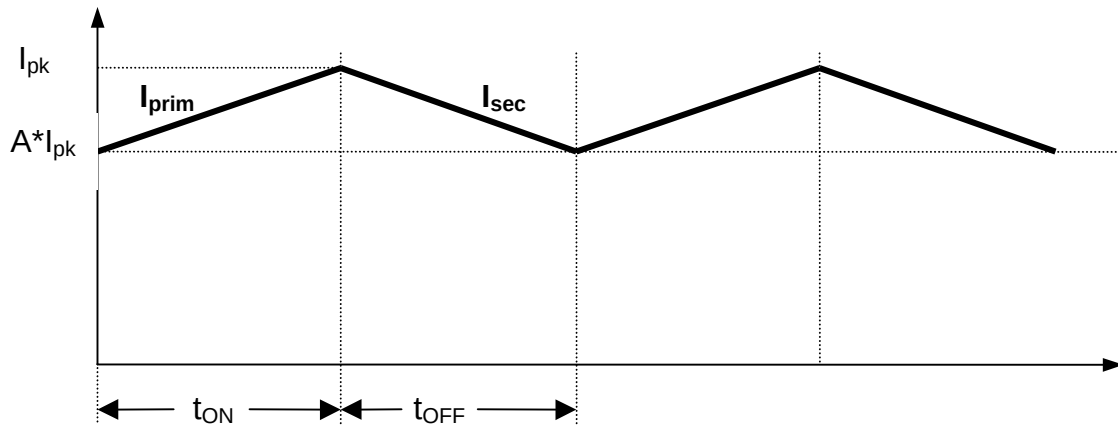


Fig. 19

Transformer calculation:

The transformer is calculated in such a way that DCM operation is just barely reached ($A=0$) at minimum output power P_{Omin} .

$$P_{Omin} = 2W$$

$$P_{Omax} = 10W$$

$$D_{max} = 0,6$$

$$p = \frac{P_{Omax}}{P_{Omin}}$$

$$I_{pk} = \frac{P_{Omin} + P_{Omax}}{D_{max} \cdot V_{dcmin} \cdot \eta}$$

$$L_p = \frac{P_{Omax} \cdot (p+1)^2 \cdot D_{max}}{I_{pk}^2 \cdot f \cdot p}$$

$$p = \frac{10W}{2W} = 5$$

$$I_{pk} = \frac{2W + 10W}{0,6 \cdot 100V \cdot 0,8} = 0,25A$$

$$L_p = \frac{10W \cdot (5+1)^2 \cdot 0,6}{0,25^2 \cdot 100kHz \cdot 5} = 6,91mH$$

Slope Compensation

Slope compensation is necessary for stable regulator operation in **Continuous Conduction Mode (CCM)**, up to and beyond a duty cycle of 0.5 (see also [4]).

An simple method of slope compensation using the components R19, C17 and C18 is illustrated in the circuit diagram on page 3 .

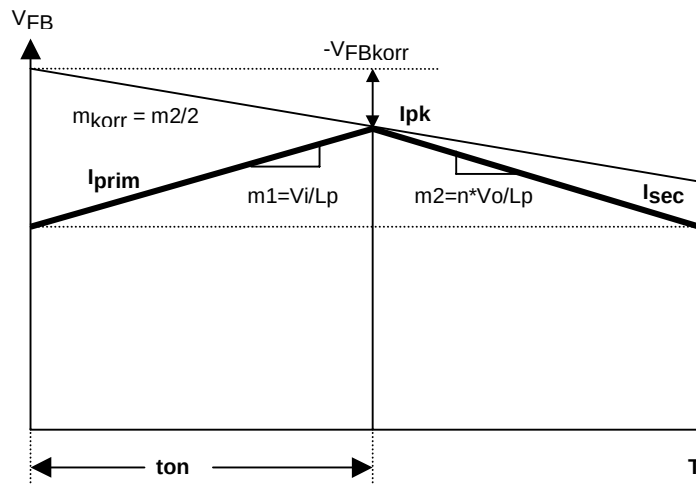


Fig. 20

$$V_R = n \cdot V_o \quad n = \frac{n_p}{n_s}$$

$$m2 = \frac{n \cdot V_o}{L_p} = \frac{V_R}{L_p} \quad m_{korr} = \frac{m2}{2} = \frac{V_R}{2 \cdot L_p}$$

For duty cycle = 0,5 applies:

$$m_{korr} = \frac{V_{FBkorr}}{5\mu s} \quad V_{FBkorr} = \left(\frac{V_R \cdot 5\mu s}{2 \cdot L_p} \right) \cdot Z_{PWM}$$

C_{Comp} (C17) is selected at 10nF.

C18 is selected at 100nF.

R_{Comp} (R19):

$$R_{Comp} = - \frac{t}{\ln \left(1 - \frac{V_{FBkorr}}{V_{CC}} \right) \cdot C_{Comp}}$$

Transformer Construction

The winding topology has a considerable influence on the performance and reliability of the transformer.

In order to reduce leakage inductance and proximity to acceptable limits, the use of a sandwich construction is recommended.

In order to meet international safety requirements a transformer for Off - Line power supply must have adequate insulation between primary and secondary windings.

This can be achieved by using a margin-wound construction or by using triple insulated wire for the secondary winding.

The creepage distance for the universal input voltage range is typically 8mm. This results in a minimum margin width (as a half of the creepage distance) of 4mm. Additionally the necessary insulation between primary and secondary winding is provided using three layers of basic insulation tape.

Example of winding topology for margin wound transformers:

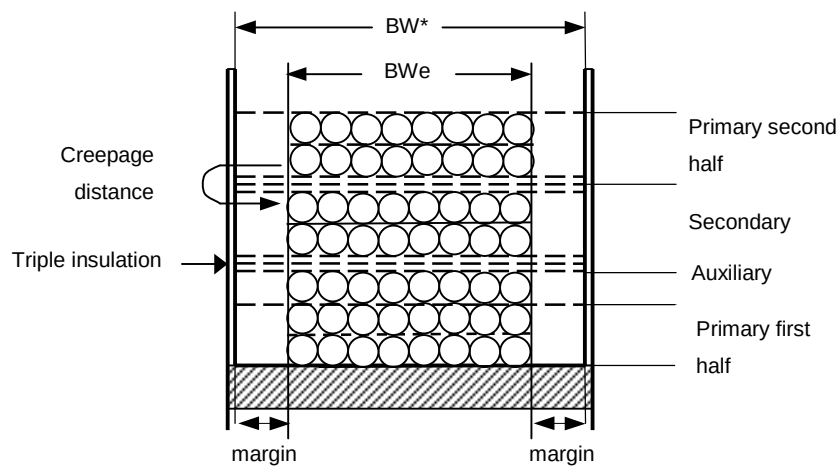


Fig. 21

Example of winding topology with triple insulated wire for secondary winding:

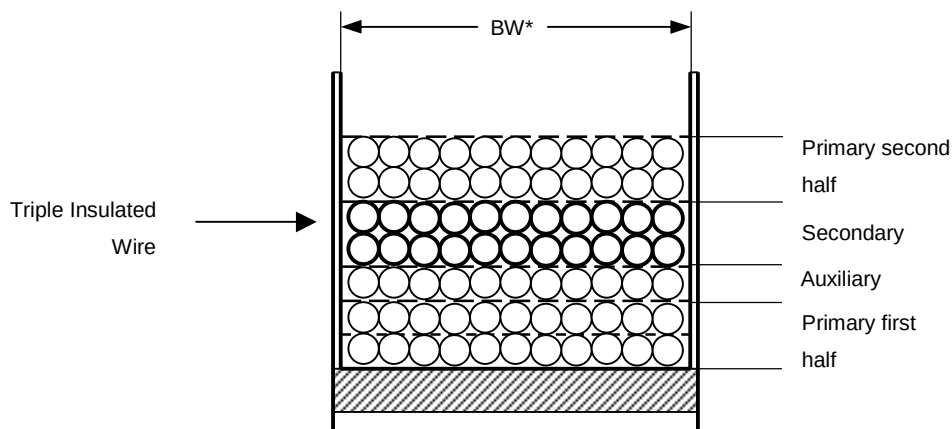


Fig. 22

BW^* : value from bobbin datasheet

Layout Recommendation:

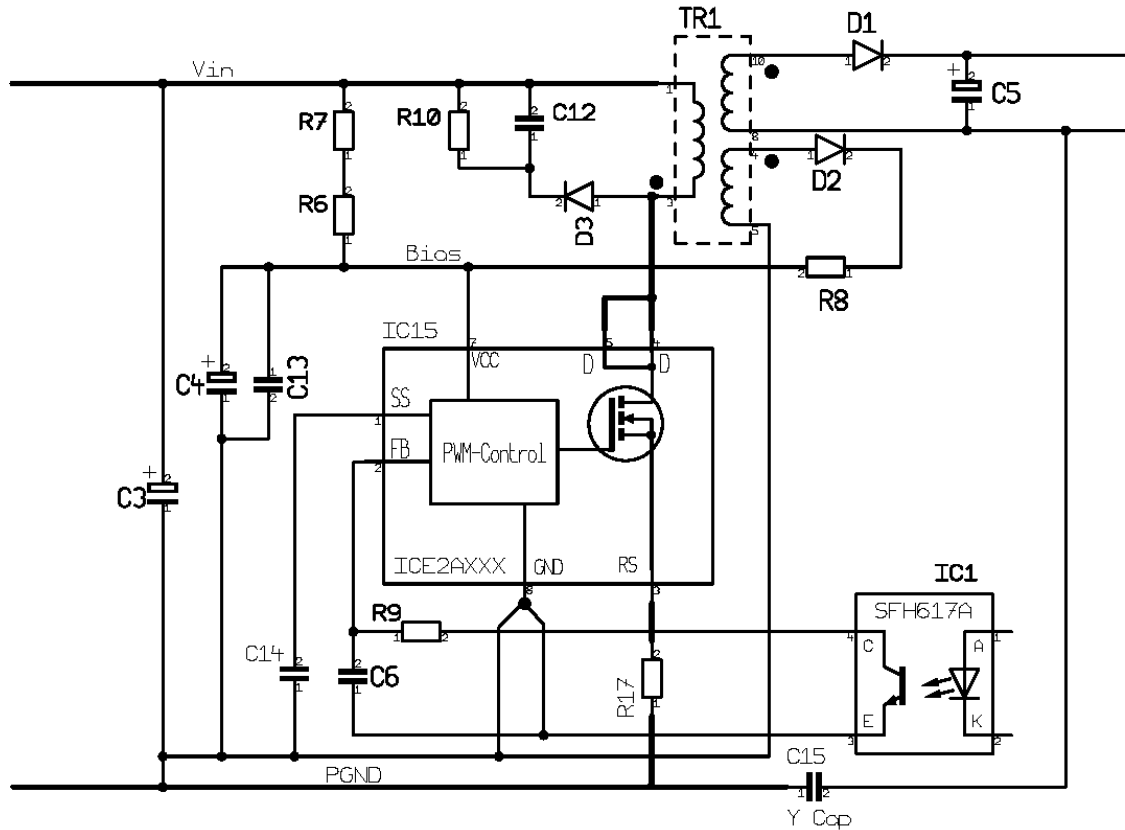


Fig. 23

In order to avoid crosstalk on the board between power and signal path we have to use care regarding the track layout when designing the PCB.

The power path (see Fig. 23) has to be as short as possible and needs to be separated from the VCC Path and the feedback path. All GND paths have to be connected together at pin 8 (star ground) of ICE2AXX.

CoolSET Table

DEVICE	Package	Current A	Rdson Ω	Pout @ 190Vacin Ta=75°C / Tj = 125°C	Pout @ 85Vacin Ta=75°C / Tj = 125°C	Heatsink	Frequency KHz
V_{DS}=650V							
ICE2A0565	DIP8	0.5	6.0	23	13	6 cm ²	100
ICE2A0565Z	DIP7	0.5	6.0	21	12	6 cm ²	100
ICE2A165	DIP8	1.0	3.0	31	18	6 cm ²	100
ICE2B165	DIP8	1.0	3.0	31	18	6 cm ²	67
ICE2A265	DIP8	2.0	0.9	52	32	6 cm ²	100
ICE2B265	DIP8	2.0	0.9	52	32	6 cm ²	67
ICE2A365	DIP8	3.0	0.45	67	45	6 cm ²	100
ICE2B365	DIP8	3.0	0.45	73	45	6 cm ²	67
ICE2A765P	TO220	7.0	0.5	240	130	2.7 k/W	100
ICE2B765P	TO220	7.0	0.5	240	130	2.7 k/W	67
V_{DS}=800V							
ICE2A180	DIP8	1.0	3.0	31	18	6 cm ²	100
ICE2A180Z	DIP7	1.0	3.0	29	17	6 cm ²	100
ICE2A280	DIP8	2.0	0.8	54	34	6 cm ²	100
ICE2A280Z	DIP7	2.0	0.8	50	31	6 cm ²	100

Output Power Notes:

The output power was created using the equations of this application note (see „Calculation of Losses“ on page 27). It shows the maximum practical continuous power @ Ta = 75 °C and Tj = 125 °C with the recommended heatsink as a copper area on PCB for DIP7 / 8 and PDSO14 packages.

Summary of used Nomenclature

B_{max}	Magnetic Inductance	P_{SON}	Switching losses of CoolMOS Transistor (On – Operation)
BW	Bobbin Width	R_{Cu}	Copper Resistor (Transformer)
BWe	Effective Bobbin Width	$R_{DS(on)}$	Resistance of switching CoolMOS Transistor (On – Operation)
C_{IN}	Capacitance of Bulk Capacitor	R_L	Load – Resistance
C_{OUT}	Output Capacitance	R_{LH}	Maximum Load
C_{OSS}	Output Capacitance of CoolMOS	R_{LL}	Minimum Load (defined by Designer)
C_{Extern}	Output Capacitance of external Components	R_{FB}	Internal Feedback Resistor (CoolSET)
C_{Clamp}	Capacitance of Clamping – Capacitor	R_{PCu}	Copper Resistor of primary Inductance
C_{VCC}	Capacitance of VCC – Capacitor	R_{SCu}	Copper Resistor of secondary Inductance
D	Duty Cycle	R_{clamp}	Clamping Resistor
D_{max}	Maximum Duty Cycle	R_{Start}	Start up Resistor
f	Operating Frequency of CoolSET (f = 100kHz)	T	Time of one Period
f_{AC}	Line Frequency (Germany $F_{AC} = 50Hz$)	T_D	Discharging Time of Input Capacitor C3
f_g	Crossover Frequency	t_{ON}	On Time (CoolMOS)
f_{Cu}	Copper Space Factor (0,2 ... 0,4)	t_{OFF}	Off Time (CoolMOS)
f_{OH}	Frequency Open Loop (High)	t_r	Rising Time (Voltage)
f_{Om}	Frequency Open Loop (middle)	t_{start}	Start up Time
f_{OL}	Frequency Open Loop (Low)	$V_{AC min}$	Minimal AC Input Voltage
f_{ZCOUT}	Zero Frequency of output Capacitor	$V_{AC max}$	Maximal AC Input Voltage
G_C	Optocoupler Gain	V_{AUX}	Auxiliary Voltage
I_{FBmax}	Maximum Feedback Current	$V_{(BR)DSS}$	Drain Source Breakdown Voltage
I_{FBmin}	Minimum Feedback Current	$V_{CC(on)}$	Turn On Threshold for CoolSET @ Vcc - Pin
I_{Fmax}	Maximum Current (Optocoupler)	$V_{DC IN}$	DC Input Voltage
I_{KAmin}	Minimum Current (TL431)	$V_{DC IN max}$	Maximum DC Input Voltage
I_{LoadC}	VCC – Capacitor Load – Current	$V_{DC IN min}$	Minimum DC Input Voltage
I_{LPK}	Peak Current through the primary Inductance	$V_{DC max PK}$	Maximum DC Input Voltage Peak
I_{ACRMS}	Root Mean Square Current through the primary Inductance	$V_{DC min PK}$	Minimum DC Input Voltage Peak
$I_{ACRMS Rectifier}$	Root Mean Square Current through the Bridge Rectifier	$V_{DC min}$	Minimum DC Input Voltage @ maximum load
I_{PRI}	Primary Current @ time t	V_{DDIODE}	Reverse Voltage rectifier Diode (secondary side)
I_{SEC}	Secondary Current @ time t	V_{FBmax}	Maximum Feedback Voltage (CoolSET)
I_{SPK}	Peak Current through the secondary diode	V_{FDIODE}	Output Diode Forward Voltage
I_{SRMS}	RMS Current through the secondary diode	V_{FD}	Forward Diode Voltage (Optocoupler)
$I_{VCC1 (IC)}$	Maximum quiescent Current of CoolSET (Control IC)	V_{OUT}	Output Voltage (secondary Side)
L_{OUT}	Inductance output Filter	$V_{OUT Ripple}$	Output Ripple Voltage (secondary Side)
L_P	Primary Inductance	V_R	Reflected Voltage (from secondary side to primary side)
L_{LK}	Leakage Inductance	V_{RDiode}	Reverse Voltage Diode
M	Margin (of Transformer)	V_{Refint}	Internal Reference Voltage (CoolSET)
n_{CP}	Number of Clock Periods	V_{REF}	Reference Voltage TL431
n_{PCOUT}	Number of parallel output Capacitors	V_{Ripple}	DC Ripple Voltage (on primary Side)
N_P	Number of primary Turns	V_{SEC}	Voltage on Sekondary Inductor
N_S	Number of secondary Turns	V_{Clamp}	Maximum Voltage overshoot @ clamping network
N_{AUX}	Number of auxiliary Turns	W_{IN}	Discharging Energie Input Capacitor
P_{Cu}	Power losses of Copper Resistor	Z_{PWM}	Transimpedanz
P_D	Conduction losses		
P_{DIN}	Power losses input Diode		
P_{DDIODE}	Power losses rectifier Diode (secondary side)		
$P_{IN MAX}$	Maximum Input Power		
$P_{OUT max}$	Maximum Output Power		
$P_{OUT min}$	Minimum Output Power		
P_{PCu}	Power losses of Copper Resistor (primary Inductance)		
P_{SCu}	Power losses of Copper Resistor (secondary Inductance)		
P_{SOFF}	Switching losses of CoolMOS Transistor (Off – Operation)		

References

- [1] **Keith Billings,**
Switch Mode Power Supply Handbook
- [2] **Ralph E. Tarter,**
Solid-State Power Conversion Handbook
- [3] **R. D. Middlebrook and Slobodan Cuk,**
Advances in Switched-Mode Power Conversion
- [4] **Herfurth Michael,**
Ansteuerschaltungen für getaktete Stromversorgungen mit Erstellung eines linearisierten Signalfußplans zur Dimensionierung der Regelung
- [5] **Herfurth Michael,**
Topologie, Übertragungsverhalten und Dimensionierung häufig eingesetzter Regelverstärker
- [6] **Infineon Technologies, Datasheet,**
CoolSET-II
Off – Line SMPS Current Mode Controller with 650V/800V CoolMOS on Board,
- [7] **Robert W. Erickson,**
Fundamentals of Power Electronics

Revision History		
Application Note AN-SMPS-ICE2xXXX-1		
Actual Release: V1.2 Date:05.02.2002		Previous Release: V1.0
Page of actual Rel.	Page of prev. Rel.	Subjects changed since last release
44	-----	Second Issue
40	-----	CoolSET Table Update

For questions on technology, delivery and prices please contact the Infineon Technologies Offices in Germany or the Infineon Technologies Companies and Representatives worldwide: see the address list on the last page or our webpage at <http://www.infineon.com>

CoolMOS™ and **CoolSET™** are trademarks of Infineon Technologies AG.

We listen to Your Comments

Any information within this dokument that you feel is wrong, unclear or missing at all?

Your feedback will help us to continuously improve the quality of this dokument.

Please send your proposal (including a reference to this dokument) to:

mcdoku.comment@infineon.com



Edition 2001-03-01

Published by Infineon Technologies AG,
St.-Martin-Strasse 53,
D-81541 München

© Infineon Technologies AG 2000.
All Rights Reserved.

Attention please!

The information herein is given to describe certain components and shall not be considered as warranted characteristics.

Terms of delivery and rights to technical change reserved.

We hereby disclaim any and all warranties, including but not limited to warranties of non-infringement, regarding circuits, descriptions and charts stated herein.

Infineon Technologies is an approved CECC manufacturer.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office in Germany or our Infineon Technologies Representatives worldwide (see address list).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Infineon Technologies AG sales offices worldwide – partly represented by Siemens AG

A Siemens AG Österreich Erdberger Lände 26 A-1031 Wien T (+43)1-17 07-3 56 11 Fax (+43)1-17 07-5 59 73 AUS Siemens Ltd. 885 Mountain Highway Bayswater, Victoria 3153 T (+61)3-97 21 21 11 Fax (+61)3-97 21 72 75 B Siemens Electronic Components Benelux Charleroisesteenweg 116/ Chaussée de Charleroi 116 B-1060 Brussel/Bruxelles T (+32)2-5 36 69 05 Fax (+32)2-5 36 28 57 Email: components@siemens.nl BR Siemens Ltda. Semicondutores Avenida Mutinga, 3800-Pirituba 05110-901 São Paulo-SP T (+55)11-39 08 25 64 Fax (+55)11-39 08 27 28 CDN Infineon Technologies Corporation 320 March Road, Suite 604 Canada, Ontario K2K 2E2 T (+1)6 13-5 91 63 86 Fax (+1)6 13-5 91 63 89 CH Siemens Schweiz AG Bauelemente Freilagerstrasse 40 CH-8047 Zürich T (+41)1-4 953065 Fax (+41)1-4 955050 D Infineon Technologies AG Völklinger Str.2 D-40219 Düsseldorf T (+49)2 11-3 99 29 30 Fax (+49)2 11-3 99 14 81 Infineon Technologies AG Werner-von-Siemens-Platz 1 D-30880 Laatzen (Hannover) T (+49)5 11-8 77 22 22 Fax (+49)5 11-8 77 15 20 Infineon Technologies AG Von-der-Tann-Straße 30 D-90439 Nürnberg T (+49)9 11-6 54 76 99 Fax (+49)9 11-6 54 76 24 Infineon Technologies AG Weissacher Straße 11 D-70499 Stuttgart T (+49)7 11-1 37 33 14 Fax (+49)7 11-1 37 24 48 D Infineon Technologies AG Halbleiter Distribution Richard-Strauss-Straße 76 D-81679 München T (+49)89-92 21 40 86 Fax (+49)89-92 21 20 71 DK Siemens A/S Borupvang 3 DK-2750 Ballerup T (+45)44 77-44 77 Fax (+45)44 77-40 17 E Siemens S.A. Dpto. Componentes Ronda de Europa, 5 E-28760 Tres Cantos-Madrid T (+34)91-5 14 71 51 Fax (+34)91-5 14 70 13	F Infineon Technologies France, 39/47, Bd. Ornano F-93527 Saint-Denis CEDEX2 T (+33)1-49 22 31 00 Fax (+33)1-49 22 28 01 FIN Siemens Components Scandinavia P.O. Box 6 0 FIN-02601 Espoo (Helsinki) T (+3 58)10-5 11 51 51 Fax (+3 58)10-5 11 24 95 Email: scs@components.siemens.se GB Infineon Technologies Siemens House Oldbury GB-Bracknell, Berkshire RG12 8FZ T (+44)13 44-39 66 18 Fax (+44)13 44-39 66 32 H Simacomp Kft. Lajos u.103 H-1036 Budapest T (+36)1-4 57 16 90 Fax (+36)1-4 57 16 92 HK Infineon Technologies Hong Kong Ltd. Suite 302, Level 3, Festival Walk, 80 Tat Chee Avenue, Yam Yat Tsuen, Kowloon Tong Hong Kong T (+8 52)28 32 05 00 Fax (+8 52)28 27 97 62 I Siemens S.A. Semiconductor Sales Via Piero e Alberto Pirelli, 10 I-20126 Milano T (+39)02-66 76 -1 Fax (+39)02-66 76 43 95 IND Siemens Ltd. Components Division No.84 Keonics Electronic City Hosur Road Bangalore 561 229 T (+91)80-8 52 11 22 Fax (+91)80-8 52 11 80 Siemens Ltd. CMP Div, 5th Floor 4A Ring Road, IP Estate New Delhi 110 002 T (+91)11-3 31 99 12 Fax (+91)11-3 31 96 04 Siemens Ltd. CMP Div, 4th Floor 130, Pandurang Budhkar Marg, Worli Mumbai 400 018 T (+91)22-4 96 21 99 Fax (+91)22-4 96 22 01 IRL Siemens Ltd. Electronic Components Division 8, Raglan Road IRL-Dublin 4 T (+3 53)1-2 16 23 42 Fax (+3 53)1-2 16 23 49 IL Nisko Ltd. 2A, Habarzel St. P.O. Box 58151 61580 Tel Aviv -Israel T (+9 72)3 -7 65 73 00 Fax (+9 72)3 -7 65 73 33	J Siemens Components K.K. Talanawa Park Tower 12F & 17F 3-20-14, Higashi-Gotanda, Shinagawa-ku Tokyo T (+81)3-54 49 64 11 Fax (+81)3 -54 49 64 01 MAL Infineon Technologies AG Sdn Bhd Bayan Lepas Free Industrial Zone1 11900 Penang T (+60)4 -6 44 99 75 Fax (+60)4 -6 41 48 72 N Siemens Components Scandinavia Østre Aker vei 24 Postboks 10, Veitvet N-0518 Oslo T (+47)22-63 30 00 Fax (+47)22-68 49 13 Email: scs@components.siemens.se NL Siemens Electronic Components Benelux Postbus 16068 NL-2500 BB Den Haag T (+31)70-3 33 20 65 Fax (+31)70-3 33 28 15 Email: components@siemens.nl NZ Siemens Auckland 300 Great South Road Greenland Auckland T (+64)9-5 20 30 33 Fax (+64)9-5 20 15 56 P Siemens S.A. an Componentes Electronicos R.Irmaos Siemens, 1 Alfragide P-2720-093 Amadora T (+351)1-4 17 85 90 Fax (+351)1-4 17 80 83 PK Siemens Pakistan Engineering Co.Ltd. PO Box 1129, Islamabad 44000 23 West Jinnah Ave Islamabad T (+92)51-21 22 00 Fax (+92)51-21 16 10 PL Siemens SP.z.o.o. ul. Zupnicza 11 PL-03-821 Warszawa T (+48)22-8 70 91 50 Fax (+48)22-8 70 91 59 ROK Siemens Ltd. Asia Tower, 10th Floor 726 Yeoksam-dong, Kang-nam Ku CPO Box 3001 Seoul 135-080 T (+82)2-5 27 77 00 Fax (+82)2-5 27 77 79 RUS INTECH electronics ul. Smolnaya, 24/1203 RUS-125 445 Moskva T (+7)0 95 -4 51 97 37 Fax (+7)0 95 -4 51 86 08 S Siemens Components Scandinavia Österögatan 1, Box 46 S-164 93 Kista T (+46)8-7 03 35 00 Fax (+46)8-7 03 35 01 Email: scs@components.siemens.se	RC Infineon Technologies Asia Pacific Pte.Ltd. Taiwan Branch 10F, No.136 Nan King East Road Section 23, Taipei T (+8 86)2-27 73 66 06 Fax (+8 86)2-27 71 20 76 SGP Infineon Technologies Asia Pacific, Pte.Ltd. 168 Kallang Way Singapore 349 253 T (+65)8 40 06 10 Fax (+65)7 42 62 39 USA Infineon Technologies Corporation 1730 North First Street San Jose, CA 95112 T (+1)4 08-5 01 60 00 Fax (+1)4 08-5 01 24 24 Siemens Components, Inc. Optoelectronics Division 19000 Homestead Road Cupertino, CA 95014 T (+1)4 08-2 57 79 10 Fax (+1)4 08-7 25 34 39 Siemens Components, Inc. Special Products Division 186 Wood Avenue South Iselin, NJ 08830-2770 T (+1)7 32-9 06 43 00 Fax (+1)7 32-6 32 28 30 VRC Infineon Technologies Hong Kong Ltd. Beijing Office Room 2106, Building A Vantone New World Plaza No.2 Fu Cheng Men Wai Da Jie Jie 100037 Beijing T (+86)10 -68 57 90 -06,-07 Fax (+86)10 -68 57 90 08 Infineon Technologies Hong Kong Ltd. Chengdu Office Room14J1, Jinyang Mansion 58 Tudu Street Chengdu, Sichuan Province 610 016 T (+86)28-6 61 54 46 /79 51 Fax (+86)28 -6 61 01 59 Infineon Technologies Hong Kong Ltd. Shanghai Office Room1101, Lucky Target Square No.500 Chengdu Road North Shanghai 200003 T (+86)21-63 6126 18 /19 Fax (+86)21-63 61 11 67 Infineon Technologies Hong Kong Ltd. Shenzhen Office Room 1502, Block A Tian An International Building Renim South Road Shenzhen 518 005 T (+86)7 55 -2 28 91 04 Fax (+86)7 55-2 28 02 17 ZA Siemens Ltd. Components Division P.O.B.3438 Halfway House 1685 T (+27)11-6 52 -27 02 Fax (+27)11-6 52 20 42
--	--	---	--

Mouser Electronics

Authorized Distributor

Click to View Pricing, Inventory, Delivery & Lifecycle Information:

[Infineon:](#)

[ICE2A180ZXKLA1](#)