

AN-1275 Optimizing LMX243x Input Sensitivity Using Simple Matching Techniques

ABSTRACT

The following application report describes how maximum power can be delivered from the voltage controlled oscillator (VCO) output to the FinRF input of a LMX243x frequency synthesizer by means of performing a single element match.

Contents

1	Overview	1
2	Evaluation Methodology	3
3	1.0 Optimizing Sensitivity at 5.0 GHz	3
4	2.0 Optimizing Sensitivity at 6.0 GHz	4
5	3.0 Optimizing Sensitivity at 2.0 GHz	6
6	Summary	7
7	References	8

List of Figures

1	Impedance Matching	2
2	LMX243x UTCSP FinRF Input Impedance	2
3	1.0 pF Shunt Match at 5.0 GHz	3
4	LMX243x UTCSP FinRF Input Impedance With 1.0 pF Shunt Match	4
5	LMX243x UTCSP FinRF Input Sensitivity Improvement at 5.0 GHz	4
6	0.5 pF Shunt Match at 6.0 GHz	5
7	LMX243x UTCSP FinRF Input Impedance With 0.5 pF Shunt Match	5
8	LMX243x UTCSP FinRF Input Sensitivity Improvement at 6.0 GHz	5
9	4.7 nH Series Match at 2.0 GHz	6
10	LMX243x UTCSP FinRF Input Impedance With 4.7 nH Series Match	6
11	LMX243x UTCSP FinRF Input Sensitivity Improvement at 2.0 GHz	7

List of Tables

1	LMX243x UTCSP FinRF Input Impedance Table $V_{CC} = EN = 2.50\text{ V}$, $T_A = +25^\circ\text{C}$	7
---	---	---

1 Overview

Maximum power transfer is achieved by designing a matching network that transforms the FinRF input (load) impedance to an impedance that is equivalent to the VCO output (source) impedance. In most applications, the VCO has an output impedance equivalent to $50\ \Omega$. Furthermore, the trace impedance of the printed circuit board (PCB) is typically designed to be $50\ \Omega$. This means that the matching network should be designed to transform the FinRF input impedance to $50\ \Omega$. [Figure 1](#) demonstrates the principal of impedance matching (transformation). The VCO output is represented as a Thevenin equivalent of a voltage source and a $50\ \Omega$ series resistance.

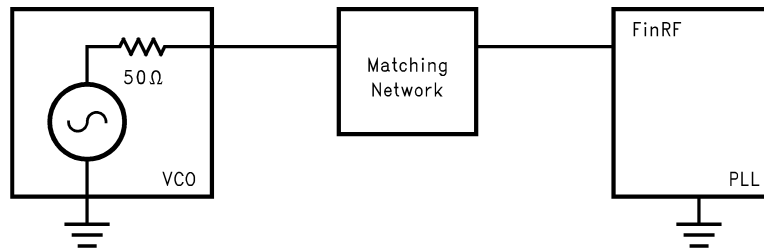


Figure 1. Impedance Matching

A typical plot for the LMX243x UTCSP FinRF input impedance is illustrated in [Figure 2](#). The Smith chart shows that for frequencies less than 3400 MHz, the reactance is primarily dominated by the capacitance from the PCB and CSP package. On the other hand, for frequencies greater than 3400 MHz, the reactance, for the most part, becomes dominated by the internal lead inductance from the package bond wires. It's worth mentioning that the FinRF input impedance is very dependent upon the type of package used.

Ideally, a perfect match is preferred everywhere within the FinRF input's range. This means that the matching network designed should be able to 'tune out' the effects of the package capacitance at the lower frequencies, as well as the effects of the lead inductance at the higher frequencies. In practice however, since the load is comprised of imaginary elements, which are frequency dependent, the perfect match can only occur at one frequency. Therefore, the matching network is only optimized for a particular frequency. In the case of PLLs, this corresponds to the VCO output frequency, f_{FinRF} .

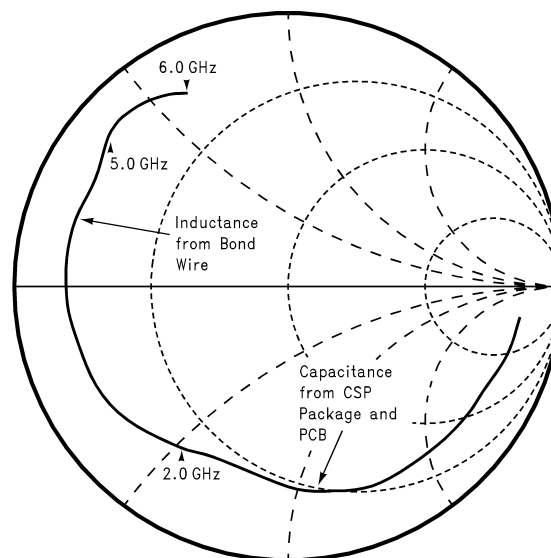


Figure 2. LMX243x UTCSP FinRF Input Impedance

2 Evaluation Methodology

To keep the matching network simple and to demonstrate that indeed an improvement in performance is achieved, a single element match is used. In order to assess the improvement achieved, the device's input sensitivity level is determined before and after the matching network is included. Therefore, an open loop sensitivity test is implemented. The purpose of this test is to measure the acceptable signal level to the FinRF input of the PLL. Outside the acceptable signal range, the feedback divider begins to divide incorrectly and miscount the frequency. Minimum sensitivity is reached when the frequency error of the divided RF input is greater than or equal to 1 Hz.

In most applications, the lower sensitivity limit is of concern because it determines the minimum acceptable signal level that is required to maintain lock. The objective of the matching network, therefore, is to push the lower sensitivity limit downwards. This means that at the particular frequency of interest, the VCO output frequency, the matching network should improve the FinRF input sensitivity.

Furthermore, a good match should also improve the frequency response of the PLL. In most applications, it is desirable to increase the upper frequency limit, push the sensitivity curve further right. In most cases however, as seen with the LMX243x UTCSP, this is difficult to achieve due to internal circuit limitations.

To demonstrate the discussion above, several examples are provided here.

3 1.0 Optimizing Sensitivity at 5.0 GHz

Suppose the requirement is to optimize the performance at 5.0 GHz for an LO to be used in a particular 802.11a WLAN application. According to [Figure 2](#), the FinRF input impedance lies on the upper half of the Smith chart. This means that the FinRF input impedance at 5.0 GHz can be represented by a series combination of a resistor and an inductor. From the [Table 1](#), $Z_{FinRF} = 4.92 + j19.79\Omega$ at 5.0 GHz.

To move closer to 50Ω and to an ideal match, a 1.0 pF shunt capacitor is placed between the VCO output and the FinRF input of the PLL as shown in [Figure 3](#). The closer the impedance gets to 50Ω , the better the sensitivity is. The impedance at 5.0 GHz is then illustrated in [Figure 4](#).

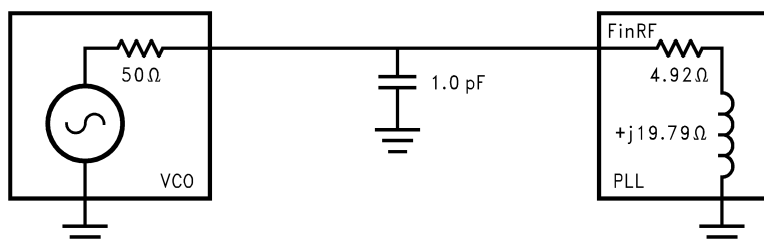


Figure 3. 1.0 pF Shunt Match at 5.0 GHz

The capacitor used should exhibit a self resonance frequency that's higher than the frequency of interest. High Q (low ESR), temperature compensating (NPO) ceramic capacitors are recommended here. Today, it is not too difficult to find 1.0 pF capacitors that have self resonance frequencies well above 5.0 GHz, such as the 600S series capacitors from American Technical Ceramics.

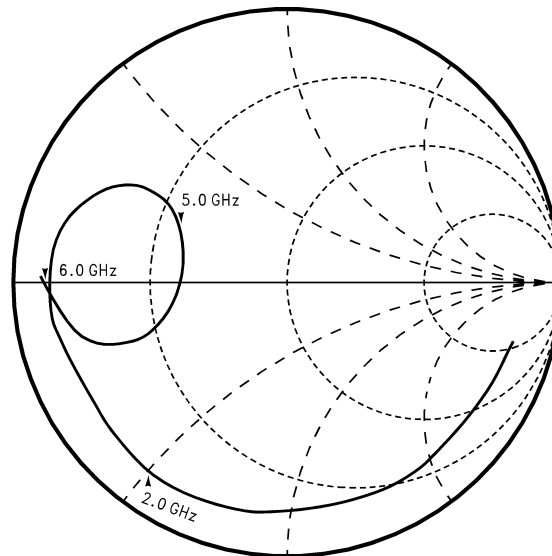


Figure 4. LMX243x UTCSP FinRF Input Impedance With 1.0 pF Shunt Match

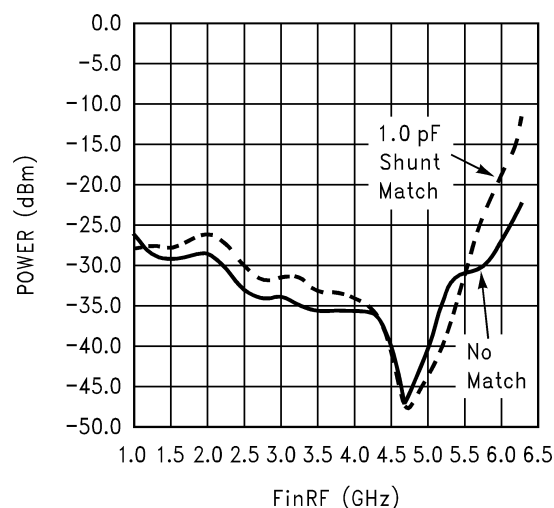


Figure 5. LMX243x UTCSP FinRF Input Sensitivity Improvement at 5.0 GHz

Figure 5 shows that an approximate 3.4 dB improvement in sensitivity is achieved at 5.0 GHz with the addition of the 1.0 pF shunt capacitor. Figure 5 also demonstrates that the sensitivity gets worse at frequencies other than 5.0 GHz. This evaluation is performed under typical conditions, with $V_{CC} = 2.50$ V and $T_A = 25^\circ\text{C}$.

NOTE: A DC blocking capacitor is typically included at the PLL's FinRF input. For all the evaluations performed in this document, the impedance and loss characteristics of the DC blocking capacitor are included in the calibration and removed from any test results.

4 2.0 Optimizing Sensitivity at 6.0 GHz

Now suppose the requirement is to optimize the performance at 6.0 GHz for an LO to be used in a particular cordless phone application. According to Figure 2, the FinRF input impedance again lies on the upper half of the Smith chart. From Table 1, $Z_{FinRF} = 7.11 + j28.00\Omega$ at 6.0 GHz.

This time a 0.5 pF shunt capacitor is placed between the VCO output and the FinRF input of the PLL as shown in Figure 6. This makes the impedance at 6.0 GHz close to 50Ω as illustrated in Figure 7.

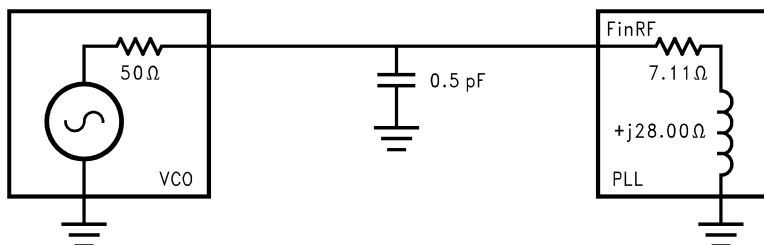


Figure 6. 0.5 pF Shunt Match at 6.0 GHz

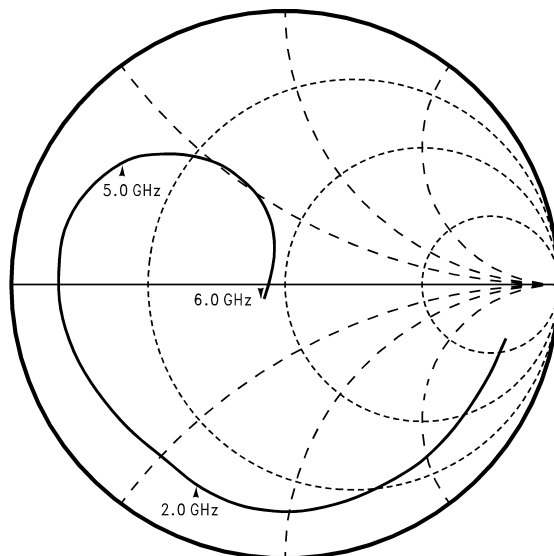


Figure 7. LMX243x UTCSP FinRF Input Impedance With 0.5 pF Shunt Match

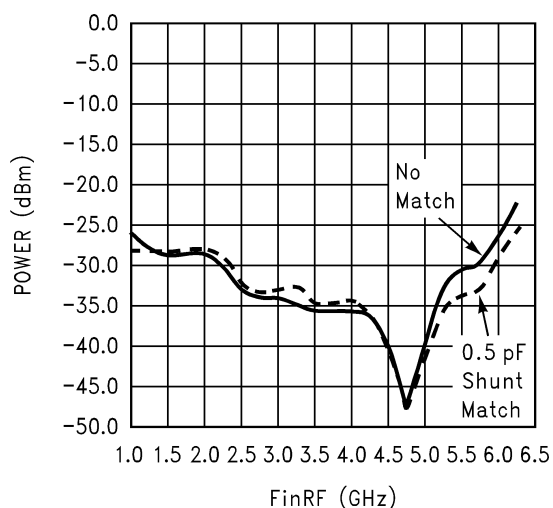


Figure 8. LMX243x UTCSP FinRF Input Sensitivity Improvement at 6.0 GHz

Figure 8 shows that an approximate 3.0 dB improvement in sensitivity is achieved at 6.0 GHz with the addition of the 0.5 pF shunt capacitor. Again, this evaluation is performed under typical conditions, with $V_{CC} = 2.50$ V and $T_A = 25^\circ\text{C}$.

NOTE: The LMX2434 is only guaranteed for operation up to 5.0 GHz. For further information, see the LMX2430/33/34 data sheet.

5 3.0 Optimizing Sensitivity at 2.0 GHz

Now suppose the requirement is to optimize the performance at 2.0 GHz for an LO to be used in a particular US TBQM handset application. Figure 2 now shows that the FinRF input impedance lies on the lower half of the Smith chart. From Table 1, $Z_{\text{FinRF}} = 14.32 - j38.66\Omega$ at 2.0 GHz.

To move closer to 50Ω and to an ideal match, a 4.7 nH series inductor is placed between the VCO output and the FinRF input of the PLL as shown in Figure 9. The impedance is then illustrated in Figure 10.

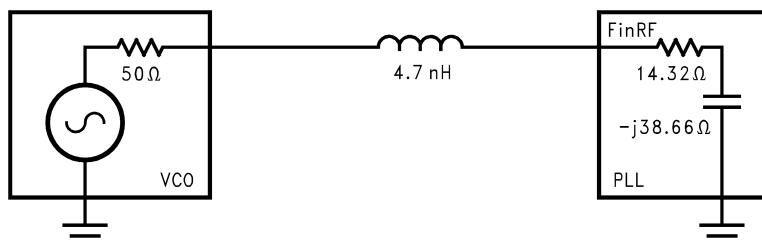


Figure 9. 4.7 nH Series Match at 2.0 GHz

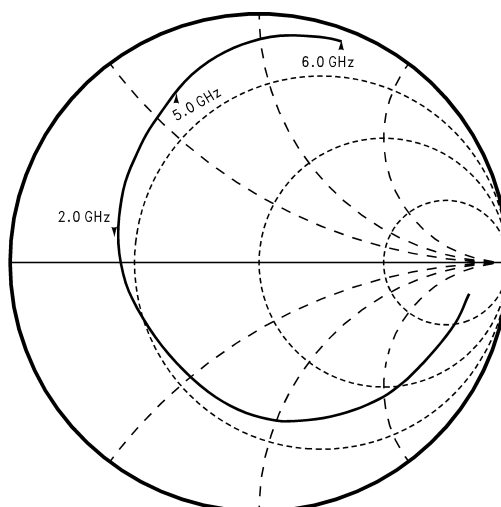


Figure 10. LMX243x UTCSF FinRF Input Impedance With 4.7 nH Series Match

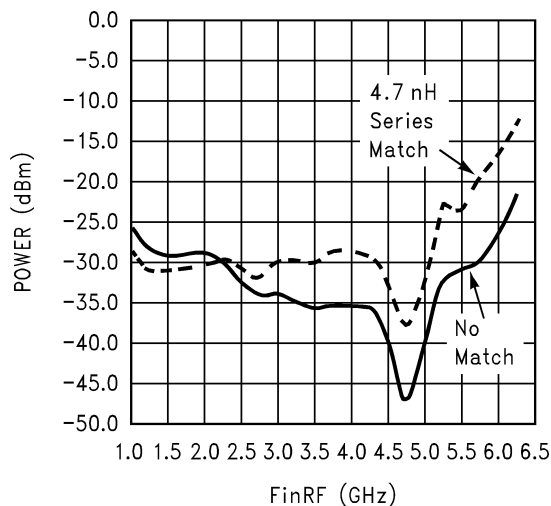


Figure 11. LMX243x UTCSP FinRF Input Sensitivity Improvement at 2.0 GHz

Figure 11 shows that an approximate 2.0 dB improvement in sensitivity is achieved at 2.0 GHz with the addition of the 4.7 nH series inductor. Figure 11 also shows that the sensitivity gets much worse at frequencies other than 2.0 GHz. Similarly, this evaluation is performed under typical conditions, with $V_{CC} = 2.50$ V and $T_A = 25^\circ\text{C}$.

6 Summary

The results shown in this application report reflect conditions using a PCB with optimized grounding around 5.0 GHz. Most PCB designs may not be well grounded at 5.0 GHz and, therefore, may not achieve the sensitivity shown in the graphs above. However, this document demonstrates that a single element match offers a seemingly good solution for today's stringent PCB space and cost reduction requirements with an enhancement in sensitivity performance over a non-matched solution.

Table 1. LMX243x UTCSP FinRF Input Impedance Table $V_{CC} = EN = 2.50$ V, $T_A = +25^\circ\text{C}$

FinRF (MHz)	$ \Gamma $	Angle ($^\circ$)	Re {ZFinRF} (Ω)	Im {ZFinRF} (Ω)	ZFinRF (Ω)
100	0.86	-8.63	334.27	-339.55	476.48
200	0.86	-10.72	265.44	-313.48	410.77
300	0.85	-13.48	202.09	-281.42	346.46
400	0.84	-17.01	150.76	-245.31	287.93
500	0.83	-21.05	112.18	-212.85	240.60
600	0.82	-25.32	85.96	-185.41	204.37
700	0.82	-29.78	67.32	-162.49	175.88
800	0.81	-34.35	54.27	-143.15	153.09
900	0.80	-39.02	44.76	-127.07	134.72
1000	0.80	-43.83	37.32	-113.62	119.59
1100	0.79	-48.76	31.65	-102.07	106.86
1200	0.79	-53.90	27.30	-91.89	95.86
1300	0.78	-59.07	23.84	-82.83	86.19
1400	0.78	-64.41	21.34	-74.84	77.82
1500	0.77	-70.04	19.20	-67.56	70.24
1600	0.76	-75.84	17.46	-60.88	63.33
1700	0.75	-82.06	16.27	-54.72	57.09
1800	0.73	-88.56	15.36	-48.89	51.25
1900	0.72	-95.19	14.90	-43.34	45.83

Table 1. LMX243x UTCSP FinRF Input Impedance Table $V_{CC} = EN = 2.50\text{ V}$, $T_A = +25^\circ\text{C}$ (continued)

FinRF (MHz)	$ \Gamma $	Angle ($^\circ$)	Re {ZFinRF} (Ω)	Im {ZFinRF} (Ω)	ZFinRF (Ω)
2000	0.70	-101.45	14.32	-38.66	41.23
2100	0.68	-107.85	14.10	-34.26	37.05
2200	0.67	-114.12	13.81	-30.35	33.34
2300	0.66	-120.12	13.27	-27.09	30.17
2400	0.66	-126.01	12.50	-24.00	27.06
2500	0.67	-131.82	11.68	-21.22	24.22
2600	0.69	-137.96	10.55	-18.24	21.07
2700	0.71	-144.21	9.53	-15.58	18.26
2800	0.72	-150.25	8.55	-12.92	15.49
2900	0.74	-156.23	7.75	-10.25	12.85
3000	0.75	-161.92	7.22	-7.77	10.61
3100	0.76	-167.18	6.87	-5.48	8.79
3200	0.77	-172.05	6.63	-3.42	7.46
3300	0.77	-177.55	6.40	-1.49	6.57
3400	0.78	179.16	6.18	0.35	6.19
3500	0.79	174.92	5.99	2.18	6.37
3600	0.79	170.77	5.85	3.99	7.08
3700	0.80	166.54	5.74	5.80	8.16
3800	0.80	162.52	5.73	7.56	9.49
3900	0.80	158.74	5.73	9.22	10.86
4000	0.80	155.06	5.68	10.84	12.24
4100	0.80	151.49	5.69	12.38	13.62
4200	0.80	148.28	5.70	13.78	14.91
4300	0.80	146.02	5.73	14.88	15.95
4400	0.80	144.12	5.60	15.84	16.80
4500	0.82	142.31	5.41	16.66	17.52
4600	0.83	140.78	5.29	17.42	18.21
4700	0.83	139.65	5.14	17.95	18.67
4800	0.84	138.75	4.99	18.38	19.05
4900	0.84	137.79	4.84	18.85	19.46
5000	0.84	136.82	4.92	19.79	20.39
5100	0.84	135.77	4.88	18.89	19.51
5200	0.84	134.64	4.99	20.44	21.04
5300	0.84	133.33	5.11	21.16	21.77
5400	0.84	131.68	5.25	21.96	22.58
5500	0.83	129.77	5.43	23.01	23.64
5600	0.83	127.55	5.70	24.16	24.82
5700	0.82	125.41	6.03	25.33	26.04
5800	0.82	123.35	6.42	26.41	27.18
5900	0.81	121.68	6.75	27.30	28.12
6000	0.80	120.42	7.11	28.00	28.89

7 References

1. Bowick, Christopher, *RF Circuit Design*, 1st ed, 1990
2. Pozar, David M., *Microwave and RF Design of Wireless Systems*, 1st ed, 2000
3. Banerjee, Dean, *PLL Performance, Simulation, and Design*, 2nd ed, 2001

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com