

## **AN-2266 LM34902/4 Current Limited Power Switch Evaluation Module**

---

---

---

### **1 Introduction**

With the advent of new handset, tablet, and notebook devices in smaller and smaller footprints, engineers are facing the challenging task of designing next-generation systems that fit into these smaller form factors. Also, consumers are placing more value on the battery life of their portable devices by seeking longer operation time between charges.

One of the standards that has become a “must have” for these devices is the USB port that enables a user to connect various accessories to their device. However, power transfer from a host device to a downstream accessory needs to be carefully managed to avoid inrush current and/or voltage transient events upon connection. The accessory typically sends a handshake signal to indicate that it is ready to accept downstream power transfer. Only then should the device’s CPU or system controller authorize current flow. Well-defined overload protection is also mandated to reliably manage capacitive loads or accessory fault modes.

With nominal 5 nA shutdown and 47  $\mu$ A quiescent supply currents, the LM34902/4 current-limited power switch is ideally suited for such applications. Offered in a tiny 6-bump 1.2 mm x 0.8 mm micro SMD package with 0.6 mm height and 0.4 mm pin pitch, the LM34902 and LM34904 are rated for 300 mA and 500 mA continuous load currents, respectively. An input voltage range of 2.8V to 5.3V is provided to cater to 3V and 5V systems. With a low ON resistance, the high-side p-channel MOSFET switch power dissipation is minimized, translating into lower temperature increase—a critical feature in space constrained applications—and longer battery life. Using an integrated sense resistor, the LM34902/4 provides accurate brickwall current limit, protecting the input supply even when the ACC\_PWR output is hard-short to ground (GND). To assure reliability, thermal shutdown protection is provided if the junction temperature exceeds 135°C (LM34904) or 170°C (LM34902).

### **2 Evaluation Module Features**


- Input voltage operating range: 2.8V to 5.3V.
- Ambient temperature range: -40°C to +85°C.
- Rated load current: 300 mA (LM34902), 500 mA (LM34904).
- PCB size: 1.7" x 1.7" (43 mm x 43 mm).

### **3 Evaluation Module Operation**

As the pinouts and footprints of the LM34902 and LM34904 are identical, the solution presented in this user’s guide enables the user to evaluate both power switches. This commonality provides flexibility if the load current specifications evolve during the design process. The schematic in [Figure 1](#) demonstrates how the LM34902/4 switch connects to a device CPU (or an ASIC with embedded  $\mu$ C core) and an accessory load. Presented also is the LM34902/4 truth table operation ([Table 1](#)).

When the accessory is connected, it asserts an active-low accessory detect ( $\overline{\text{ACC\_DET}}$ ) control input. The CPU can then selectively turn on (or off) the switch using the ENABLE input, providing power to the accessory (or conserving power when needed). Both the ENABLE and  $\overline{\text{ACC\_DET}}$  inputs are 1.8V logic compatible. Both inputs need to be asserted to turn on the MOSFET switch ( $\overline{\text{ACC\_DET}}$  first and then ENABLE). Note that the power switch is not bidirectional: the input voltage must therefore be higher than the output voltage under all conditions.

All trademarks are the property of their respective owners.

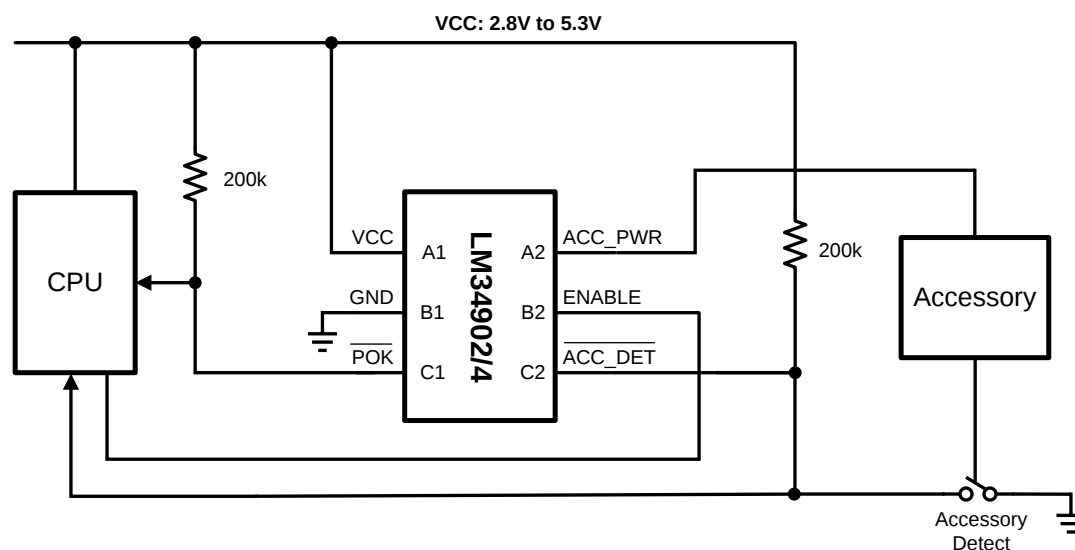
**Figure 1. Typical System Schematic**
**Table 1. Power Switch Truth Table**

| Input <sup>(1)</sup> |                              |                        |                               |                   | Output             |                         |
|----------------------|------------------------------|------------------------|-------------------------------|-------------------|--------------------|-------------------------|
| ENABLE               | $\overline{\text{ACC\_DET}}$ | Current Limit Detected | T <sub>J</sub> Limit Exceeded | 2.8V < VCC < 5.3V | PFET Switch Status | $\overline{\text{POK}}$ |
| 0                    | x                            | No                     | No                            | Yes               | Open               | Open Drain              |
| x                    | 1                            | No                     | No                            | Yes               | Open               | Open Drain              |
| 0 to 1               | 0                            | No                     | No                            | Yes               | On                 | Grounded                |
| 0 to 1               | 0                            | Yes                    | No                            | Yes               | Current Limited    | Grounded                |
| x                    | x                            | x                      | Yes                           | 2.2V < VCC < 5.3V | Open               | Open Drain              |
| 0                    | x                            | x                      | No                            | 2.2V < VCC < 2.8V | Open               | Open Drain              |

<sup>(1)</sup> x = stands for "don't care".

## 4 Evaluation Module Schematic

The schematic of the evaluation module is shown in Figure 2. Note that ENABLE and  $\overline{\text{ACC\_DET}}$  default to their off-states if left open-circuited in this implementation. An active-low open-drain output ( $\overline{\text{POK}}$ ) provides an indication of switch status to the CPU. As shown in Figure 2, the module provides pullup resistors to VCC for  $\overline{\text{POK}}$  and  $\overline{\text{ACC\_DET}}$  and a pulldown resistor to GND for ENABLE.

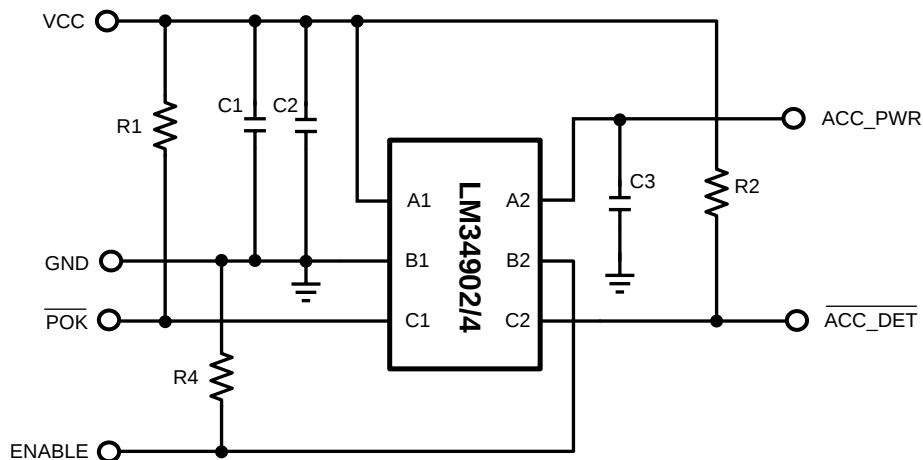


Figure 2. Evaluation Module Schematic

## 5 Evaluation Module Bill of Materials

| Designator                                                     | Value       | Description                               | Manufacturer         | Part Number        | Qty |
|----------------------------------------------------------------|-------------|-------------------------------------------|----------------------|--------------------|-----|
| C1, C2                                                         | 22 $\mu$ F  | Ceramic, 22 $\mu$ F, X5R, 10V, 10%, 0805  | Taiyo Yuden          | LMK212BJ226MG-T    | 2   |
| C3                                                             | 4.7 $\mu$ F | Ceramic, 4.7 $\mu$ F, X5R, 25V, 10%, 0805 | Murata               | GRM21BR61E475KA12L | 1   |
| VCC, ACC_PWR                                                   |             | Test Point, TH, Miniature, Red            | Keystone Electronics | 5000               | 2   |
| ENABLE, $\overline{\text{ACC\_DET}}$ , $\overline{\text{POK}}$ |             | Test Point, TH, Miniature, White          | Keystone Electronics | 5002               | 3   |
| GND                                                            |             | Test Point, TH, Miniature, Black          | Keystone Electronics | 5001               | 1   |
| R1, R2, R4                                                     | 220k        | Resistor, 220k ohm, 1%, 0.1W, 0603        | Vishay-Dale          | CRCW0603220KFKEA   | 3   |
| U1                                                             |             | 500mA Current Limited Power Switch        | Texas Instruments    | LM34904            | 1   |

## 6 Evaluation Module Component Selection

Ceramic input and output capacitors are positioned close to the load switch. Specifically, two 22  $\mu\text{F}$  bypass capacitors from VCC to GND minimize input voltage drop during a high current startup event or momentary output short circuit condition. A 1  $\mu\text{F}$  capacitor is usually adequate even though larger capacitance will further reduce the voltage drop. A 4.7  $\mu\text{F}$  decoupling capacitor from ACC\_PWR to GND alleviates any negative swing of ACC\_PWR induced by parasitic inductance in the load lines as the load current ramps to zero during a turn-off event. Of course, all traces should be kept as short as possible with VCC, ACC\_PWR and GND power bus traces kept wide to minimize conduction drop and assist with thermal spreading.

When the output is short-circuited, the input voltage appears across the switch, and the instantaneous power dissipation can be quite high. If the fault condition is not removed, the die temperature may increase to the level where the thermal shutdown protection activates. If the faulted short-circuit condition persists and the device engages thermal shutdown, it latches off. ENABLE can be cycled to initiate a re-start.

## 7 Evaluation Module Power Up Procedure

**Step 1:** Apply an input voltage between 2.8V and 5.3V (VCC to GND).

**Step 2:** Connect  $\overline{\text{ACC\_DET}}$  to GND.

**Step 3:** Connect ENABLE to VCC. The load switch turns on – measure voltage from ACC\_PWR to GND.

**Step 4:** Apply a load current up to the rated current of the device – check voltage from ACC\_PWR to GND.

**Step 5:** Apply and remove an overload or short circuit – confirm recovery from this condition.

**Step 6:** Cycle ENABLE high and low to assess turn on and turn off waveforms, respectively.

## 8 Evaluation Module Performance Characteristics

Using the LM34904 with  $\overline{\text{ACC\_DET}}$  and  $\overline{\text{POK}}$  pullup resistors connected to a pullup voltage source of 1.8V, various performance characteristics of the evaluation module are presented in Figure 3 through Figure 9.

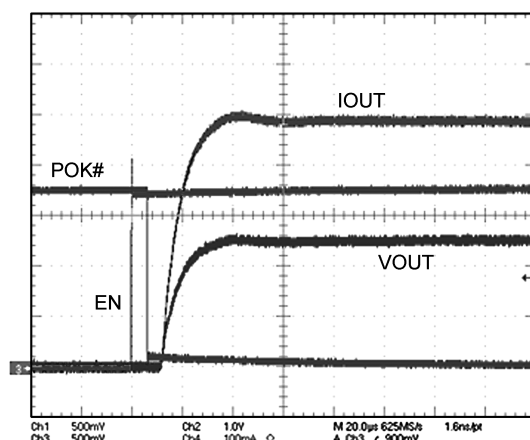


Figure 3. ENABLE Turn On, VCC = 2.8V, IOU = 0.5A (Resistive Load)

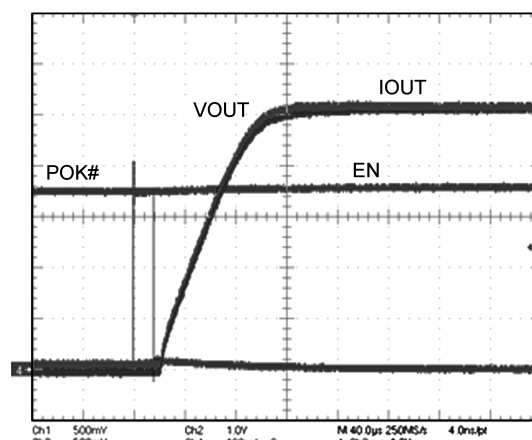


Figure 4. ENABLE Turn On, VCC = 5.3V, IOU = 0.5A (Resistive Load)

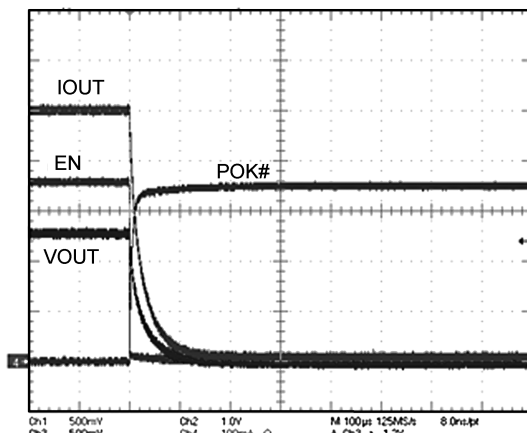


Figure 5. ENABLE Turn Off,  $V_{CC} = 2.8V$ ,  $I_{OUT} = 0.5A$  (Resistive Load)

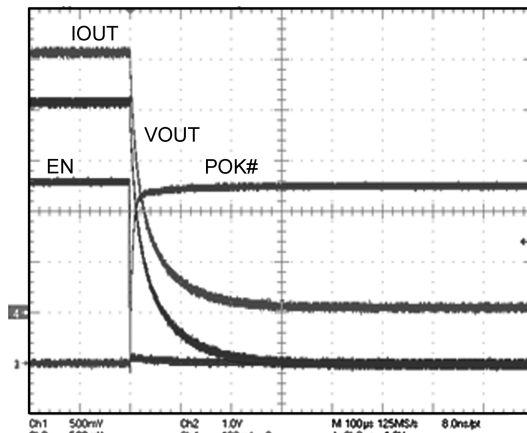


Figure 6. ENABLE Turn Off,  $V_{CC} = 5.3V$ ,  $I_{OUT} = 0.5A$  (Resistive Load)

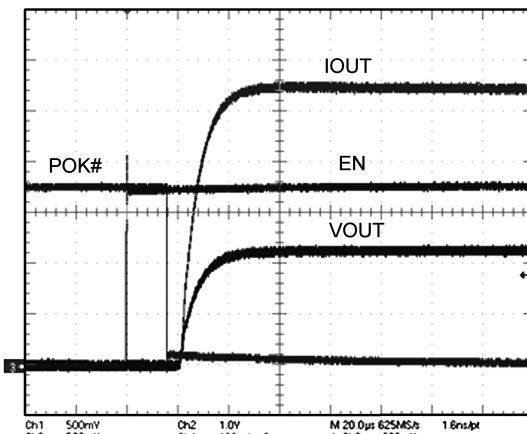


Figure 7. ENABLE Turn On Into An Overload Condition ( $4\Omega$  Resistive Load),  $V_{CC} = 5.3V$

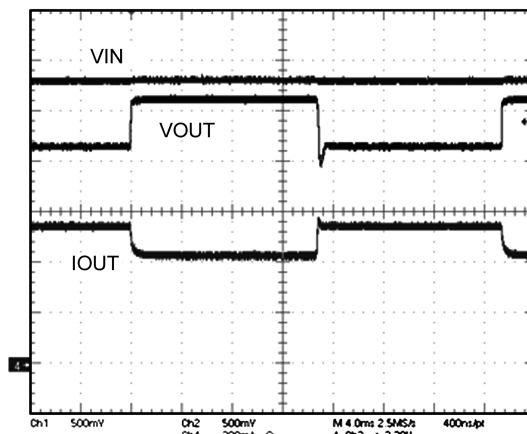


Figure 8. Output Transient Response When Cycling Into and Out Of Current Limit (Electronic Load Output),  $V_{CC} = 5.3V$

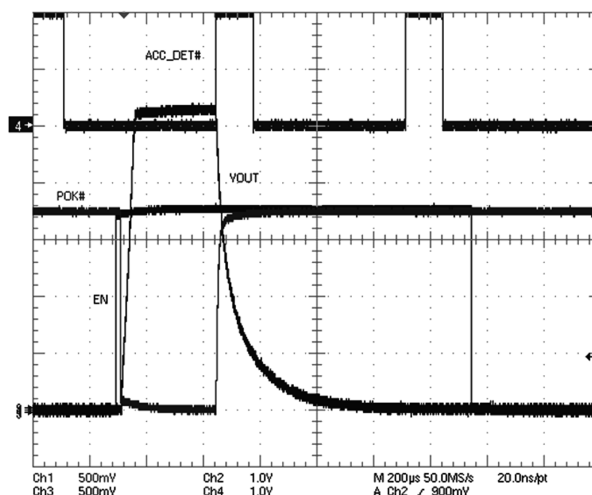


Figure 9. ENABLE and  $\overline{ACC\_DET}$  Cycled Independently,  $V_{CC} = 5.3V$

## 9 PCB Layout

The LM34902/4 evaluation module uses a two-layer FR4 PCB with terminal connections provided for VCC, ACC\_PWR, GND, ENABLE, ACC\_DET and POK. The top and bottom side PCB layouts are shown in [Figure 10](#) and [Figure 11](#), respectively.


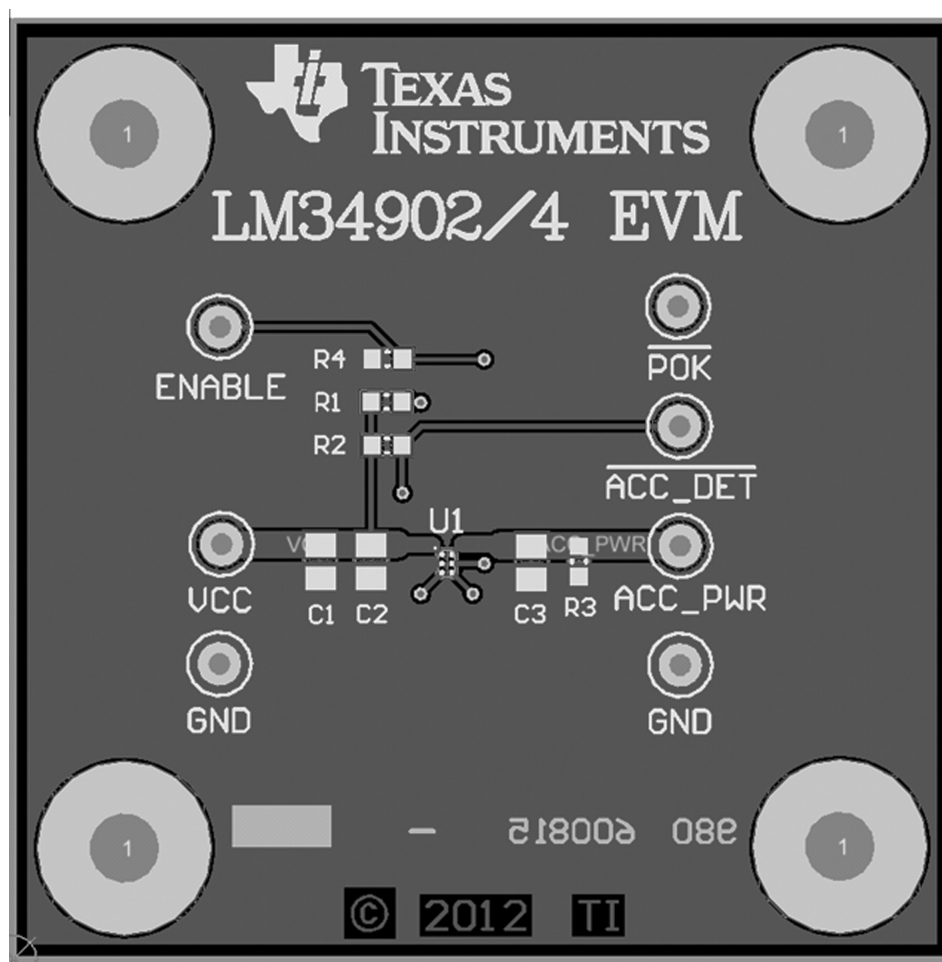


Figure 10. PCB Top Layer

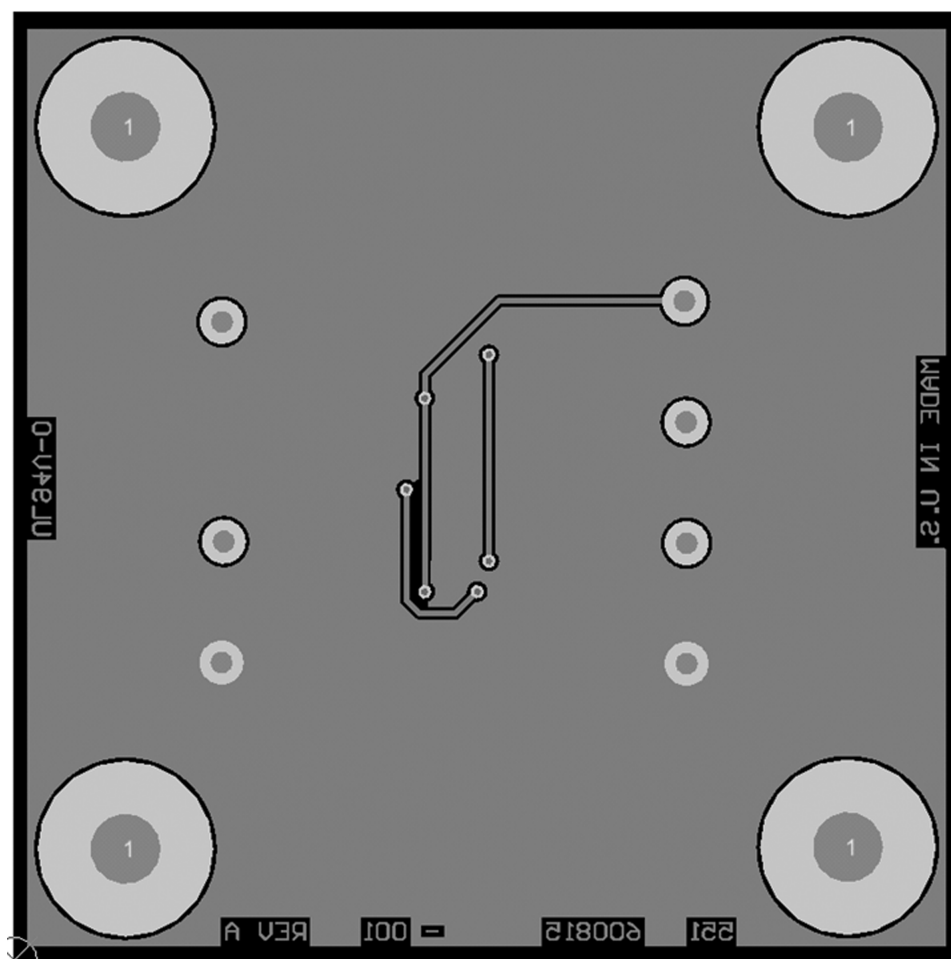

**Figure 11. PCB Bottom Layer**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

|                              |                                                                                      |
|------------------------------|--------------------------------------------------------------------------------------|
| Audio                        | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                               |
| Amplifiers                   | <a href="http://amplifier.ti.com">amplifier.ti.com</a>                               |
| Data Converters              | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>                       |
| DLP® Products                | <a href="http://www.dlp.com">www.dlp.com</a>                                         |
| DSP                          | <a href="http://dsp.ti.com">dsp.ti.com</a>                                           |
| Clocks and Timers            | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>                             |
| Interface                    | <a href="http://interface.ti.com">interface.ti.com</a>                               |
| Logic                        | <a href="http://logic.ti.com">logic.ti.com</a>                                       |
| Power Mgmt                   | <a href="http://power.ti.com">power.ti.com</a>                                       |
| Microcontrollers             | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a>                   |
| RFID                         | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>                                 |
| OMAP Applications Processors | <a href="http://www.ti.com/omap">www.ti.com/omap</a>                                 |
| Wireless Connectivity        | <a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a> |

### Applications

|                               |                                                                                          |
|-------------------------------|------------------------------------------------------------------------------------------|
| Automotive and Transportation | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>                         |
| Communications and Telecom    | <a href="http://www.ti.com/communications">www.ti.com/communications</a>                 |
| Computers and Peripherals     | <a href="http://www.ti.com/computers">www.ti.com/computers</a>                           |
| Consumer Electronics          | <a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>                   |
| Energy and Lighting           | <a href="http://www.ti.com/energy">www.ti.com/energy</a>                                 |
| Industrial                    | <a href="http://www.ti.com/industrial">www.ti.com/industrial</a>                         |
| Medical                       | <a href="http://www.ti.com/medical">www.ti.com/medical</a>                               |
| Security                      | <a href="http://www.ti.com/security">www.ti.com/security</a>                             |
| Space, Avionics and Defense   | <a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a> |
| Video and Imaging             | <a href="http://www.ti.com/video">www.ti.com/video</a>                                   |

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)