

Single-chip Type with Built-in FET Switching Regulator Series



Low Noise High Efficiency Step-down Switching Regulator with Built-in Power MOSFET

BD8964FVM

No.09027EAT23

● Description

ROHM's high efficiency step-down switching regulator BD8964FVM is a power supply designed to produce a low voltage including 1 volts from 5/3.3 volts power supply line. Offers high efficiency with synchronous rectifier. Employs a current mode control system to provide faster transient response to sudden change in load.

● Features

- 1) Offers fast transient response with current mode PWM control system.
- 2) Offers highly efficiency for all load range with synchronous rectifier (Nch/Pch FET)
- 3) Incorporates soft-start function.
- 4) Incorporates thermal protection and ULVO functions.
- 5) Incorporates short-current protection circuit with time delay function.
- 6) Incorporates shutdown function
- 7) Employs small surface mount package : MSOP8

● Use

Power supply for LSI including DSP, Micro computer and ASIC

● Line up

Parameter	Symbol	Limits		Unit
Vcc Voltage	Vcc	-0.3~+7 ^{*1}		V
PVcc Voltage	PVcc	-0.3~+7 ^{*1}		V
EN Voltage	V _{EN}	-0.3~+7		V
SW,ITH Voltage	V _{SW} ,V _{ITH}	-0.3~+7		V
Power Dissipation 1	P _{d1}	387.5 ^{*2}		mW
Power Dissipation 2	P _{d2}	587.4 ^{*3}		mW
Operating temperature range	T _{opr}	-25~+85		°C
Storage temperature range	T _{stg}	-55~+150		°C
Maximum junction temperature	T _{jmax}	+150		°C

*1 Pd should not be exceeded.

*2 Derating is done 3.1mW/°C for temperatures above Ta=25°C.

*3 Derating is done 4.7mW/°C for temperatures above Ta=25°C, Mounted on 70mm×70mm×1.6mm Glass Epoxy PCB.

● Operating Conditions (Ta=25°C)

Parameter	Symbol	Limits			Unit
		Min.	Typ.	Max.	
Vcc Voltage	V _{CC} ^{*4}	4.0	5.0	5.5	V
PVcc Voltage	PV _{CC} ^{*4}	4.0	5.0	5.5	V
EN Voltage	V _{EN}	0	-	V _{CC}	V
Output voltage Setting Range	V _{OUT}	1.0	-	1.8	V
SW average output current	I _{sw} ^{*4}	-	-	1.2	A

*4 Pd should not be exceeded.

● Electrical Characteristics

◎ (Ta=25°C, Vcc=5V, EN=Vcc, R1=20kΩ, R2=10kΩ unless otherwise specified.)

Parameter	Symbol	Min.	Typ.	Max.	Unit	Conditions
Standby current	I _{STB}	-	0	10	μA	EN=GND
Bias current	I _{CC}	-	250	450	μA	
EN Low voltage	V _{ENL}	-	GND	0.8	V	Standby mode
EN High voltage	V _{ENH}	2.0	V _{CC}	-	V	Active mode
EN input current	I _{EN}	-	1	10	μA	V _{EN} =5V
Oscillation frequency	F _{OOSC}	0.8	1	1.2	MHz	
Pch FET ON resistance	R _{ONP}	-	350	600	mΩ	P _{VCC} =5V
Nch FET ON resistance	R _{ONN}	-	250	500	mΩ	P _{VCC} =5V
ADJ voltage	V _{ADJ}	0.78	0.80	0.82	V	
ITH sink current	I _{THSI}	10	20	-	μA	V _{ADJ} =H
ITH source current	I _{THSO}	10	20	-	μA	V _{ADJ} =L
UVLO threshold voltage	V _{UVLO1}	3.6	3.8	4.0	V	V _{CC} =4→0V
UVLO release voltage	V _{UVLO2}	3.65	3.90	4.2	V	V _{CC} =0→4V
Soft start time	T _{SS}	0.5	1	2	ms	V _{ADJ} =H
Timer latch time	T _{LATCH}	1	2	3	ms	SCP/TSD operated

● Block Diagram, Application Circuit

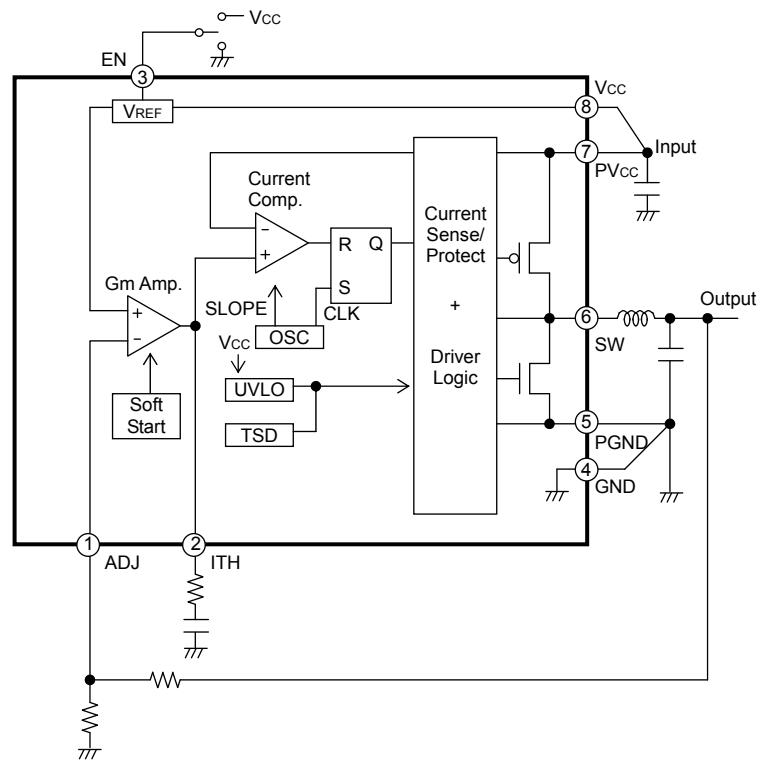
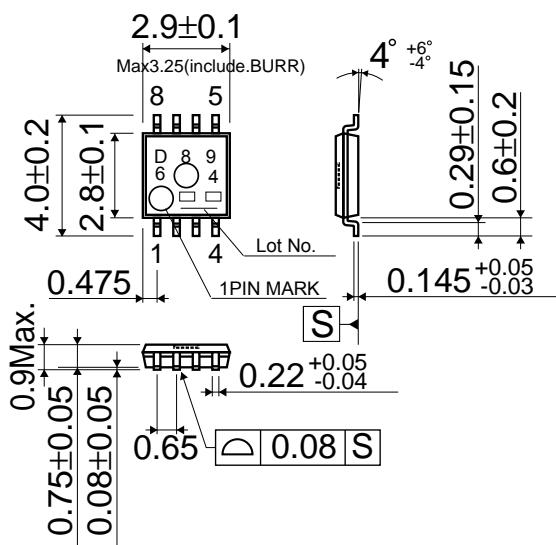


Fig.1 BD8964FVM View

Fig.2 BD8964FVM Block Diagram

● Pin No. & function table

Pin No.	Pin name	PIN function
1	ADJ	Output voltage detect pin
2	ITH	GmAmp output pin/Connected phase compensation capacitor
3	EN	Enable pin(Active High)
4	GND	Ground
5	PGND	Nch FET source pin
6	SW	Pch/Nch FET drain output pin
7	PVcc	Pch FET source pin
8	Vcc	VCC power supply input pin

● Characteristics data (Reference data)

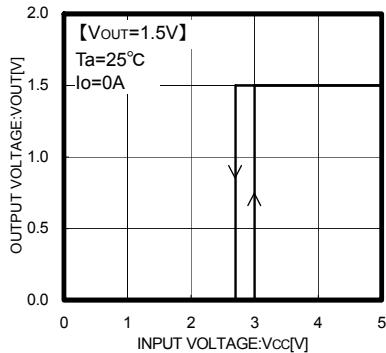


Fig.3 Vcc-Vout

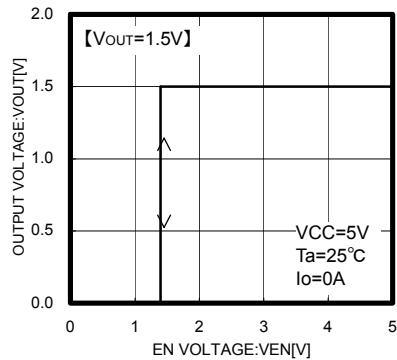


Fig.4 Ven-Vout

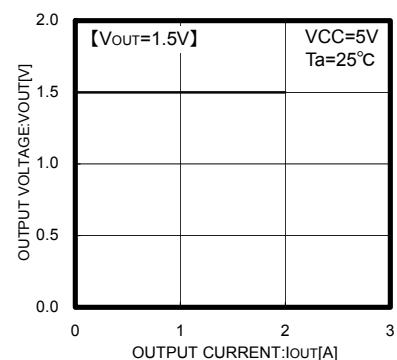


Fig.5 Iout-Vout

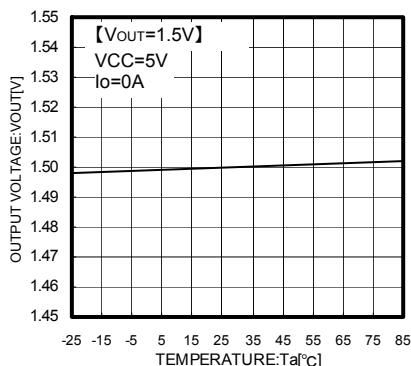


Fig.6 Ta-VOUT

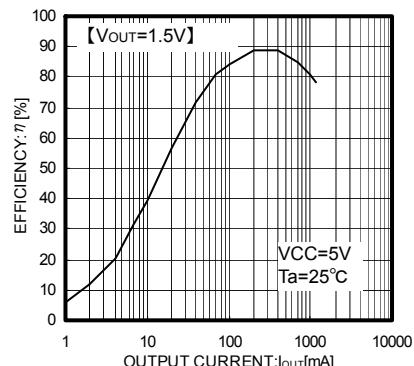


Fig.7 Efficiency

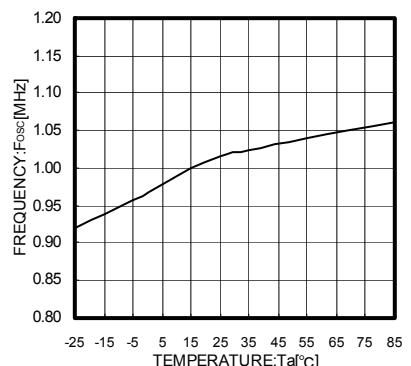


Fig.8 Ta-Fosc

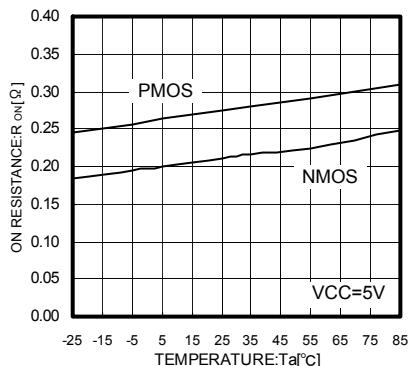


Fig.9 Ta-RONN, RONP

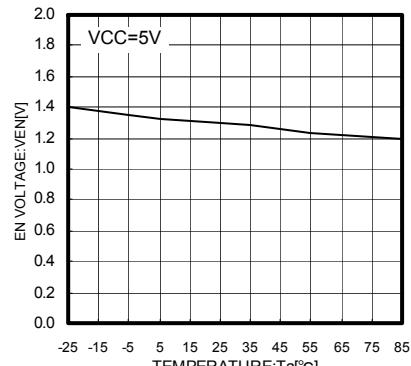


Fig.10 Ta-VEN

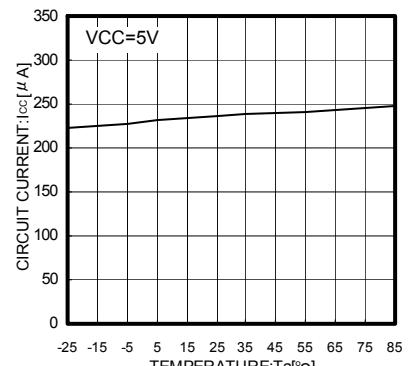


Fig.11 Ta-ICC

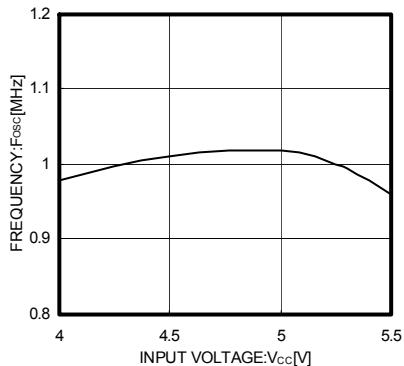


Fig.12 Vcc-Fosc

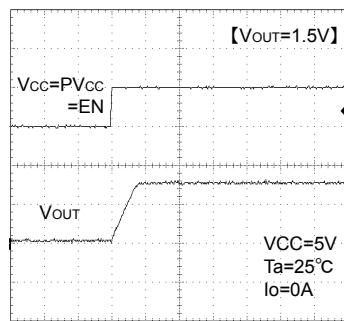


Fig.13 Soft start waveform

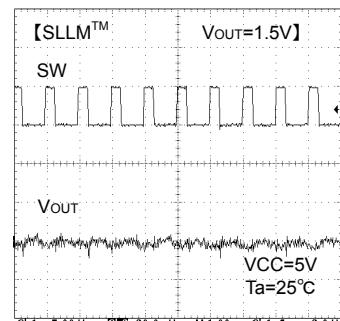
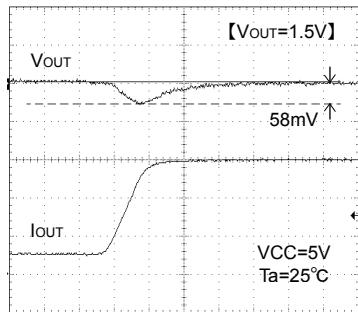
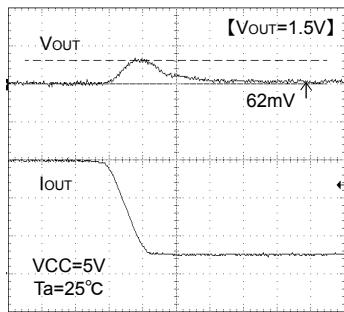



Fig.14 SW waveform

Fig. 15 Transient response
Io=100→600mA(10μs)Fig.16 Transient response
Io=600→100mA(10μs)


● Information on advantages

Advantage 1 : Offers fast transient response with current mode control system.

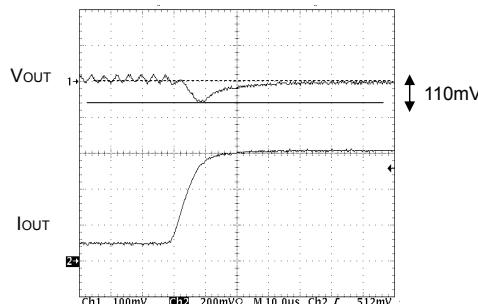Conventional product (Load response $I_{O}=0.1A \rightarrow 0.6A$)



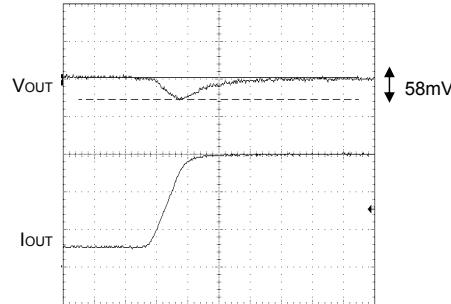BD8964FVM (Load response $I_{O}=0.1A \rightarrow 0.6A$)




Voltage drop due to sudden change in load was reduced

Fig.17 Comparison of transient response

Advantage 2 : Offers high efficiency with synchronous rectifier

- For heavier load:
Utilizes the synchronous rectifying mode and the low on-resistance MOS FETs incorporated as power transistor.

{ ON resistance of P-channel MOS FET : 350mΩ(Typ.)
ON resistance of N-channel MOS FET : 250mΩ(Typ.)

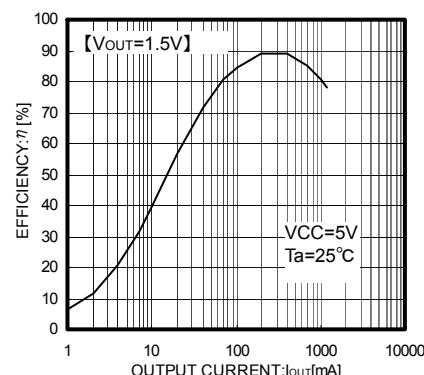

Advantage 3 : Supplied in smaller package due to small-sized power MOS FET incorporated.

- ↓
- Output capacitor C_o required for current mode control: 10μF ceramic capacitor
 - Inductance L required for the operating frequency of 1 MHz: 4.7μH inductor

Reduces a mounting area required.

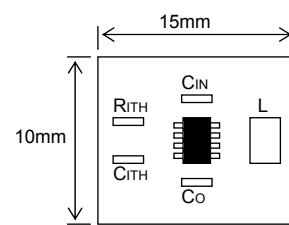
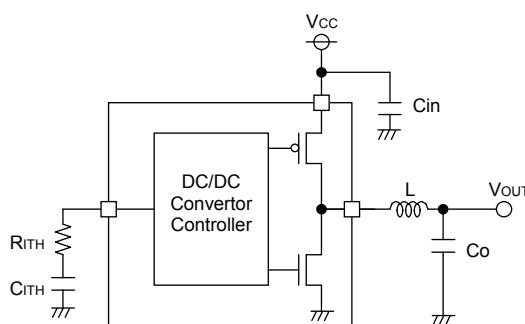


Fig.19 Example application

● Operation

BD8964FVM is a synchronous rectifying step-down switching regulator that achieves faster transient response by employing current mode PWM control system.

○ Synchronous rectifier

It does not require the power to be dissipated by a rectifier externally connected to a conventional DC/DC converter IC, and its P.N junction shoot-through protection circuit limits the shoot-through current during operation, by which the power dissipation of the set is reduced.

○ Current mode PWM control

Synthesizes a PWM control signal with a inductor current feedback loop added to the voltage feedback.

- PWM (Pulse Width Modulation) control

The oscillation frequency for PWM is 1 MHz. SET signal from OSC turns ON a P-channel MOS FET (while a N-channel MOS FET is turned OFF), and an inductor current I_L increases. The current comparator (Current Comp) receives two signals, a current feedback control signal (SENSE: Voltage converted from I_L) and a voltage feedback control signal (FB), and issues a RESET signal if both input signals are identical to each other, and turns OFF the P-channel MOS FET (while a N-channel MOS FET is turned ON) for the rest of the fixed period. The PWM control repeat this operation.

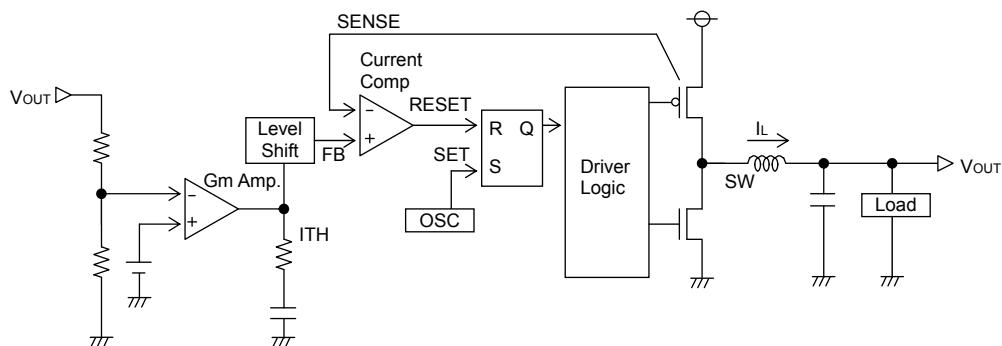


Fig.20 Diagram of current mode PWM control

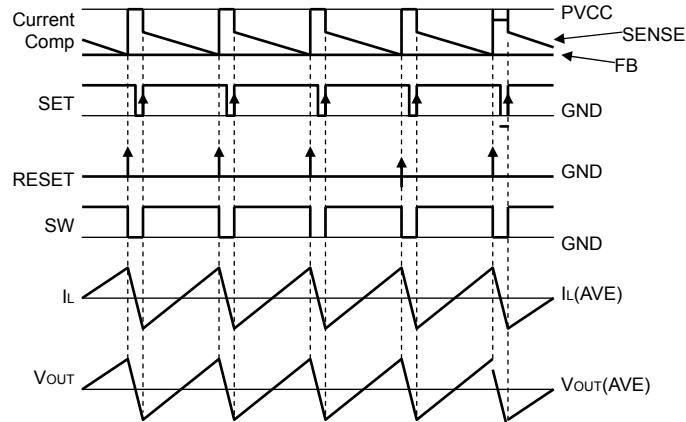


Fig.21 PWM switching timing chart

● Description of operations

- Soft-start function

EN terminal shifted to "High" activates a soft-starter to gradually establish the output voltage with the current limited during startup, by which it is possible to prevent an overshoot of output voltage and an inrush current.

- Shutdown function

With EN terminal shifted to "Low", the device turns to Standby Mode, and all the function blocks including reference voltage circuit, internal oscillator and drivers are turned to OFF. Circuit current during standby is $0\mu\text{F}$ (Typ.).

- UVLO function

Detects whether the input voltage sufficient to secure the output voltage of this IC is supplied. And the hysteresis width of 300mV (Typ.) is provided to prevent output chattering.

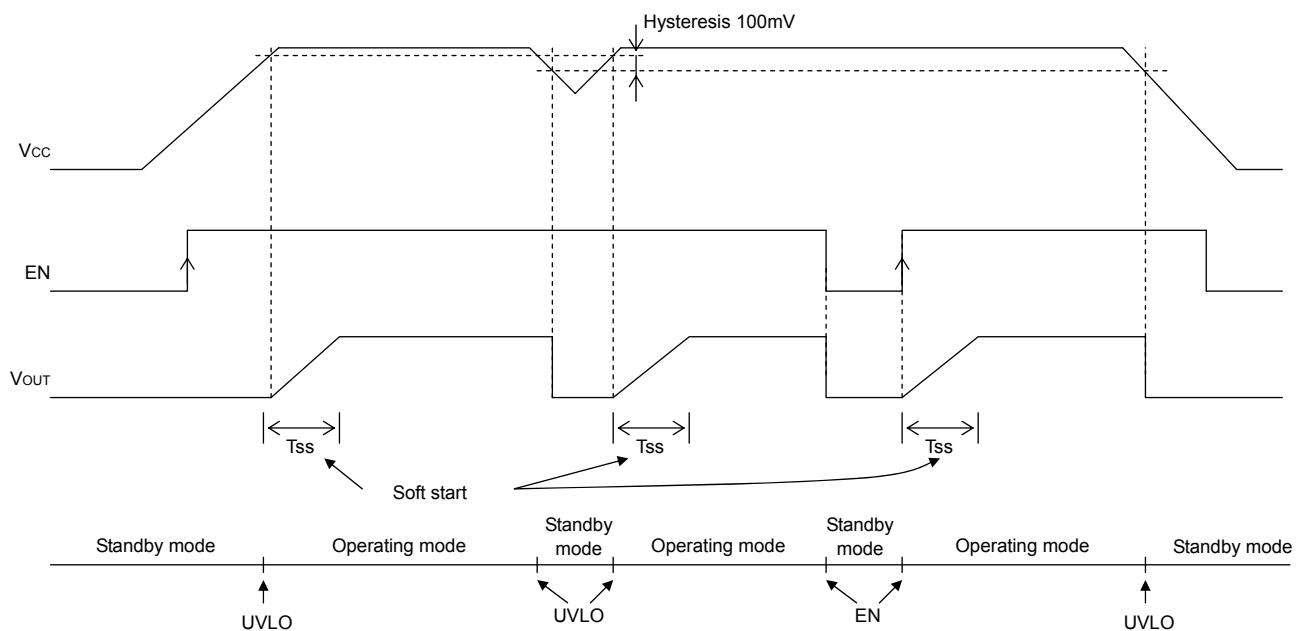


Fig.22 Soft start, Shutdown, UVLO timing chart

- Short-current protection circuit with time delay function

Turns OFF the output to protect the IC from breakdown when the incorporated current limiter is activated continuously for at least 1 ms. The output thus held tuned OFF may be recovered by restarting EN or by re-unlocking UVLO.

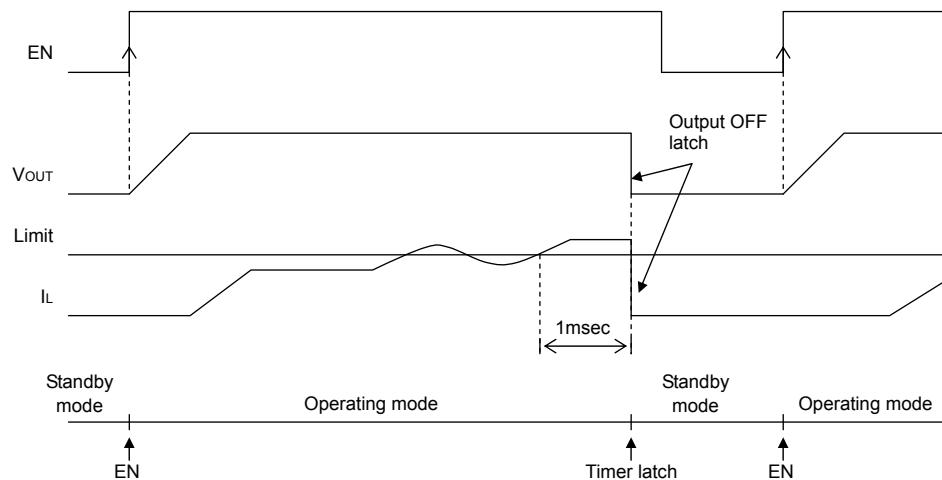


Fig.23 Short-current protection circuit with time delay timing chart

● Switching regulator efficiency

Efficiency η may be expressed by the equation shown below:

$$\eta = \frac{V_{OUT} \times I_{OUT}}{V_{IN} \times I_{IN}} \times 100[\%] = \frac{P_{OUT}}{P_{IN}} \times 100[\%] = \frac{P_{OUT}}{P_{OUT} + P_{D\alpha}} \times 100[\%]$$

Efficiency may be improved by reducing the switching regulator power dissipation factors $P_{D\alpha}$ as follows:

Dissipation factors:

1) ON resistance dissipation of inductor and FET : $PD(I^2R)$

2) Gate charge/discharge dissipation : $PD(\text{Gate})$

3) Switching dissipation : $PD(\text{SW})$

4) ESR dissipation of capacitor : $PD(\text{ESR})$

5) Operating current dissipation of IC : $PD(\text{IC})$

1) $PD(I^2R) = I_{OUT}^2 \times (R_{COIL} + R_{ON})$ ($R_{COIL}[\Omega]$: DC resistance of inductor, $R_{ON}[\Omega]$: ON resistance of FET, $I_{OUT}[\text{A}]$: Output current.)

2) $PD(\text{Gate}) = C_{GS} \times f \times V$ ($C_{GS}[\text{F}]$: Gate capacitance of FET, $f[\text{Hz}]$: Switching frequency, $V[\text{V}]$: Gate driving voltage of FET)

3) $PD(\text{SW}) = \frac{V_{IN}^2 \times C_{RSS} \times I_{OUT} \times f}{I_{DRIVE}}$ ($C_{RSS}[\text{F}]$: Reverse transfer capacitance of FET, $I_{DRIVE}[\text{A}]$: Peak current of gate.)

4) $PD(\text{ESR}) = I_{RMS}^2 \times ESR$ ($I_{RMS}[\text{A}]$: Ripple current of capacitor, $ESR[\Omega]$: Equivalent series resistance.)

5) $PD(\text{IC}) = V_{IN} \times I_{CC}$ ($I_{CC}[\text{A}]$: Circuit current.)

● Consideration on permissible dissipation and heat generation

As this IC functions with high efficiency without significant heat generation in most applications, no special consideration is needed on permissible dissipation or heat generation. In case of extreme conditions, however, including lower input voltage, higher output voltage, heavier load, and/or higher temperature, the permissible dissipation and/or heat generation must be carefully considered.

For dissipation, only conduction losses due to DC resistance of inductor and ON resistance of FET are considered. Because the conduction losses are considered to play the leading role among other dissipation mentioned above including gate charge/discharge dissipation and switching dissipation.

$$P = I_{OUT}^2 \times (R_{COIL} + R_{ON})$$

$$R_{ON} = D \times R_{ONP} + (1-D)R_{ONN}$$

D : ON duty ($=V_{OUT}/V_{CC}$)

R_{COIL} : DC resistance of coil

R_{ONP} : ON resistance of P-channel MOS FET

R_{ONN} : ON resistance of N-channel MOS FET

I_{OUT} : Output current

If $V_{CC}=5\text{V}$, $V_{OUT}=1.5\text{V}$, $R_{COIL}=0.15\Omega$, $R_{ONP}=0.35\Omega$, $R_{ONN}=0.25\Omega$

$I_{OUT}=0.8\text{A}$, for example,

$$D = V_{OUT}/V_{CC} = 1.5/5 = 0.3$$

$$R_{ON} = 0.3 \times 0.35 + (1-0.3) \times 0.25$$

$$= 0.105 + 0.175$$

$$= 0.28[\Omega]$$

$$P = 0.8^2 \times (0.15 + 0.28)$$

$$\doteq 275.2[\text{mW}]$$

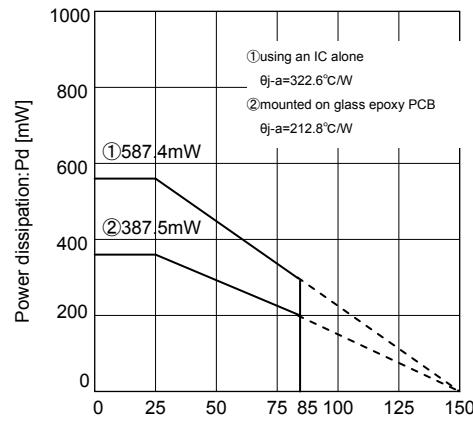


Fig. 24

As R_{ONP} is greater than R_{ONN} in this IC, the dissipation increases as the ON duty becomes greater. With the consideration on the dissipation as above, thermal design must be carried out with sufficient margin allowed.

● Selection of components externally connected

1. Selection of inductor (L)

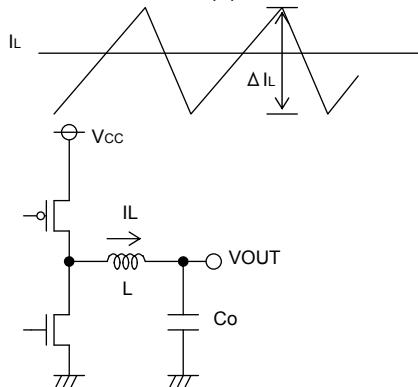


Fig.25 Output ripple current

The inductance significantly depends on output ripple current. As seen in the equation (1), the ripple current decreases as the inductor and/or switching frequency increases.

$$\Delta IL = \frac{(Vcc - Vout) \times Vout}{L \times Vcc \times f} [A] \quad \dots (1)$$

Appropriate ripple current at output should be 30% more or less of the maximum output current.

$$\Delta IL = 0.3 \times Iout_{max} [A] \quad \dots (2)$$

$$L = \frac{(Vcc - Vout) \times Vout}{\Delta IL \times Vcc \times f} [H] \quad \dots (3)$$

(ΔIL: Output ripple current, and f: Switching frequency)

* Current exceeding the current rating of the inductor results in magnetic saturation of the inductor, which decreases efficiency. The inductor must be selected allowing sufficient margin with which the peak current may not exceed its current rating. If Vcc=5V, Vout=1.5V, f=1MHz, ΔIL=0.3×0.8A=0.24A, for example,

$$L = \frac{(5-1.5) \times 1.5}{0.24 \times 5 \times 1M} = 4.375 \mu H \rightarrow 4.7[\mu H]$$

*Select the inductor of low resistance component (such as DCR and ACR) to minimize dissipation in the inductor for better efficiency.

2. Selection of output capacitor (Co)

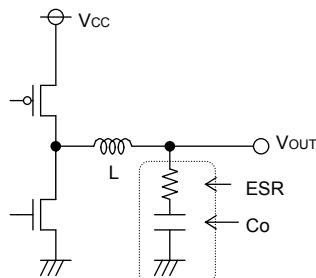


Fig.26 Output capacitor

Output capacitor should be selected with the consideration on the stability region and the equivalent series resistance required to smooth ripple voltage. Output ripple voltage is determined by the equation (4) :

$$\Delta Vout = \Delta IL \times ESR [V] \quad \dots (4)$$

(ΔIL: Output ripple current, ESR: Equivalent series resistance of output capacitor)

*Rating of the capacitor should be determined allowing sufficient margin against output voltage. Less ESR allows reduction in output ripple voltage.

As the output rise time must be designed to fall within the soft-start time, the capacitance of output capacitor should be determined with consideration on the requirements of equation (5):

$$Co \leq \frac{Tss \times (Ilimit - Iout)}{Vout} \quad \dots (5) \quad \begin{cases} Tss: \text{Soft-start time} \\ Ilimit: \text{Over current detection level, 2A(Typ)} \end{cases}$$

In case of BD8964FVM, for instance, and if Vout=1.5V, Iout=0.8A, and Tss=1ms,

$$Co \leq \frac{1m \times (2-0.8)}{1.5} \approx 800[\mu F]$$

Inappropriate capacitance may cause problem in startup. A 10 μF to 100 μF ceramic capacitor is recommended.

3. Selection of input capacitor (Cin)

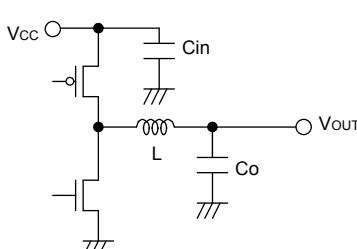


Fig.27 Input capacitor

Input capacitor to select must be a low ESR capacitor of the capacitance sufficient to cope with high ripple current to prevent high transient voltage. The ripple current IRMS is given by the equation (5):

$$IRMS = Iout \times \frac{\sqrt{Vout(Vcc - Vout)}}{Vcc} [A] \quad \dots (5)$$

< Worst case > IRMS(max.)

$$\text{When } Vcc \text{ is twice the } Vout, \text{ IRMS} = \frac{Iout}{2}$$

If Vcc=5.0V, Vout=1.5V, and Ioutmax.=0.8A

$$IRMS = 0.8 \times \frac{\sqrt{5(5-1.5)}}{5} = 0.67[\text{ARMS}]$$

A low ESR 10μF/10V ceramic capacitor is recommended to reduce ESR dissipation of input capacitor for better efficiency.

4. Determination of RITH, CITH that works as a phase compensator

As the Current Mode Control is designed to limit a inductor current, a pole (phase lag) appears in the low frequency area due to a CR filter consisting of a output capacitor and a load resistance, while a zero (phase lead) appears in the high frequency area due to the output capacitor and its ESR. So, the phases are easily compensated by adding a zero to the power amplifier output with C and R as described below to cancel a pole at the power amplifier.

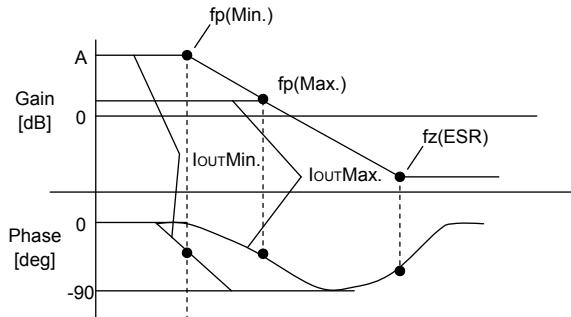


Fig.28 Open loop gain characteristics

$$fp = \frac{1}{2\pi \times Ro \times Co}$$

$$fz(ESR) = \frac{1}{2\pi \times ESR \times Co}$$

Pole at power amplifier

When the output current decreases, the load resistance Ro increases and the pole frequency lowers.

$$fp(\text{Min.}) = \frac{1}{2\pi \times Ro_{\text{Max.}} \times Co} \text{ [Hz]} \leftarrow \text{with lighter load}$$

$$fp(\text{Max.}) = \frac{1}{2\pi \times Ro_{\text{Min.}} \times Co} \text{ [Hz]} \leftarrow \text{with heavier load}$$

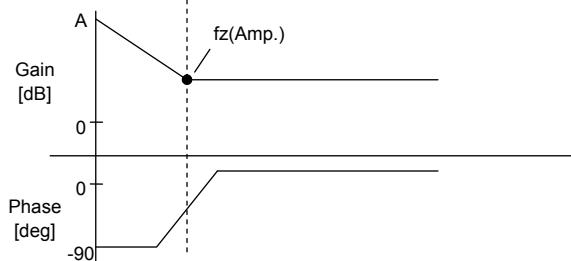


Fig.29 Error amp phase compensation characteristics

Zero at power amplifier

Increasing capacitance of the output capacitor lowers the pole frequency while the zero frequency does not change. (This is because when the capacitance is doubled, the capacitor ESR reduces to half.)

$$fz(\text{Amp.}) = \frac{1}{2\pi \times RITH \times CITH}$$

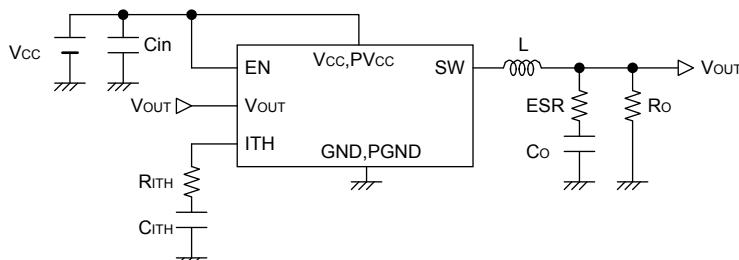


Fig.30 Typical application

Stable feedback loop may be achieved by canceling the pole fp (Min.) produced by the output capacitor and the load resistance with CR zero correction by the error amplifier.

$$fz(\text{Amp.}) = fp(\text{Min.})$$

$$\rightarrow \frac{1}{2\pi \times RITH \times CITH} = \frac{1}{2\pi \times Ro_{\text{Max.}} \times Co}$$

5. Determination of output voltage

The output voltage $VOUT$ is determined by the equation (7):

$VOUT = (R2/R1+1) \times VADJ \dots (7)$ $VADJ$: Voltage at ADJ terminal (0.8V Typ.)
With $R1$ and $R2$ adjusted, the output voltage may be determined as required.
(Adjustable output voltage range : 1.0V ~ 1.8V)
Use 1 k Ω ~ 100 k Ω resistor for $R1$. If a resistor of the resistance higher than 100 k Ω is used, check the assembled set carefully for ripple voltage etc.

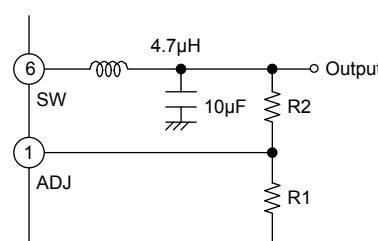


Fig.31 Determination of output voltage

● BD8964FVM Cautions on PC Board layout

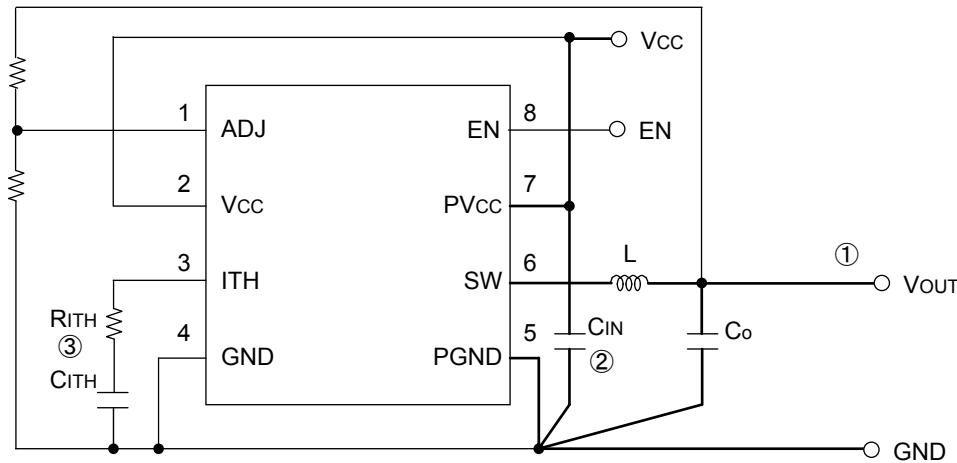


Fig.32 Layout diagram

- ① For the sections drawn with heavy line, use thick conductor pattern as short as possible.
- ② Lay out the input ceramic capacitor CIN closer to the pins PVCC and PGND, and the output capacitor Co closer to the pin PGND.
- ③ Lay out CITH and RITH between the pins ITH and GND as near as possible with least necessary wiring.

● Recommended components Lists on above application

Symbol	Part	Value	Manufacturer	Series
L	Coil	4.7 μ H	Sumida	CMD6D11B
			TDK	VLF5014AT-4R7M1R1
CIN	Ceramic capacitor	10 μ F	Kyocera	CM316X5R106K10A
Co	Ceramic capacitor	10 μ F	Kyocera	CM316X5R106K10A
CITH	Ceramic capacitor	1000pF	murata	GRM18series
RITH	Resistance	VOUT=1.0V	ROHM	MCR10 4301
		4.3k Ω	ROHM	MCR10 6801
		VOUT=1.2V	ROHM	MCR10 9101
		6.8k Ω	ROHM	MCR10 1202

* The parts list presented above is an example of recommended parts. Although the parts are sound, actual circuit characteristics should be checked on your application carefully before use. Be sure to allow sufficient margins to accommodate variations between external devices and this IC when employing the depicted circuit with other circuit constants modified. Both static and transient characteristics should be considered in establishing these margins. When switching noise is substantial and may impact the system, a low pass filter should be inserted between the VCC and PVCC pins, and a schottky barrier diode established between the SW and PGND pins.

● I/O equivalence circuit

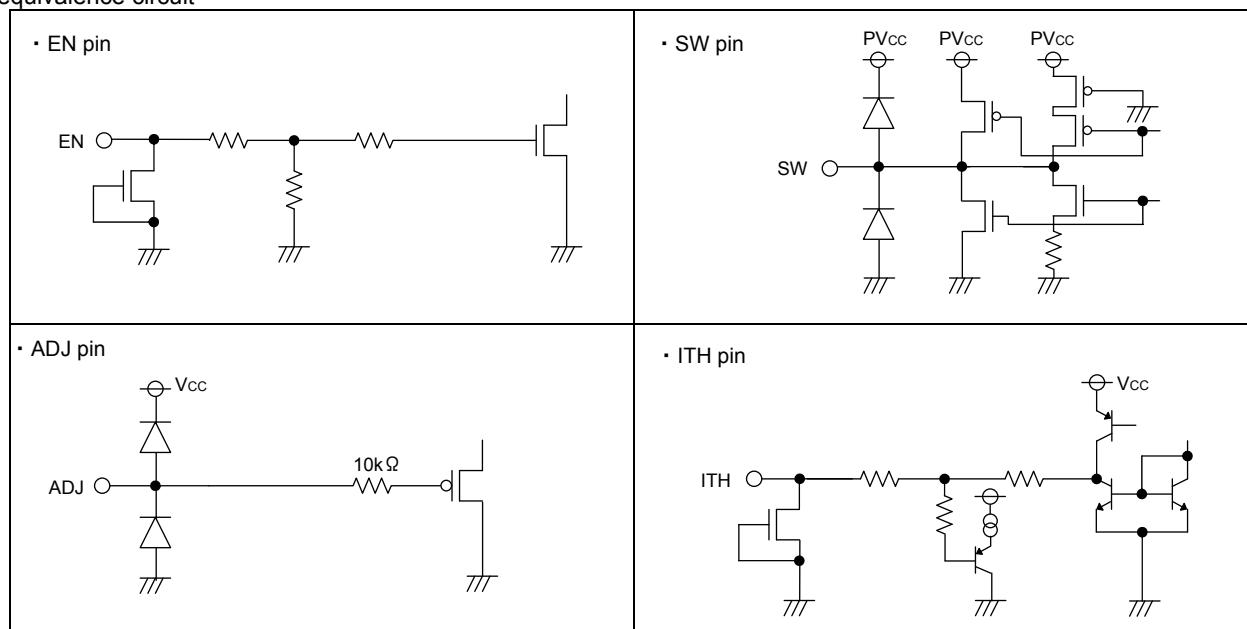


Fig.33 I/O equivalence circuit

● Notes for use

1. Absolute Maximum Ratings

While utmost care is taken to quality control of this product, any application that may exceed some of the absolute maximum ratings including the voltage applied and the operating temperature range may result in breakage. If broken, short-mode or open-mode may not be identified. So if it is expected to encounter with special mode that may exceed the absolute maximum ratings, it is requested to take necessary safety measures physically including insertion of fuses.

2. Electrical potential at GND

GND must be designed to have the lowest electrical potential in any operating conditions.

3. Short-circuiting between terminals, and mismounting

When mounting to pc board, care must be taken to avoid mistake in its orientation and alignment. Failure to do so may result in IC breakdown. Short-circuiting due to foreign matters entered between output terminals, or between output and power supply or GND may also cause breakdown.

4. Operation in Strong electromagnetic field

Be noted that using the IC in the strong electromagnetic radiation can cause operation failures.

5. Thermal shutdown protection circuit

Thermal shutdown protection circuit is the circuit designed to isolate the IC from thermal runaway, and not intended to protect and guarantee the IC. So, the IC the thermal shutdown protection circuit of which is once activated should not be used thereafter for any operation originally intended.

6. Inspection with the IC set to a pc board

If a capacitor must be connected to the pin of lower impedance during inspection with the IC set to a pc board, the capacitor must be discharged after each process to avoid stress to the IC. For electrostatic protection, provide proper grounding to assembling processes with special care taken in handling and storage. When connecting to jigs in the inspection process, be sure to turn OFF the power supply before it is connected and removed.

7. Input to IC terminals

This is a monolithic IC with P⁺ isolation between P-substrate and each element as illustrated below. This P-layer and the N-layer of each element form a P-N junction, and various parasitic element are formed.

If a resistor is joined to a transistor terminal as shown in Fig 34.

○ P-N junction works as a parasitic diode if the following relationship is satisfied; GND>Terminal A (at resistor side), or GND>Terminal B (at transistor side); and

○ if GND>Terminal B (at NPN transistor side),

a parasitic NPN transistor is activated by N-layer of other element adjacent to the above-mentioned parasitic diode.

The structure of the IC inevitably forms parasitic elements, the activation of which may cause interference among circuits, and/or malfunctions contributing to breakdown. It is therefore requested to take care not to use the device in such manner that the voltage lower than GND (at P-substrate) may be applied to the input terminal, which may result in activation of parasitic elements.

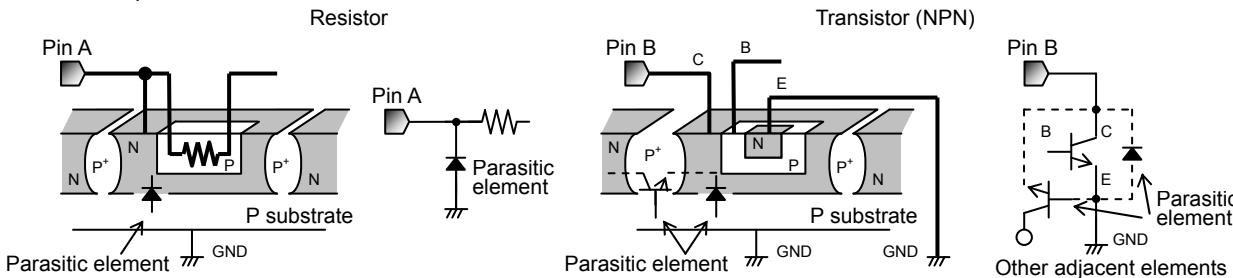


Fig.34 Simplified structure of monolithic IC

8. Ground wiring pattern

If small-signal GND and large-current GND are provided, it will be recommended to separate the large-current GND pattern from the small-signal GND pattern and establish a single ground at the reference point of the set PCB so that resistance to the wiring pattern and voltage fluctuations due to a large current will cause no fluctuations in voltages of the small-signal GND. Pay attention not to cause fluctuations in the GND wiring pattern of external parts as well.

9. Selection of inductor

It is recommended to use an inductor with a series resistance element (DCR) 0.1Ω or less. Note that use of a high DCR inductor will cause an inductor loss, resulting in decreased output voltage. Should this condition continue for a specified period (soft start time + timer latch time), output short circuit protection will be activated and output will be latched OFF. When using an inductor over 0.1Ω, be careful to ensure adequate margins for variation between external devices and this IC, including transient as well as static characteristics. Furthermore, in any case, it is recommended to start up the output with EN after supply voltage is within operation range.

● Ordering part number

B	D
---	---

Part No.

8	9	6	4
---	---	---	---


Part No.

F	V	M
---	---	---

T	R
---	---

Package
FVM:MSOP8Packaging and forming specification
TR: Embossed tape and reel
(MSOP8)

MSOP8

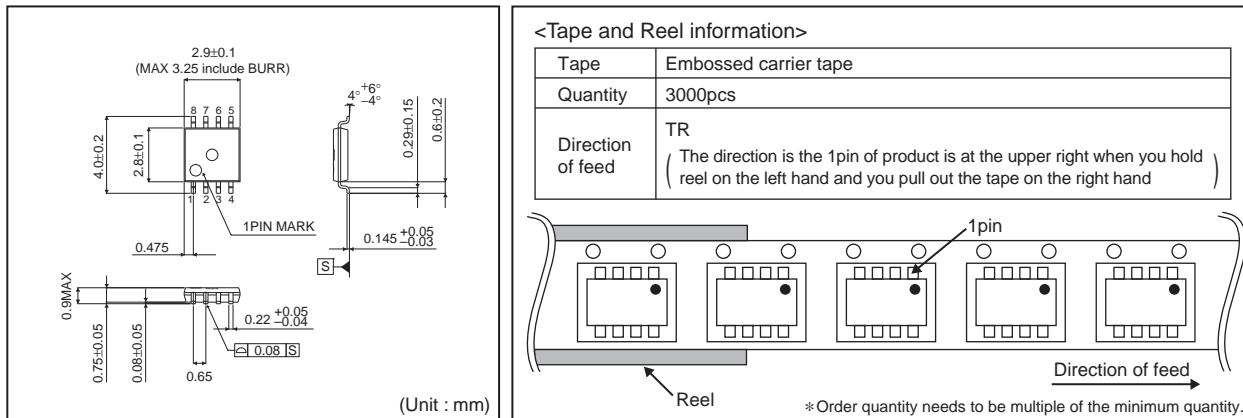

Notes

No copying or reproduction of this document, in part or in whole, is permitted without the consent of ROHM Co.,Ltd.

The content specified herein is subject to change for improvement without notice.

The content specified herein is for the purpose of introducing ROHM's products (hereinafter "Products"). If you wish to use any such Product, please be sure to refer to the specifications, which can be obtained from ROHM upon request.

Examples of application circuits, circuit constants and any other information contained herein illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.

Great care was taken in ensuring the accuracy of the information specified in this document. However, should you incur any damage arising from any inaccuracy or misprint of such information, ROHM shall bear no responsibility for such damage.

The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM and other parties. ROHM shall bear no responsibility whatsoever for any dispute arising from the use of such technical information.

The Products specified in this document are intended to be used with general-use electronic equipment or devices (such as audio visual equipment, office-automation equipment, communication devices, electronic appliances and amusement devices).

The Products specified in this document are not designed to be radiation tolerant.

While ROHM always makes efforts to enhance the quality and reliability of its Products, a Product may fail or malfunction for a variety of reasons.

Please be sure to implement in your equipment using the Products safety measures to guard against the possibility of physical injury, fire or any other damage caused in the event of the failure of any Product, such as derating, redundancy, fire control and fail-safe designs. ROHM shall bear no responsibility whatsoever for your use of any Product outside of the prescribed scope or not in accordance with the instruction manual.

The Products are not designed or manufactured to be used with any equipment, device or system which requires an extremely high level of reliability the failure or malfunction of which may result in a direct threat to human life or create a risk of human injury (such as a medical instrument, transportation equipment, aerospace machinery, nuclear-reactor controller, fuel-controller or other safety device). ROHM shall bear no responsibility in any way for use of any of the Products for the above special purposes. If a Product is intended to be used for any such special purpose, please contact a ROHM sales representative before purchasing.

If you intend to export or ship overseas any Product or technology specified herein that may be controlled under the Foreign Exchange and the Foreign Trade Law, you will be required to obtain a license or permit under the Law.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>