

# **ADC12EU050: Ultra-low Power, Octal, 12-bit, 45MSPS Sigma-Delta Analog-to-Digital Converter**

This Evaluation Board is used to evaluate one of the A/D Converter ADC12EU050. The ADC is a 12 bit converter that provides data at a rate of 45 MHz.

The evaluation board is designed to be used with the WaveVision5™ Data Capture Board which is connected to a personal computer through a USB port and running WaveVision5™ software, operating under Microsoft Windows. The software can perform an FFT on the captured data upon command and, in addition to a frequency domain plot, shows dynamic performance in the form of SNR, SINAD, THD SFDR and ENOB.

## **Contents**

|   |                                              |    |
|---|----------------------------------------------|----|
| 1 | Board Assembly .....                         | 2  |
| 2 | Quick Start .....                            | 2  |
| 3 | Functional Description .....                 | 3  |
|   | 3.1 Analog Input .....                       | 3  |
|   | 3.2 ADC Reference .....                      | 3  |
|   | 3.3 ADC Input Clock .....                    | 3  |
|   | 3.4 Power Supply Connections .....           | 4  |
|   | 3.5 Reset .....                              | 4  |
|   | 3.6 Sleep .....                              | 4  |
|   | 3.7 Input Common Mode .....                  | 5  |
|   | 3.8 Default Jumper and Switch Settings ..... | 5  |
| 4 | Software and SPI Registers .....             | 5  |
|   | 4.1 SPI Registers .....                      | 5  |
| 5 | Hardware Schematics .....                    | 6  |
| 6 | Evaluation Board Layout .....                | 9  |
| 7 | Evaluation Board Bill of Materials .....     | 13 |

## **List of Figures**


|    |                                       |    |
|----|---------------------------------------|----|
| 1  | Major Component Locations.....        | 2  |
| 2  | Input clock circuit.....              | 3  |
| 3  | Power Supply Connections .....        | 4  |
| 4  | Schematic - 1 of 3 .....              | 6  |
| 5  | Schematic - 2 of 3 .....              | 7  |
| 6  | Schematic - 3 of 3 .....              | 8  |
| 7  | Layer 1: Top .....                    | 9  |
| 8  | Layer 2 : Internal Ground Plane ..... | 10 |
| 9  | Layer 3 : Internal Power Plane .....  | 11 |
| 10 | Layer 4: Bottom.....                  | 12 |

## **List of Tables**

|   |                                  |    |
|---|----------------------------------|----|
| 1 | Board Jumpers and Switches ..... | 5  |
| 2 | Bill of Materials.....           | 13 |

## 1 Board Assembly

The ADC12EU050 Evaluation Board comes pre-assembled. Refer to the Bill of Materials in [Section 7](#) for a description of components, to [Figure 1](#) for major component placement and to [Section 5](#) for the Evaluation Board schematic.

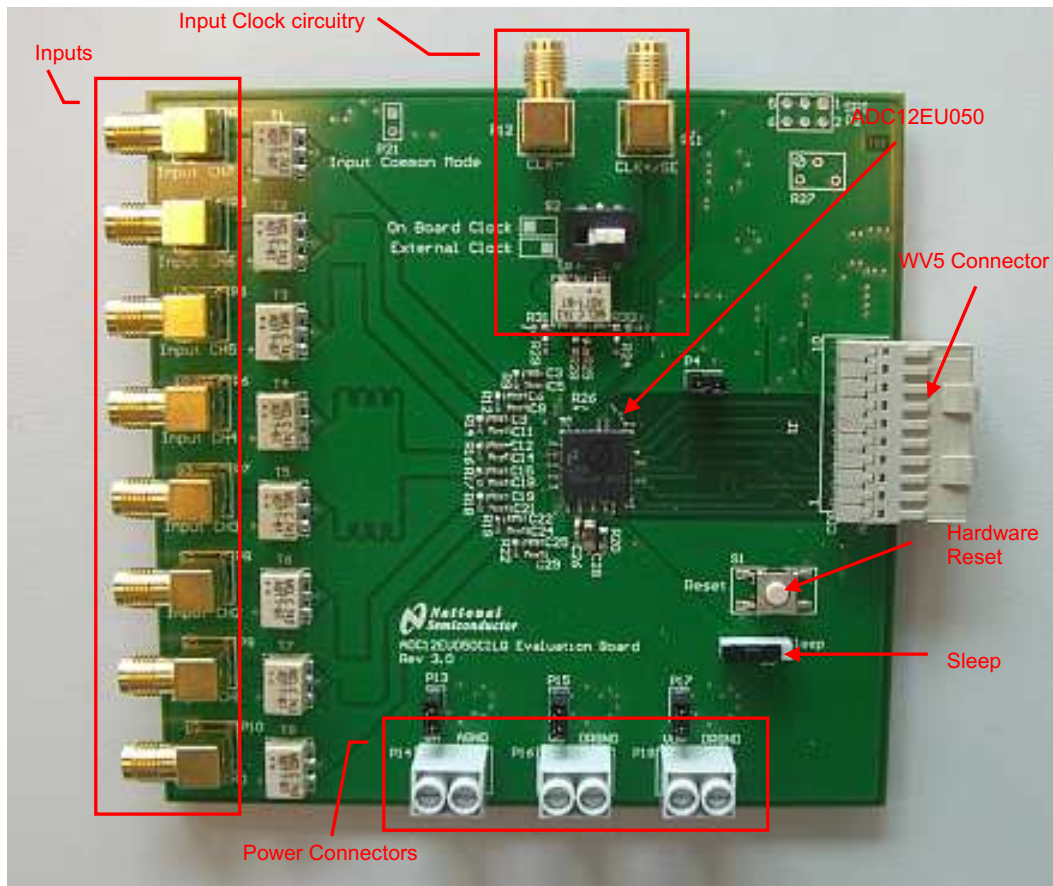

**Figure 1. Major Component Locations**

## 2 Quick Start

Refer to [Figure 1](#) for locations of jumpers, test points and major components. The board is configured by default to use an on board crystal clock source and internal reference. Refer to [Section 3](#) for detailed information on jumper settings.

You must have the WaveVision5™ software to test this board. You can download the latest version from the Texas Instruments website.

1. Connect the ADC12EU050 evaluation board to the WaveVision5™ Data Capture Board.
2. Apply power to the WaveVision5™ Data Capture Board.
3. Connect power to the ADC12EU050 board as described in [Section 3.4](#), and power it up.
4. Connect the WaveVision5™ board to the computer using a USB cable.
5. Start the WaveVision5™ software.
6. Connect a signal from a 50-Ω source to connector a channel input. Be sure to use a bandpass filter before the Evaluation Board.
7. Adjust the input signal amplitude as needed to ensure that the signal does not over-range by examining an FFT of the output data with the WaveVision™ software.

### 3 Functional Description

The ADC12EU050 Evaluation Board schematic is shown in [Section 5](#). A list of default switch and jumper settings can be found in [Section 3.8](#).

#### 3.1 Analog Input

The analog input is supplied through standard SMA connectors. The evaluation board is designed for single ended inputs, which are converted to differential by the transformers.


It must be ensured that a high quality signal source is used so that the ADC dynamic performance can be properly evaluated. A bandpass filter on the input signal is highly recommended.

#### 3.2 ADC Reference

The ADC12EU050 can use an internal or external reference. This evaluation board is configured to use the internal reference.

#### 3.3 ADC Input Clock

The ADC12EU050 can only be clocked at 45MHz. The input clock circuit is shown in [Figure 2](#).

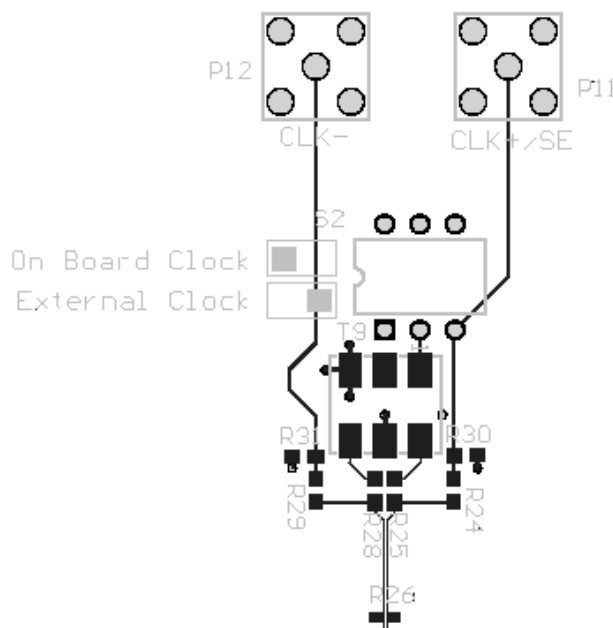

**Figure 2. Input clock circuit**

Select "External Clock" with switch S2 which disables the on-board crystal oscillator. It enables the user to connect a single ended clock to P11. This clock is converted to a differential signal by the transformer T9.

Selecting "On Board Clock" with switch S2 is not supported unless a 45MHz Crystal Oscillator is populated at IC1.


The external clock amplitude and waveform are fairly flexible, but a 600mVpp differential square wave at the chip inputs is recommended.

By changing the 0 ohm resistors R24, R25, R28 and R29 other clock input configurations can be realized. For example, a fully differential clock could be supplied, bypassing the on-board transformer.

If a single ended clock is supplied to the ADC, then the LVDS termination resistor, R26, must be removed.

### 3.4 Power Supply Connections

Power to the board is supplied through the power connectors P14, P16 and P18. The required voltages are shown in Figure 3 and described underneath.

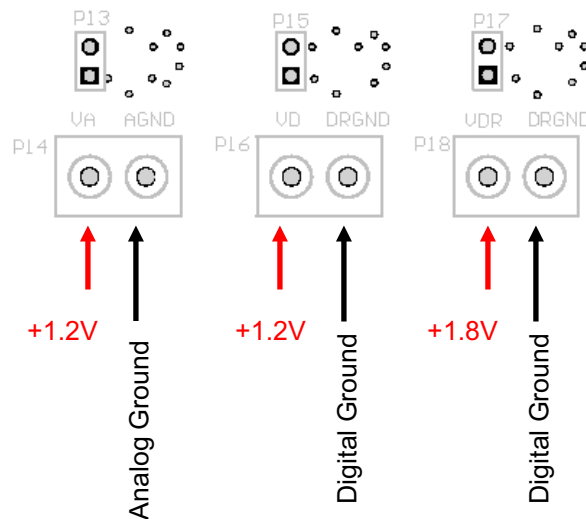

**Figure 3. Power Supply Connections**

P14: Analog power and ground

- ADC12EU050 analog supply, VA.
- Connect VA to 1.2V, AGND to ground
- Current can be measured across P13

P16: Digital power and ground

- ADC12EU050 digital supply, VD
- Connect VD to 1.2V, DRGND to ground
- Current can be measured across P15

P18: Output driver power and ground

- ADC12EU050 output driver supply, VDR
- Connect VDR to 1.8V, DRGND to ground (same as DRGND of P16)
- Current can be measured across P17

Generally, all grounds can be tied together, as can analog and digital supplies (VA and VD).

The data sheet for the ADC12EU050 specifies that the output driver supply voltage (VDR) can be 1.2V or 1.8V. Due to the design of the evaluation system, specifically the distance from the ADC12EU050 to the Xilinx Virtex4 FPGA on the WaveVision5™ board and the connector through which the LVDS outputs are routed, VDR should be kept at 1.8V.

A VDR of 1.2V can be used, but in this case the LVDS current drive ( $I_{drive}$ , SPI register 0x18, bits 3:2) must be increased to 5mA.

### 3.5 Reset

The reset button pulls the RSTb pin of the ADC12EU050 low, resetting the ADC. The reset button only affects the ADC, not any other component on the board, or on the WaveVision5™ board.

### 3.6 Sleep

The sleep switch puts the ADC input sleep mode, by connecting the SLEEP pin to VDR.

### 3.7 Input Common Mode

Jumper P21 can be used to force a common mode on the ADC inputs. In its default configuration, the evaluation board has capacitively coupled ADC inputs, and using the Input Common Mode jumper will not have any effect.

### 3.8 Default Jumper and Switch Settings

On delivery, the board's jumpers and switches should be set as defined in [Table 1](#). Any directions are defined when the board is positioned as in [Figure 1](#).

**Table 1. Board Jumpers and Switches**

| Jumper or Switch | Default Position             |
|------------------|------------------------------|
| P2               | Open                         |
| P4               | Closed                       |
| P13              | Closed                       |
| P15              | Closed                       |
| P17              | Closed                       |
| P21              | Open                         |
| S2               | Left (On Board Clock)        |
| S3               | Left (Sleep mode not active) |

## 4 Software and SPI Registers

The ADC12EU050 evaluation board is designed to be used with the WaveVision5™ data capture board and software. The latest version of the WaveVision5™ software must be used.

### 4.1 SPI Registers

As described in the ADC12EU050 datasheet, there are many user registers accessible via the SPI interface.

These registers can all be programmed via the "Registers" tab in the WaveVision5™ software.

All registers and values are described in the ADC12EU050 data sheet, which is available from the Texas Instruments website.

## 5 Hardware Schematics


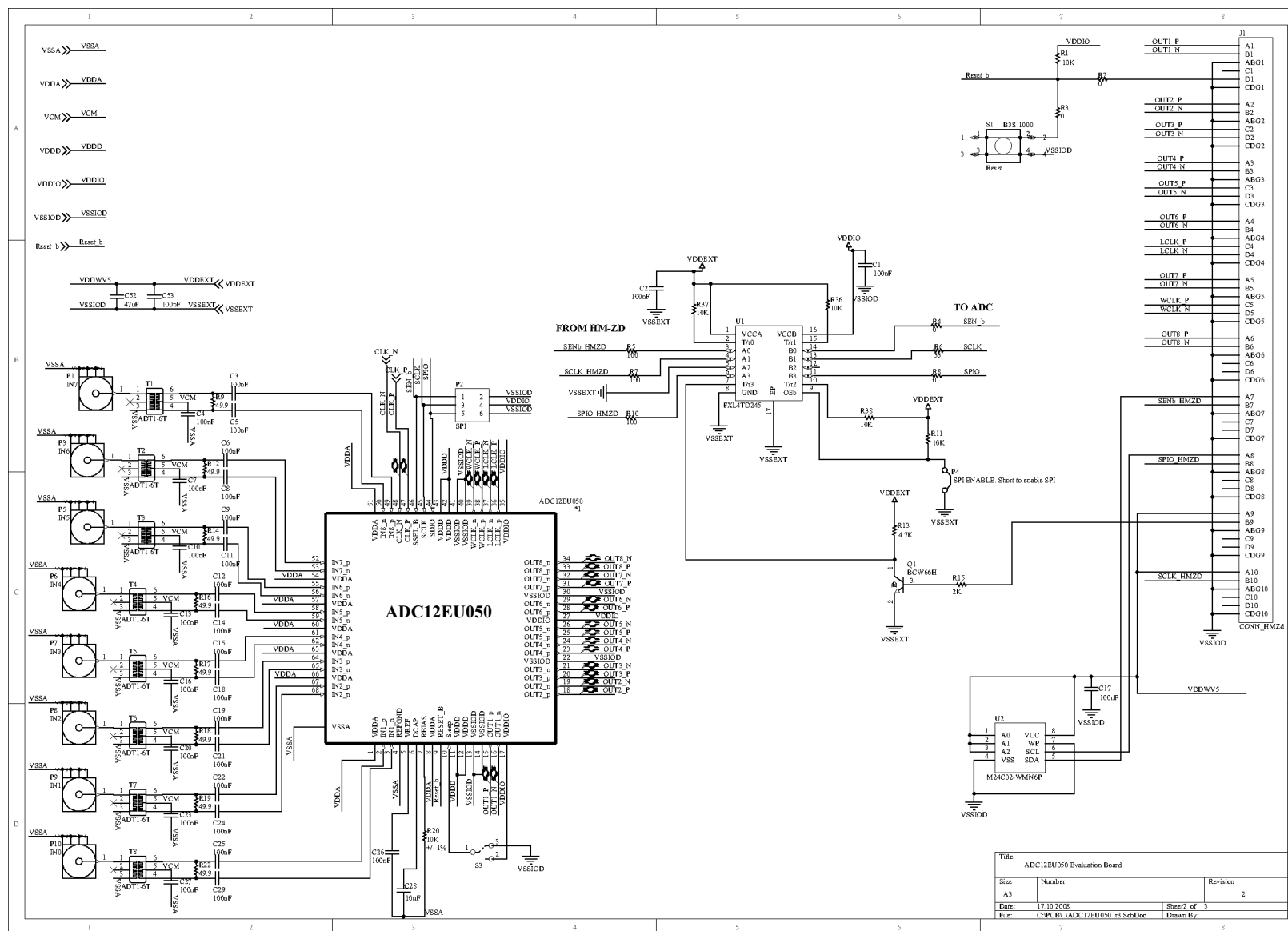



Figure 4. Schematic - 1 of 3

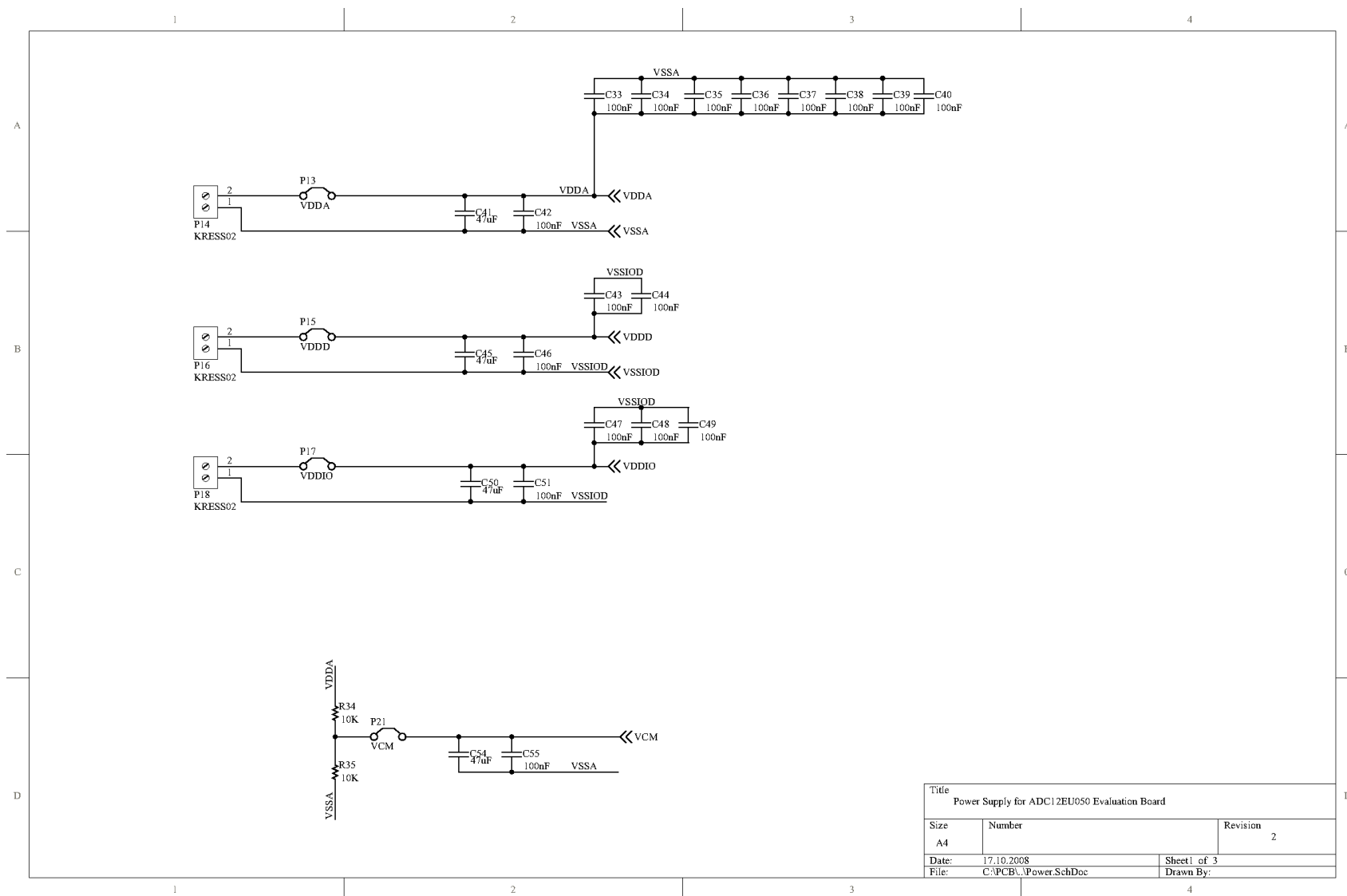

**Figure 5. Schematic - 2 of 3**



## 6 Evaluation Board Layout

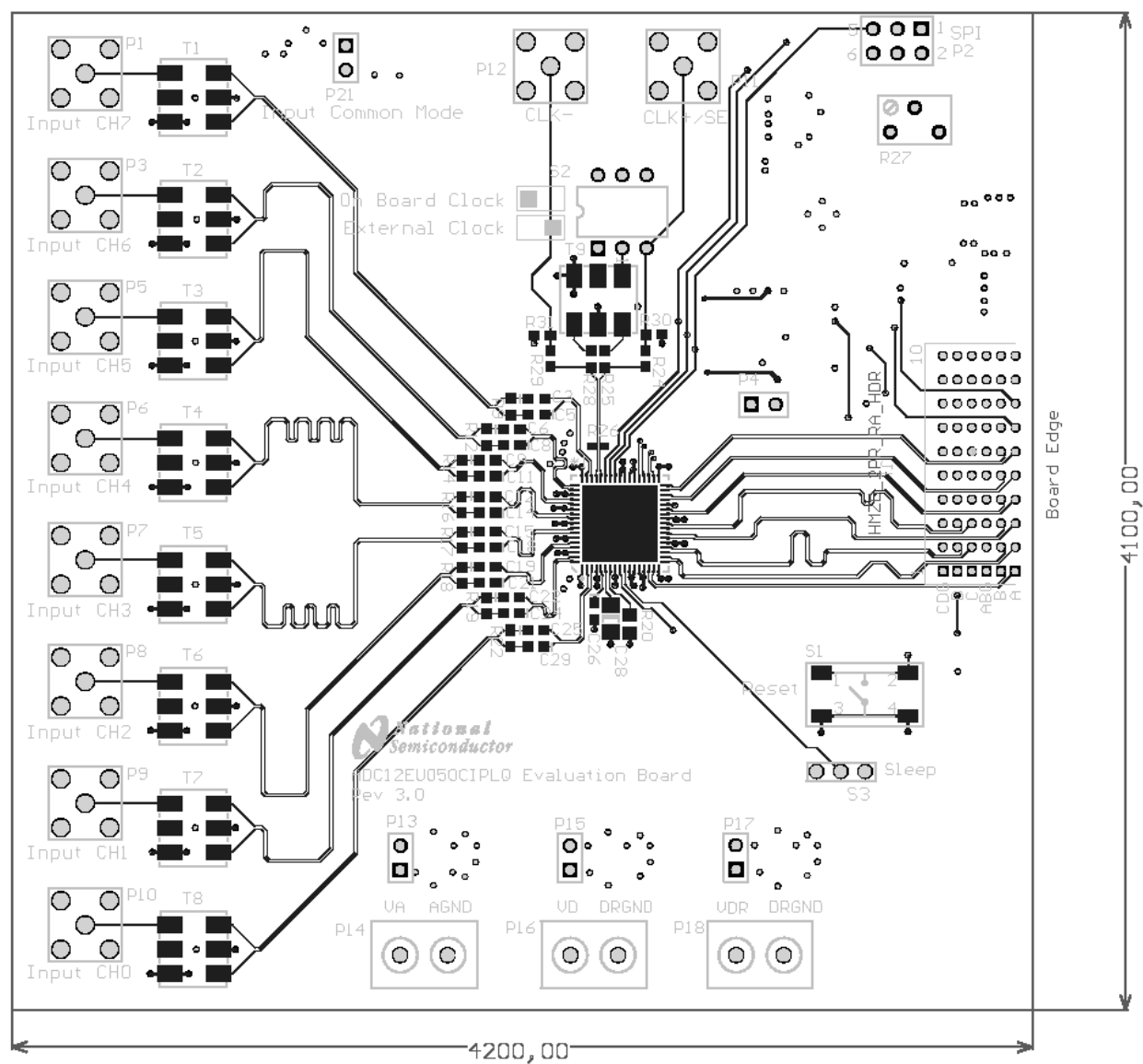

**Figure 7. Layer 1: Top**



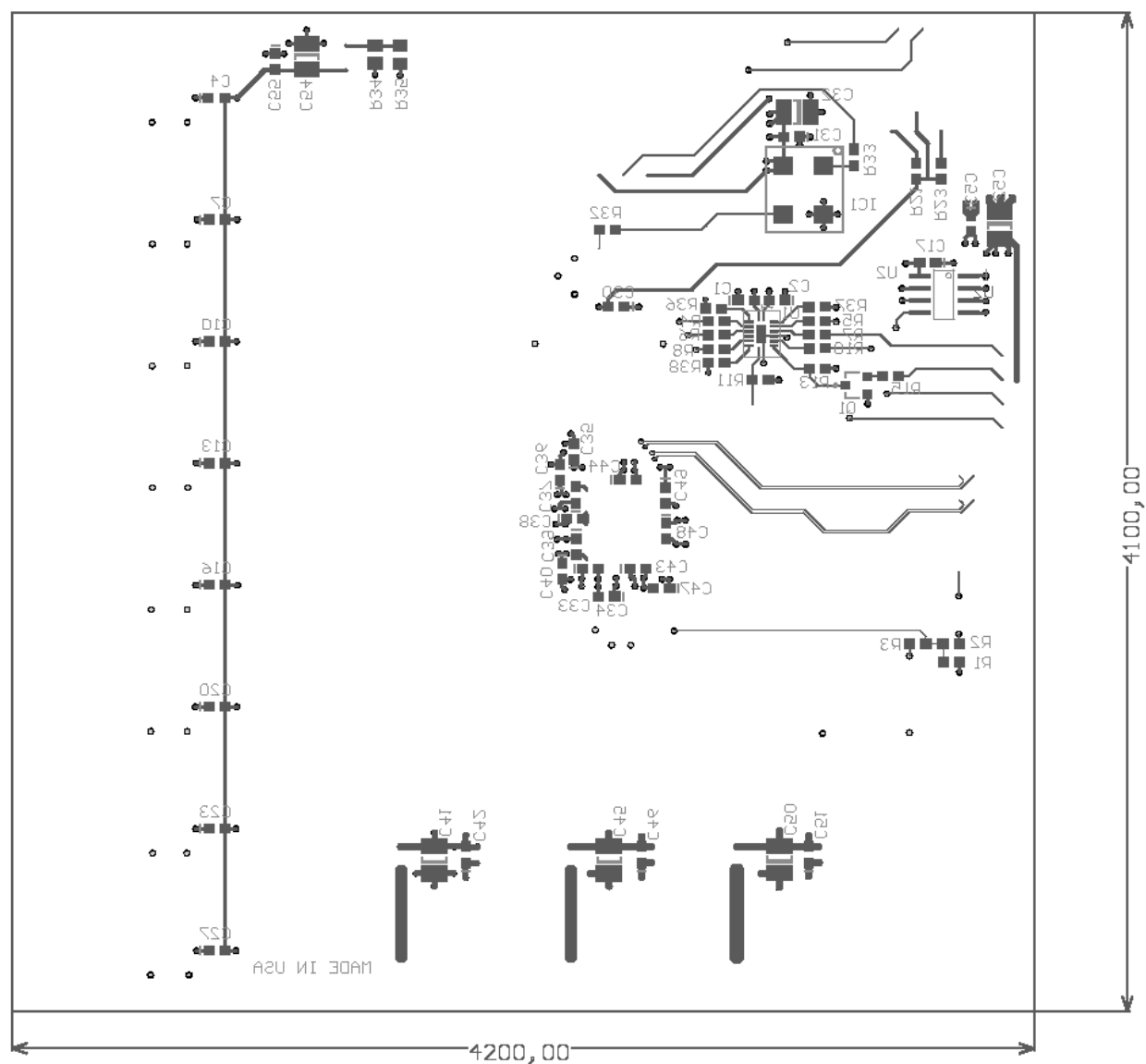


Figure 8. Layer 2 : Internal Ground Plane

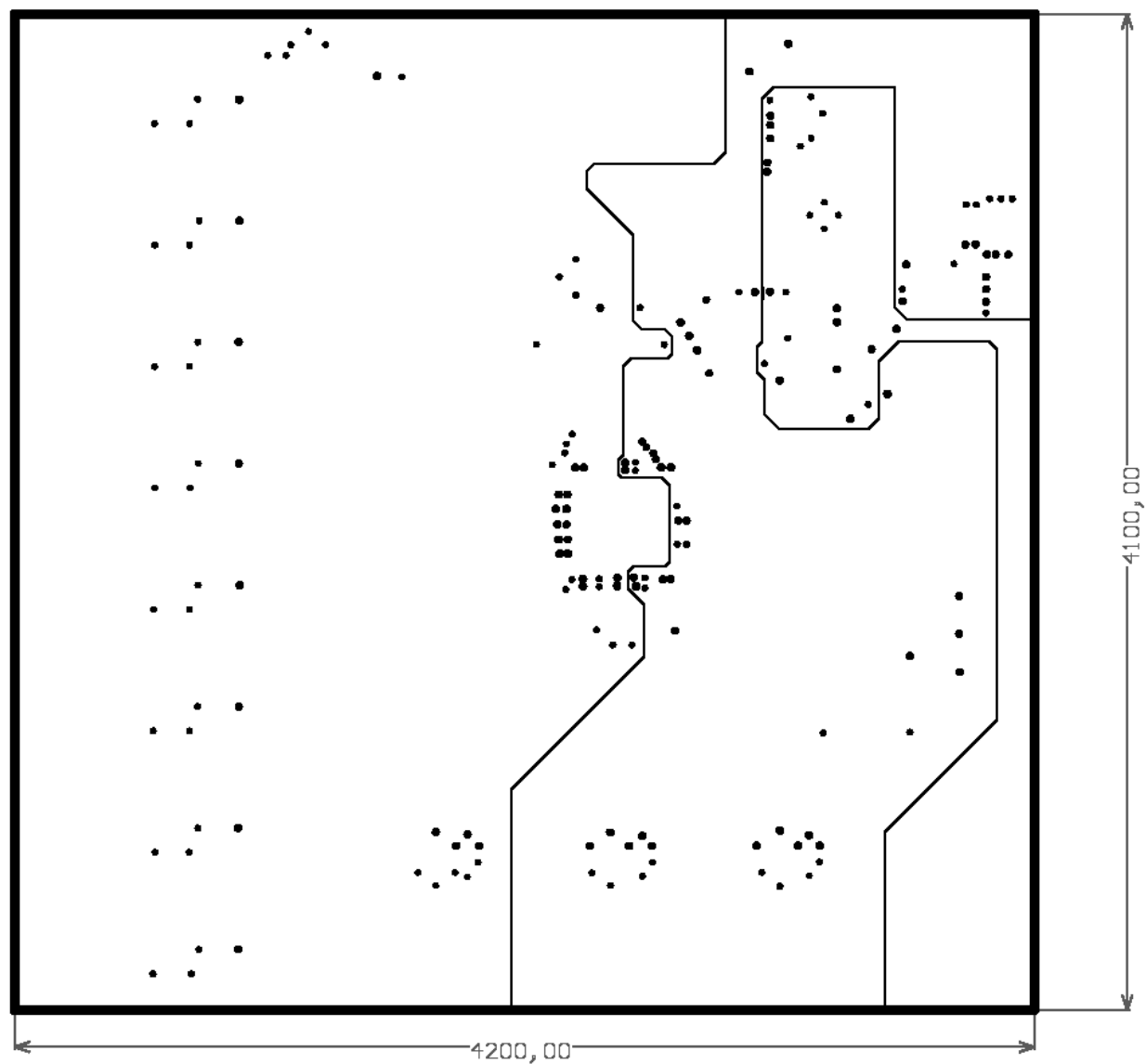

**Figure 9. Layer 3 : Internal Power Plane**

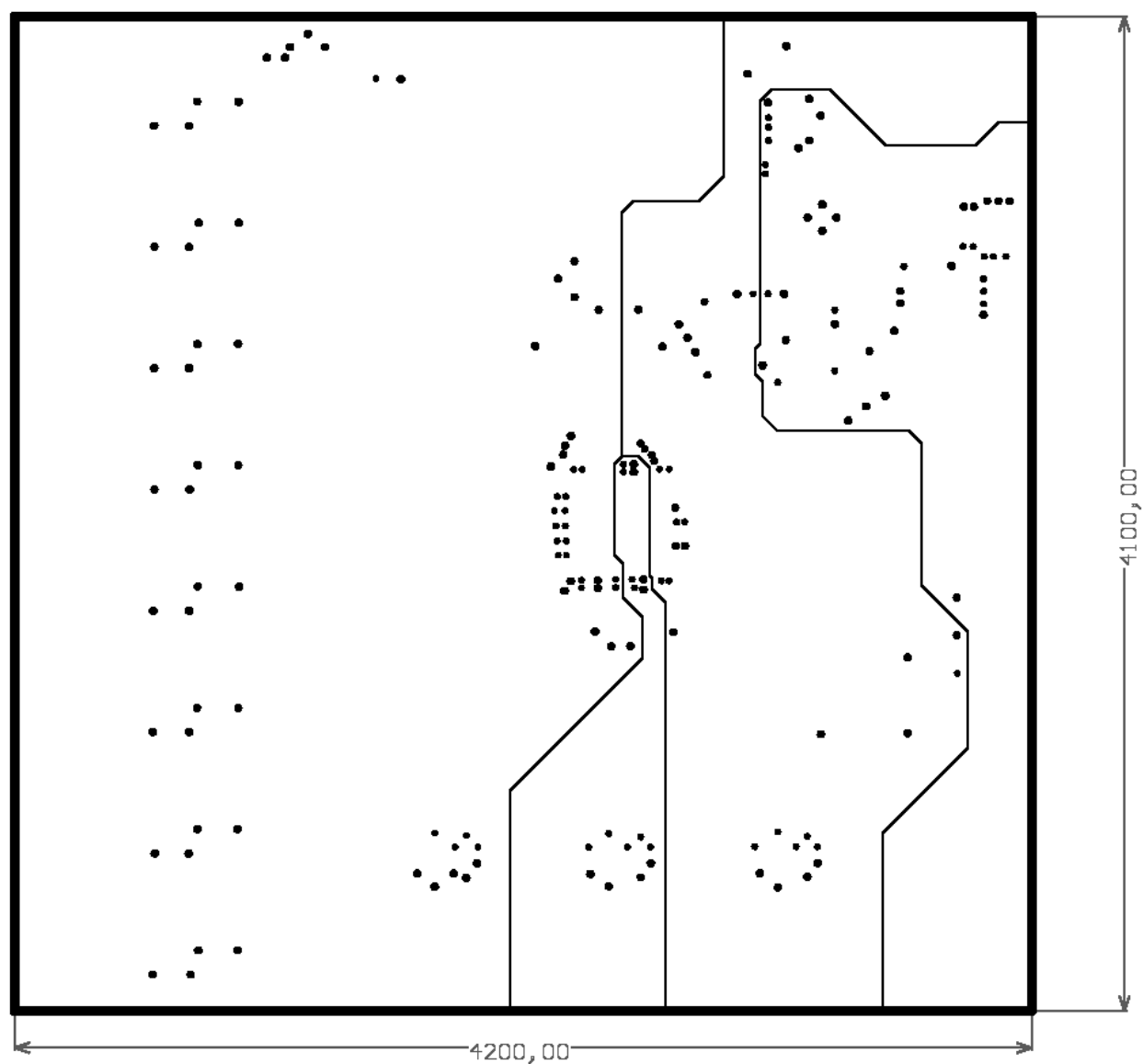

**Figure 10. Layer 4: Bottom**

## 7 Evaluation Board Bill of Materials

**Table 2. Bill of Materials**

| QTY. | Designator                                             | Footprint           | Value                                        | Description                                                                               |
|------|--------------------------------------------------------|---------------------|----------------------------------------------|-------------------------------------------------------------------------------------------|
| 1    | *1                                                     | QFN10X10-68         | ADC12EU050                                   | ADC                                                                                       |
| 48   | C1–C31, C33–C40,<br>C42–C44, C46–C49,<br>C51, C53, C55 | CC1608-0603         | 100nF                                        | Capacitor (Semiconductor SIM Model)                                                       |
| 1    | C28                                                    | CC3216-1206         | 10uF                                         | Capacitor (Semiconductor SIM Model)                                                       |
| 6    | C32, C41, C45, C50,<br>C52, C54                        | CC3225-1210         | 47uF                                         | Capacitor (Semiconductor SIM Model)                                                       |
| 1    | IC1                                                    | CSX750FJC           | Citizen CSX750FJC50.000M-UT                  | Crystal Oscillator                                                                        |
| 1    | J1                                                     | HMZD_2PR_RA_HDR     | HMZd – Tyco Electronics part no<br>6469028-1 | HMZd Connector 60 pin                                                                     |
| 10   | P1, P3, P5–P12                                         | SMA                 |                                              | RF Coaxial PCB Connector, MMCX; Thru-<br>Hole, Vertical Mount Plug, 50 $\Omega$ Impedance |
| 1    | P2                                                     | HDR2X3              | Header 2x3                                   | Header, 3-Pin, Dual row                                                                   |
| 4    | P14, P16, P18                                          | LP2                 | Lumberg KRESS02 Terminal Block               | Terminal Block                                                                            |
| 4    | P4, P13, P15, P17, P21                                 | HDR1X2              | Header2x1                                    | Jumper Wire                                                                               |
| 1    | Q1                                                     | SOT23               | BCW66H                                       | NPN General Purpose Transistor                                                            |
| 9    | R33, R24, R25, R28,<br>R29, R4, R8, R2, R3             | CR1608-0603         | 0                                            | Semiconductor Resistor                                                                    |
| 1    | R15                                                    | CR1608-0603         | 2K                                           | Semiconductor Resistor                                                                    |
| 1    | R13                                                    | CR1608-0603         | 4.7K                                         | Semiconductor Resistor                                                                    |
| 7    | R11, R36, R37, R38,<br>R1, R21, R23                    | CR1608-0603         | 10K                                          | Semiconductor Resistor                                                                    |
| 1    | R6                                                     | CR1608-0603         | 33                                           | Semiconductor Resistor                                                                    |
| 10   | R9, R12, R14,<br>R16–R19, R22, R30,<br>R31             | CR1608-0603         | 49.9                                         | Semiconductor Resistor                                                                    |
| 4    | R32, R5, R7, R10                                       | CR1608-0603         | 100                                          | Semiconductor Resistor                                                                    |
| 3    | R20, R34, R35                                          | CR2012-0805         | 10K $\pm$ 1%                                 | Semiconductor Resistor                                                                    |
| 1    | R26                                                    | CR1005-0402         | 100                                          | Semiconductor Resistor                                                                    |
| 1    | R27                                                    | 3296Y               | 25K                                          | Potentiometer                                                                             |
| 1    | S1                                                     | PushButton          | OMRON B3S-1000                               | Push Button                                                                               |
| 1    | S2                                                     | DIP-6               | Tyco ASE22                                   | Double-Pole, Double-Throw Switch                                                          |
| 1    | S3                                                     | SW-DIP1             | EAO part no 09-03290-01                      | Single Switch                                                                             |
| 9    | T1–T9                                                  | ADT1-6T             | Mini Circuits ADT1-6T                        | Transformer                                                                               |
| 1    | U1                                                     | DQFN_50M_16_2P5X3P5 | FXL4TD245                                    | 4-bit level shifter                                                                       |
| 1    | U2                                                     | SOIC8_05_WG244_L200 | M24C02-WMN6P                                 | EEPROM, STMicroelectronics,<br>M24C02-WMN6P                                               |

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

|                              |                                                                                      |
|------------------------------|--------------------------------------------------------------------------------------|
| Audio                        | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                               |
| Amplifiers                   | <a href="http://amplifier.ti.com">amplifier.ti.com</a>                               |
| Data Converters              | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>                       |
| DLP® Products                | <a href="http://www.dlp.com">www.dlp.com</a>                                         |
| DSP                          | <a href="http://dsp.ti.com">dsp.ti.com</a>                                           |
| Clocks and Timers            | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>                             |
| Interface                    | <a href="http://interface.ti.com">interface.ti.com</a>                               |
| Logic                        | <a href="http://logic.ti.com">logic.ti.com</a>                                       |
| Power Mgmt                   | <a href="http://power.ti.com">power.ti.com</a>                                       |
| Microcontrollers             | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a>                   |
| RFID                         | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>                                 |
| OMAP Applications Processors | <a href="http://www.ti.com/omap">www.ti.com/omap</a>                                 |
| Wireless Connectivity        | <a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a> |

### Applications

|                               |                                                                                          |
|-------------------------------|------------------------------------------------------------------------------------------|
| Automotive and Transportation | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>                         |
| Communications and Telecom    | <a href="http://www.ti.com/communications">www.ti.com/communications</a>                 |
| Computers and Peripherals     | <a href="http://www.ti.com/computers">www.ti.com/computers</a>                           |
| Consumer Electronics          | <a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>                   |
| Energy and Lighting           | <a href="http://www.ti.com/energy">www.ti.com/energy</a>                                 |
| Industrial                    | <a href="http://www.ti.com/industrial">www.ti.com/industrial</a>                         |
| Medical                       | <a href="http://www.ti.com/medical">www.ti.com/medical</a>                               |
| Security                      | <a href="http://www.ti.com/security">www.ti.com/security</a>                             |
| Space, Avionics and Defense   | <a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a> |
| Video and Imaging             | <a href="http://www.ti.com/video">www.ti.com/video</a>                                   |

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)